



ACE

Engineering Academy



Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Bengaluru | Lucknow | Patna | Chennai | Vijayawada | Visakhapatnam | Tirupati | Kukatpally | Kolkata

H.O: 204, II Floor, Rahman Plaza, Opp. Methodist School, Abids, Hyderabad-500001,

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

ACE Pre-GATE 2017

Branch: EE

Q.1 – Q.5 Carry One Mark Each

01. Reaching a place of appointment on Friday. I found that I was two days earlier than the scheduled day. If I had reached on the following Wednesday then how many days late would I have been?

- (a) one (b) Two
(c) three (d) four

01. Ans: (c)

Sol: Friday → 2 days earlier

Therefore, scheduled day = Friday + 2 = Sunday

Sunday + 3 = Wednesday

Therefore, I would have been late by 3 days

02. Choose the most appropriate phrase from the options given below to complete the following sentence.

The bus stopped to _____ more passengers.

- (a) Take in (b) Take on
(c) Take up (d) Take for

02. Ans: (b)

03. Choose the appropriate sentence from the following options.

- (a) She has been discharged since.
(b) She has since been discharged.
(c) She has been since discharged.
(d) She since has been discharged.

03. Ans: (b)



04. Fill in the blank with an appropriate phrase.

The jet _____ into the air.

- (a) Soared. (b) Soured.
(c) Sourced. (d) Sored.

04. Ans: (a)

05. Choose the most appropriate word from the options given below to complete the following sentence.

If I had known that you were coming, I _____ you at the airport.

- (a) Would meet (b) Would have met
(c) Will have met (d) Had met

05. Ans: (b)

SHORT TERM BATCHES FOR GATE+PSUs - 2018

HYDERABAD

29TH APRIL 2017

06TH MAY 2017

13TH MAY 2017

18TH MAY 2017

01ST JUNE 2017

NEW BATCHES FOR ESE | GATE | PSUs - 2018

CONTACT : 040 - 23234418 / 19 / 20

www.aceenggacademy.com



Q.6 – Q.10 Carry two marks each

06. Which of the following can be logically inferred from the given statement.

“No other studied medicine except Helen”

- (a) Helen only studied medicine
- (b) Only Helen studied medicine
- (c) Helen studied only medicine
- (d) Helen studied medicine only

06. Ans: (b)

07. The average electricity bill of a household for January to June is ₹ 980, for July to September is ₹ 670, for October to December is ₹ 720. If the family goes on vacation for June and July and no electricity is used, what would be the average electricity bill for that year?

- (a) ₹ 500
- (b) ₹ 600
- (c) ₹ 700
- (d) ₹ 800

07. Ans: (c)

Sol: Average electricity bill from January to June = ₹ 980

∴ Total electricity bill from January to May = $980 \times 5 = ₹ 4900$

(As no electricity is used in June)

Similarly, total electricity bill from August to September (as no electricity is used in July)
= $670 \times 2 = ₹ 1340$

And total electricity bill from October to December = $720 \times 3 = ₹ 2160$

Therefore, total electricity bill from January to December = $4900 + 1340 + 2160 = ₹ 8400$

Thus, average electricity bill for the whole year = $\frac{8400}{12} = ₹ 700$

08. The following question has four statements of three segments each. Choose the alternative where the third segment in the statement can be deduced using both the preceding two but not just from one of them.

A. Sonia is an actress. Some actresses are pretty. Sonia is pretty.

B. All actors are pretty. Manoj is not an actor. Manoj is not pretty



- C. Some men are cops. Some men are brave. Some brave people are cops.
 D. All cops are brave. Some men are cops. Some men are brave.


- (a) only C (b) only A (c) only D (d) B and C

08. Ans: (c)

Sol: Statements:

All cops are brave

Some men are cops

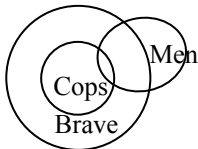

Conclusion:

Some men are brave (True)

Hence, only D follows.

09. A contractor, who got the contract for building the flyover, failed to construct the flyover in the specified time and was supposed to pay ₹ 50,000 for the first day of extra time. This amount increased by ₹ 4,000 each day. If he completes the flyover after one month of stipulated time, he suffers a loss of 10% in the business. What is the amount he received for making the flyover in crores of rupee? (One month = 30 days)

- (a) 3.1 (b) 3.24 (c) 3.46 (d) 3.68

09. Ans: (b)

Sol: The sum of money that the contractor was supposed to pay for the period of an month over the stipulated time is

$$= S_n = \frac{n}{2}[2a + (n-1)d]$$

$$a = 50,000, n = 30, d = 4000$$

$$S_{30} = \frac{30}{2}[2 \times 50,000 + (30-1) \times 4000] = 15[100,000 + 29 \times 4000]$$



₹ 3240000 = ₹ 32.4 lakhs


Loss in the business = 10%

∴ Amount he received for making the flyover = $\frac{3240000}{0.1} = 32400,000 = ₹ 3.24$ crores

10. Study the following pie chart and table carefully to answer the following question that follow: Percentage break up of employees working in various departments of an organisation and the ratio of men to women in them.

Total number of employees = 1800

Percentage break up of employees:

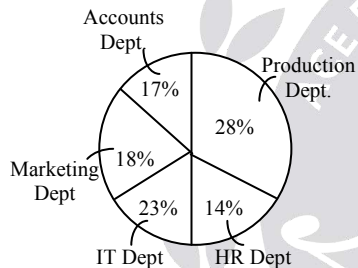

Ratio of men to women

Department	Men	Women
Production	11	1
HR	1	3
IT	5	4
Marketing	7	5
Accounts	2	7

What is the number of men working in the marketing department?

- (a) 132
- (b) 174
- (c) 126
- (d) 189


10. Ans: (d)

Sol: Number of men working in the marketing department = $1800 \times \frac{18}{100} \times \frac{7}{12} = 189$




Q.11 – Q.35 Carry one mark each.

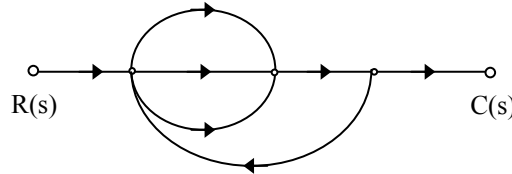11. The number of loops in the following signal flow graph is/are _____



Ans: 3 (Range 3 to 3)

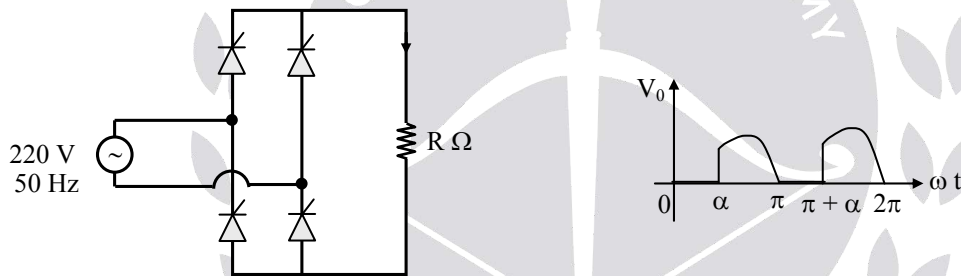12. Input voltage to the following single phase bridge rectifier is 220 V (RMS), 50 Hz. The load resistance is 7 Ω. The delay angle (in degree) required to deliver 3.61 kW is _____.



Ans:88 (Range 88.0 to 88.3)

$$\text{Sol: } V_{or}^2 = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t$$

$$= \frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]$$

$$P_0 = \frac{V_{or}^2}{R} = \frac{V_m^2}{2\pi R} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]$$

$$= \frac{(220\sqrt{2})^2}{2\pi \times 7} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] = 3610$$

$$\Rightarrow (\pi - \alpha) + \frac{1}{2} \sin 2\alpha = 1.64 \Rightarrow \alpha = 88^\circ$$



13. $\lim_{x \rightarrow \infty} \sqrt{(x^2 + x + 1)} - x = \underline{\hspace{2cm}}$

Ans: 0.5

Sol: $\lim_{x \rightarrow \infty} \sqrt{(x^2 + x + 1)} - x = \lim_{x \rightarrow \infty} \left[\sqrt{x^2 + x + 1} - x \right] \left[\frac{\sqrt{x^2 + x + 1} + x}{\sqrt{x^2 + x + 1} + x} \right]$

$$= \frac{1 + 0}{\sqrt{1 + 0 + 0} + 1} = \frac{1}{2}$$

14. The area frequency response characteristics of a 200MW, 50Hz power system is 105 MW/Hz and regulation constant is 0.01Hz/MW. The load frequency constant of power system is _____ MW/Hz

Ans: 5 (no range)

Sol: $B = D + \frac{1}{R}$

$$105 = D + \frac{1}{0.01} \Rightarrow D = 5 \text{ MW / Hz}$$

15. The signal $x(t) = \cos(50\pi t) + \cos(80\pi t)$ is sampled at 200Hz. The minimum number of samples required to prevent leakage is _____

Ans: 40 (No Range)


Sol: $\frac{\omega_1 T_s}{2\pi} = \frac{50\pi/200}{2\pi} = \frac{1}{8} = \frac{5}{40}$

$$\frac{\omega_2 T_s}{2\pi} = \frac{80\pi/200}{2\pi} = \frac{1}{5} = \frac{8}{40}$$

\therefore The minimum number of samples required to prevent leakage is 40



16. What is $V_{c_1}(0^+) = ?$

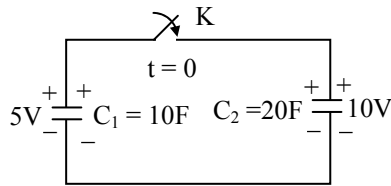

(a) $\frac{25}{3}$ V

(b) $\frac{20}{3}$ V

(c) 5V

(d) None

Ans: (a)

Sol: $V_{c_1}(0^+) = \frac{5 \times 10}{30} + \frac{10 \times 20}{30} = \frac{5}{3} + \frac{20}{3} = \frac{25}{3}$

DISTRACTOR LOGIC:

Option: B $V_{c_1}(0^+) = \frac{10 \times 20}{30} = \frac{20}{3}$

Option: C $V_{c_1}(0^+) = V_{c_1}(0^-) = 5$ V

Option: D At $t=0^+$ KVL is violated

17. A 3- ϕ , 460V, 1740 rpm, 60Hz, 4 pole WRIM has the following parameter per phase

$R_1 = 0.25 \Omega, R_2^1 = 0.2\Omega$

$X_1 = X_2^1 = 0.5 \Omega, X_m = 30\Omega$

The rotational losses are 1700 W with the rotor terminals short circuited. Find breakdown frequency, when motor is operated from a 3- ϕ , 460V, 60Hz supply.

(A) 0.39 HZ

(B) 11.5 HZ

(C) 11.75 HZ

(D) 26.44 HZ

Ans: (c)

Sol: $S_{T_{max}} = \frac{0.2}{\sqrt{0.25^2 + (0.49 + 0.5)^2}}$

$= 0.1958$

$f_{2_{T_{max}}} = 0.1958 \times 60 = 11.752$ Hz



DISTRACTOR LOGIC

Option:A

Sol: $S_{T_{max}} = \frac{0.2}{\sqrt{0.25^2 + (30 + 0.5)^2}}$
 $= 0.0065$

$f_{2_{T_{max}}} = 0.0065 \times 60 = 0.39 \text{ Hz}$

Option B:

$S_{T_{max}} = \frac{0.2}{0.25^2 + (0.49 + 0.5)^2}$
 $= 0.1918$

$f_{2_{T_{max}}} = 0.1918 \times 60 = 11.5 \text{ Hz}$

Option:D

$S_{T_{max}} = \frac{0.45}{\sqrt{0.25^2 + (0.49 + 0.5)^2}}$
 $= 0.4407$


$f_{2_{T_{max}}} = 0.4407 \times 60 = 26.44 \text{ Hz}$

18. An electro-dynamometer wattmeter measures a power in single phase, 50 Hz AC circuit. The load voltage is 230V and load current is 10A at 0.5 lagging p.f. The wattmeter pressure coil resistance is 10kΩ and inductance is 100mH, then % error will be

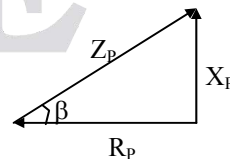- (A) zero (B) -1.68% (C) 0.54% (D) 0.156%

Ans: (C)

Sol: $\tan \beta = \frac{X_p}{R_p}$
 $= \frac{2\pi \times 50 \times 100 \times 10^{-3}}{10 \times 10^3} = 0.00312$



$\beta = 0.179$

% error = $+(\tan \phi \tan \beta) \times 100$
 $= 1.732 \times 0.00312 \times 100$
 $= 0.54 \%$



DISTRACTOR LOGIC

Option: (A) There is no effect of pressure coil resistance on wattmeter reading

Option: (B) if it is energy meter

$$\begin{aligned} \% \text{ error} &= \frac{\sin(10-30) - 0.5}{0.5} \times 100 \\ &= -1.68\% \end{aligned}$$

Option: (D) $\% \text{ error} = + (\cos\phi \tan\beta) \times 100$
 $= 0.5 \times 0.00312 \times 100 = 0.156\%$

19. If A, B & C are $n \times n$ matrices and $|A| = 2$, $|B| = 3$ & $|C| = 5$ then the value of $|A^2 B C^{-1}| = ?$

(A) $\frac{6}{5}$

(B) $\frac{12}{5}$

(C) $\frac{18}{5}$

(D) $\frac{24}{5}$

Ans: (B)

Sol: $|A^2 B C^{-1}| = \frac{|A||A||B|}{|C|} = \frac{2 \times 2 \times 3}{5} = \frac{12}{5}$

NEW BATCHES FOR


ESE – 2017 Stage – II (Mains)

BATCH - 1	BATCH - 2
18 th Jan 2017 (E&T, EE, CE & ME)	9 th Feb 2017 (E&T & ME)
	15 th Feb 2017 (EE & CE)

ESE - 2017 MAINS OFFLINE TEST SERIES
 WILL BE CONDUCTED FROM MARCH 1ST WEEK
 DETAILED SCHEDULE WILL BE ANNOUNCED SOON



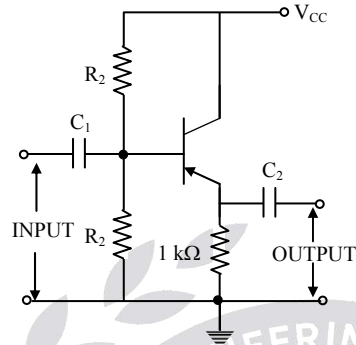20. In the amplifier circuit shown in figure, the transistor parameters with usual notations are $g_m = 0.015S$, $r_{be}^1 = 1K$, $r_{bb}^1 = 90\Omega$, $C_{be}^1 = 20pF$ and $C_{bc}^1 = 3pF$. Neglecting the loading effect of biasing resistors, R_1 & R_2 , the mid-frequency voltage gain of the amplifier is



(A) - 13.76


(B) 0

(C) 0.936

(D) 1

Ans: (C)

Sol:

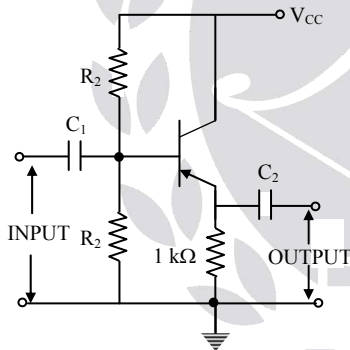

Consider the parameters of BJT

$$r_{be}^1 = 1K, r_{bb}^1 = 90\Omega \text{ \& } g_m = 0.015S,$$

Step(1) : $h_{ie} = r_{be}^1 + r_{bb}^1 = 1090\Omega$

Consider, $r_{be}^1 = \frac{h_{fe}}{g_m} \Rightarrow h_{fe} = r_{be}^1 \times g_m = 1k\Omega \times 0.015 \text{ S} = 15$

Step(2): The given circuit is emitter follower (CC Amplifier)

\therefore The mid-frequency voltage gain in a CC amplifier,

$$A_V = \frac{(1 + h_{fe})R_E}{h_{ie} + (1 + h_{fe})R_E} = \frac{16 \times 1K}{1.09K + 16 \times 1K} = \frac{16K}{17.09K}$$

$$A_V = 0.936$$



DISTRACTOR LOGIC

Option: A: If the given circuit is assumed as CE Amplifier, with a load resistance of $R_L=1k$; then,

$$\text{Step(1)} : h_{ie} = r_{be}^1 + r_{bb}^1 = 1090\Omega$$

$$\text{Consider, } r_{be}^1 = \frac{h_{fe}}{g_m} \Rightarrow h_{fe} = r_{be}^1 \times g_m = 1k\Omega \times 0.015 \text{ U} = 15$$

$$\text{Step(2): } A_v = - \frac{h_{fe} R_L}{h_{ie}} = - \frac{15 \times 1k}{1.09k} = -13.76$$

Option: B If the given circuit is assumed as CE Amplifier, with load resistance of R_c ;

$$\text{Step(1)} : h_{ie} = r_{be}^1 + r_{bb}^1 = 1090\Omega$$

$$\text{Consider, } r_{be}^1 = \frac{h_{fe}}{g_m} \Rightarrow h_{fe} = r_{be}^1 \times g_m = 1k\Omega \times 0.015 \text{ U} = 15$$


Step(2) : As $R_c = 0$ given in the circuit.

$$A_v = - \frac{h_{fe} R_c}{h_{ie}} = - \frac{15 \times 0}{1.09k} = 0$$

Option : C: CC Amplifier; $A_v = 0.936$

Option : D : The voltage gain in a cc amplifier ideally is '1'

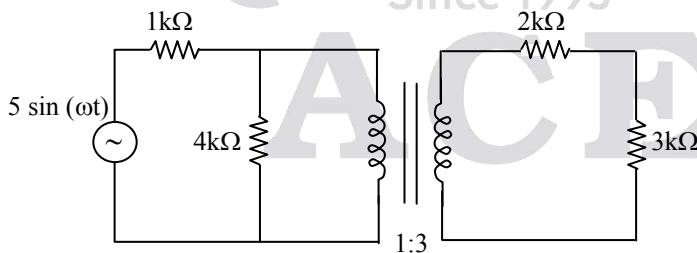21. The AC source in the circuit shown below has a voltage magnitude of 5 volts, which is divided partly over the $1k\Omega$ resistor and the remainder over the rest of the circuit. Compute the magnitude of the voltage over the $1k\Omega$.



(A) 0.1 V

(B) 0.89 V

(C) 1.08 V

(D) 3.36 V

Ans: (D)

Sol: First, find the equivalent resistance looking into the primary (left) terminals of the transformer. The resistance on the right side of the transformer is $5 k\Omega$ since the $2 k\Omega$ and $3 k\Omega$ are in series. This is

then reflected to the left side by the transformer resistance equation: $R_{eq} = \left(\frac{1}{3}\right)^2 5k\Omega$



$R_{eq} = 0.56 \text{ k}\Omega$ Now we have the $4 \text{ k}\Omega$ and $0.56 \text{ k}\Omega$ resistors in parallel, which is $0.488 \text{ k}\Omega$. The $0.488 \text{ k}\Omega$ is in series with the $1 \text{ k}\Omega$, so we can use a voltage divider equation to find the voltage

over the $1 \text{ k}\Omega$ resistor:
$$V = \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 0.488 \text{ k}\Omega} \right) 5 \text{ V}$$

$$V = 3.36 \text{ V}$$

DISTRACTOR LOGIC

Option A: $R_{eq} = (3)^2 \times 5 \text{ k}\Omega = 45 \text{ k}\Omega$

$4 \text{ k}\Omega$ series with $45 \text{ k}\Omega$ and is equal to $49 \text{ k}\Omega$.

$$V = \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 49 \text{ k}\Omega} \right) 5 \text{ V} = 0.1 \text{ V}$$

Option B: $R_{eq} = \left(\frac{1}{3} \right)^2 5 \text{ k}\Omega = 0.56 \text{ k}\Omega$

$4 \text{ k}\Omega$ in series with $0.56 \text{ k}\Omega$ and is equal to $4.56 \text{ k}\Omega$.

$$V = \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 4.56 \text{ k}\Omega} \right) 5 \text{ V} = 0.89 \text{ V}$$

Option C: $R_{eq} = (3)^2 \times 5 \text{ k}\Omega = 45 \text{ k}\Omega$

$4 \text{ k}\Omega$ parallel with $45 \text{ k}\Omega$ and is equal to $3.6 \text{ k}\Omega$.

$$V = \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 3.6 \text{ k}\Omega} \right) 5 \text{ V} = 1.08 \text{ V}$$

22. A dual slope integrating type DVM is used to measure a voltage signal $V(t) = (100 + 100 \sin 100\pi t) \text{ V}$, in its $(0-200) \text{ V}$ range of operation and it has $3\frac{1}{2}$ - digit display. The accuracy specification of this DVM is 0.5% of reading + 1 digit. What is the reading of this DVM and percentage error in reading?

- (A) 100 V , 0.6% (B) 100 V , 1.5% (C) 70.7 V , 1.5% (D) 200 V , 0.6%

Ans: (A)

Sol: DVM measures average value of input voltage signal.

$$\therefore \text{DVM reading} = 100 \text{ V}$$

$$1 \text{ digit} = 1 \text{ count}$$

$$= 1 \text{ step}$$



= r (resolution)

Resolution of DVM in 200V range is $\frac{200}{2 \times 10^3}$

$$= 0.1 \text{ V}$$

$$\text{Error} = \frac{0.5}{100} \times 100 + 0.1$$

$$= 0.6 \text{ V}$$

$$\% \text{ error in reading of } 100\text{V} = \frac{0.6}{100} \times 100\%$$

$$= 0.6\%$$

DISTRACTOR LOGIC

Option: (B) DVM measures average value of input voltage signal.

$$\therefore \text{DVM reading} = 100 \text{ V}$$

$$1 \text{ digit} = 1 \text{ count}$$

$$= 1\% \text{ of error}$$

$$\% \text{error} = \frac{0.5}{100} \times 100 + 1 = 1.5\%$$

Option: (C) DVM measures RMS value of input voltage signal.

$$\therefore \text{DVM reading} = 70.7 \text{ V}$$

$$1 \text{ digit} = 1 \text{ count}$$

$$= 1\% \text{ of error}$$

$$\% \text{error} = \frac{0.5}{100} \times 100 + 1 = 1.5\%$$

Option: (D) DVM reading = $V_{dc} + V_{m(ac)}$

$$= 100 + 100$$

$$= 200\text{V}$$

$$1 \text{ digit} = 1 \text{ count} = 1 \text{ step}$$

$$= r \text{ (resolution)}$$

Resolution of DVM in 200V range

$$= \frac{200}{2 \times 10^3}$$

$$= 0.1 \text{ V}$$



$$\begin{aligned} \text{Error} &= \frac{0.5}{100} \times 100 + 0.1 \\ &= 0.6 \text{ V} \end{aligned}$$

$$\begin{aligned} \% \text{ error in reading of } 100\text{V} &= \frac{0.6}{100} \times 100\% \\ &= 0.6\% \end{aligned}$$

23. The electric field intensity is given inside a sphere of radius $R \leq b$ m as $\vec{E} = 4R^2 \hat{r}$ (N/C). If the sphere has permittivity ' ϵ ', then the total electric displacement leaving the sphere $R = \frac{b}{2}$ m will be
- (A) $4\pi\epsilon b^4$ Coulomb (B) $\pi\epsilon b^4$ Coulomb
(C) πb^4 Coulomb (D) $\frac{\pi b^4}{4}$ Coulomb

Ans: (B)

Sol: Given: $\vec{E} = 4R^2 \hat{r}$ (N/C); $R \leq b$

$$\begin{aligned} \vec{D} &= \epsilon \vec{E} \\ &= 4 \epsilon R^2 \hat{r} \text{ C/m}^2 \end{aligned}$$

From Gauss's Law

$$\Psi_{\text{net}} \equiv Q_{\text{enc}} = \oint_s \vec{D} \cdot d\vec{S}$$

(or)

$$\begin{aligned} \Psi_{\text{net}} &= D_r \times \text{Area} \\ &= 4\epsilon R^2 \times 4\pi R^2 \\ &= 16\pi\epsilon R^4 \end{aligned}$$

The net electric flux leaving the sphere of radius $R = \frac{b}{2}$ is given by

$$\begin{aligned} \Psi_{\text{net}} &= 16\pi\epsilon \left(\frac{b}{2}\right)^4 \\ \therefore \Psi_{\text{net}} &= \pi\epsilon b^4 \text{ C} \end{aligned}$$



DISTRACTOR LOGIC

Option A: Simplification mistake

$$\begin{aligned}\psi_{\text{net}} &= 16\pi\epsilon\left(\frac{b}{2}\right)^4 \\ &= 16\pi\epsilon \times \frac{b^4}{4} = 4\pi\epsilon b^4\end{aligned}$$

Which is wrong answer

Option C: If we take directly \vec{E} , while applying

Gauss's law, then $\psi_{\text{net}} = 4R^2 \times 4\pi R^2$

$$= 16\pi\left(\frac{b}{2}\right)^4 = \pi b^4$$

Which is wrong answer

Option D: $\psi_{\text{net}} = D_r \times \text{Area}$

If we take area = πR^2 then which results $\psi_{\text{net}} = \frac{\pi b^4}{4}$, which is wrong answer.

24. The general solution of $\frac{dy^4}{dx^4} - 6\frac{dy^3}{dx^3} + 12\frac{dy^2}{dx^2} - 8\frac{dy}{dx} = 0$ is

- (A) $y = C_1 + (C_2 + C_3 x + C_4 x^2) e^{2x}$ (B) $y = (C_1 + C_2 x + C_3 x^2) e^{2x}$
 (C) $y = (C_1 + C_2 x + C_3 x^2 + C_4 x^3) e^{2x}$ (D) $y = C_1 + C_2 x + C_3 x^2 + C_4 e^{2x}$

Ans: (A)

Sol: The given equation is $(D^4 - 6D^3 + 12D^2 - 8D) y = 0$

$$D(D^3 - 6D^2 + 12D - 8) y = 0$$

$$D(D - 2)^3 = 0$$

$$\therefore D = 0, 2, 2, 2$$

\therefore The required solution is (A)

25. The Decimal equivalent of 2's complement representation of 8 bit integer is most positive when except _____

- (A) MSB are zeros (B) LSB are zeros
 (C) MSB are ones (D) LSB are ones



Ans: (C)

Sol: If MSB of 2's complement representation of integer is zero then it represents the positive number.

So option (C) is correct.

DISTRACTOR LOGIC

Option (A): If 'Except' is ignored in the given question, then option (A) is correct option.

Option (B): If LSB is considered as sign bit and 'Except' is ignored in the given question, then option (B) is correct option.

Option (D): If LSB is considered as sign, then option (D) is correct option.

26. $L^{-1}\left\{\frac{e^{-1/s}}{s^{1/2}}\right\} = \frac{\cos 2\sqrt{t}}{\sqrt{t}}$ then $L^{-1}\left\{\frac{e^{-a/s}}{s^{1/2}}\right\} = ?$

(A) $\frac{\cos 2\sqrt{at}}{\sqrt{at}}$

(B) $\frac{\cos 2\sqrt{t}}{\sqrt{at}}$

(C) $\frac{\cos 2\sqrt{at}}{\sqrt{t}}$

(D) $\frac{\cos \sqrt{at}}{\sqrt{t}}$

Ans: (C)

Sol: By using change of scale properly

$$L^{-1}\left\{f\left(\frac{s}{a}\right)\right\} = a F(at)$$

$$L^{-1}\left\{\frac{e^{-\frac{1}{(s/a)}}}{\left(\frac{s}{a}\right)^{\frac{1}{2}}}\right\} = \frac{a \cos 2\sqrt{at}}{\sqrt{at}}$$

$$\Rightarrow L^{-1}\left\{\frac{e^{-a/s}}{s^{1/2}}\right\} = \frac{\cos 2\sqrt{at}}{\sqrt{t}}$$

27. A 220V, 3- ϕ system supplies 363W to a wye connected balanced load at 0.8 pf lagging. The value of phase current is

(A) $1.2\angle -36.87^\circ$

(B) $1.2\angle 36.87^\circ$


(C) $2\angle -36.87^\circ$

(D) $2\angle +36.87^\circ$



Ans: (A)

Sol:

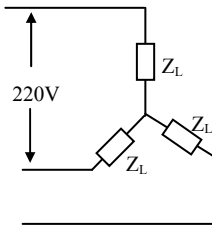

$$\text{Phase voltage} = \frac{220}{\sqrt{3}}$$

Total real power supplied by source

$$P = 3V_{ph}I_{ph}\cos\phi$$

$$I_{ph} = \frac{P}{3V_{ph}\cos\phi} = \frac{363}{3\left[\frac{220}{\sqrt{3}}\right][0.8]} = 1.2 \text{ A}$$

$$\therefore \phi = \cos^{-1}[0.8] = 36.87^\circ$$

$$\text{Lagging so, } I_{ph} = 1.2 \angle -36.87^\circ \text{ A}$$

(option A is correct)

DISTRACTOR LOGIC

Option: B Phase voltage = $\frac{220}{\sqrt{3}}$

Total real power supplied by source

$$P = 3V_{ph}I_{ph}\cos\phi$$

$$I_{ph} = \frac{P}{3V_{ph}\cos\phi} = \frac{363}{3\left[\frac{220}{\sqrt{3}}\right][0.8]} = 1.2 \text{ A}$$

$$\therefore \phi = \cos^{-1}[0.8] = 36.87^\circ$$

$$\text{Lagging so, } I_{ph} = 1.2 \angle 36.87^\circ \text{ A}$$

Option: C Phase voltage = 220 V

Total real power supplied by source

$$P = 3V_{ph}I_{ph}\cos\phi$$

$$I_{ph} = \frac{P}{3V_{ph}\cos\phi} = \frac{363}{220 \times 0.8} = 2 \text{ A}$$

$$\therefore \phi = \cos^{-1}[0.8] = 36.87^\circ$$

$$\text{Lagging so, } I_{ph} = 2 \angle -36.87^\circ \text{ A}$$



Option: D Phase voltage = 220 V

Total real power supplied by source

$$P = 3V_{ph}I_{ph}\cos\phi$$

$$I_{ph} = \frac{P}{3V_{ph}\cos\phi} = \frac{363}{220 \times 0.8} = 2 \text{ A}$$

$$\therefore \phi = \cos^{-1}[0.8] = 36.87^\circ$$

Lagging so, $I_{ph} = 2 \angle 36.87^\circ \text{ A}$

28. A synchronous motor is operating on bus bar at no-load condition with normal excitation. If the load on the motor is increased by keeping the field excitation same, for this
- (A) the motor operates at lagging pf, absorbs reactive power
 - (B) the motor operates at leading pf, absorbs reactive power
 - (C) the motor operates at lagging pf, delivers reactive power
 - (D) the motor operates at leading pf, delivers reactive power

Ans: (A)


Sol: At normal excitation, no load condition $\delta = 0, E = V$

As load increases 'δ' increases then

$$E\cos\delta < V \Rightarrow \text{under excitation}$$

\therefore lagging pf, absorbs reactive power.

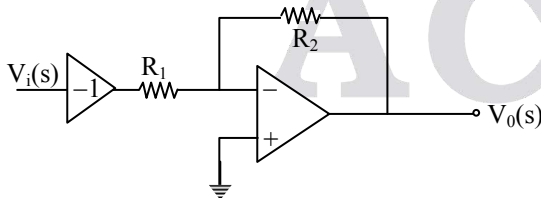29. The controller shows in figure below is



(A) proportional controller

(B) PI controller

(C) PD controller

(D) PID controller

Ans: (A)

Sol: $\frac{V_0(s)}{V_i(s)} = \text{TF} = G(s) = (-1) \frac{R_2}{R_1}$; $\frac{R_2}{R_1} = \text{constant}$

\therefore It is a proportional controller



30. For a lossless transmission line 50% series compensation and 50% shunt compensation is provided. Then surge impedance loading (SIL) and maximum power transfer capacity (P_{\max}) will be
- (A) SIL reduced by 1.732 times, P_{\max} increased by two times
 (B) SIL remains same, P_{\max} increased by two times
 (C) SIL increased by 1.732 times, P_{\max} remains same
 (D) Both SIL and P_{\max} remain same

Ans: (B)

Sol: $SIL = \frac{V^2}{Z_{C_0}}$ Z_{C_0} is surge impedance with compensation

$Z_{C_0} = Z_C \sqrt{\frac{1-K_{se}}{1-K_{sh}}}$ where Z_C is surge impedance of uncompensated line K_{se} & K_{sh} are degree of series and shunt compensations

From data $K_{se} = 0.5$, $K_{sh} = 0.5$

So, $Z_{C_0} = Z_C$ and no change in SIL

$$P_{\max} = \frac{|V_s| |V_r|}{|B|} = \frac{|V_s| |V_r|}{Z_c \sin \beta \ell} = \frac{|V_s| |V_r|}{Z_c \beta \ell} = \frac{|V_s| |V_r|}{X_{line}}$$

With 50% series compensation,

$$P_{\max \text{ new}} = \frac{|V_s| |V_r|}{X_{line} - 0.5X_{line}} = 2 \cdot \frac{|V_s| |V_r|}{X_{line}}$$

P_{\max} increased by 2 times

DISTRACTOR LOGIC

Option A: $SIL = \frac{V^2}{Z_{C_0}}$, Z_{C_0} ; is surge impedance with compensation

$Z_{C_0} = z_c \sqrt{\frac{1-K_{se}}{1+K_{sh}}}$; where Z_c is surge impedance, and series and shunt compensations from data

$K_{se} = 0.5$; $K_{sh} = 0.5$



$$\begin{aligned} Z_{C_0} &= z_c \sqrt{\frac{1-0.5}{1+0.5}} \\ &= z_c \sqrt{\frac{0.5}{1.5}} \\ &= \frac{1}{\sqrt{3}} \times Z_C \end{aligned}$$

Reduced by 1.732 times

$$P_{\max} = \frac{|V_s \parallel V_r|}{|B|} = \frac{|V_s| |V_r|}{Z_C \sin \beta \ell} = \frac{|V_s| |V_r|}{Z_C \beta \ell} = \frac{|V_s| |V_r|}{X_{\text{line}}}$$

With 50% series compensation, $P_{\max, \text{new}}$

$$\begin{aligned} &= \frac{|V_s \parallel V_r|}{X_{\text{line}} - 0.5X_{\text{line}}} \\ &= 2 \frac{|V_s \parallel V_r|}{X_{\text{line}}} \end{aligned}$$

P_{\max} increased by 2 times

Option C: $SIL = \frac{V^2}{Z_{C_0}}$, Z_{C_0} is surge impedance with compensations

$$Z_{C_0} = z_c \sqrt{\frac{1+K_{sh}}{1-K_{se}}}; \text{ Where } Z_C \text{ is surge impedance, and series and shunt compensation}$$

from data $K_{se} = 0.5$; $K_{sh} = 0.5$ Since 1995

$$\begin{aligned} Z_{C_0} &= z_c \sqrt{\frac{1+0.5}{1-0.5}} \\ &= Z_C \sqrt{3} \end{aligned}$$

Increased by 1.732 times

$$\begin{aligned} P_{\max} &= \frac{|V_s \parallel V_r|}{|B|} = \frac{|V_s \parallel V_r|}{Z_C \sin \beta \ell} \\ &= \frac{|V_s \parallel V_r|}{Z_C \beta \ell} \\ &= \frac{|V_s \parallel V_r|}{X_{\text{line}} - K_{se} X_{\text{line}} + K_{sh} X_{\text{line}}} \\ &= \frac{|V_s \parallel V_r|}{X_{\text{line}} - 0.5X_{\text{line}} + 0.5X_{\text{line}}} \end{aligned}$$



$$= \frac{|V_s \parallel V_r|}{X_{line}}$$

P_{max} remains same

Option D: $SIL = \frac{V^2}{Z_{C_0}}$, Z_{C_0} is surge impedance with compensation $Z_{C_0} = Z_C \sqrt{\frac{1 - K_{se}}{1 - K_{sh}}}$; where Z_C is surge

impedance of uncompensated line, and K_{se} & K_{sh} are degree of series and shunt compensation from data $K_{se} = 0.5$; $K_{sh} = 0.5$

$$Z_C \sqrt{\frac{1 - 0.5}{1 - 0.5}} = Z_C \sqrt{1} = Z_C$$

So, $Z_{C_0} = Z_C$ no change in SIL

$$\begin{aligned} P_{max} &= \frac{|V_s \parallel V_r|}{|B|} = \frac{|V_s \parallel V_r|}{Z_C \sin \beta \ell} \\ &= \frac{|V_s \parallel V_r|}{Z_C \beta \ell} \\ &= \frac{|V_s \parallel V_r|}{X_{line} - K_{se} X_{line} + K_{sh} X_{line}} \\ &= \frac{|V_s \parallel V_r|}{X_{line} - 0.5 X_{line} + 0.5 X_{line}} \\ &= \frac{|V_s \parallel V_r|}{X_{line}} \end{aligned}$$

P_{max} remains same

31. In a uniform region of free space, if the electric field intensity is given by $\vec{E} = \hat{x}4x + \hat{y}3y$ Volt/m, then the potential at X(0, 2, 2)m with respect to Y(2, 2, 2)m is
- (A) 8V (B) -8V (C) -16V (D) 16V

Ans: (A)

Sol: Potential at X w.r.t Y is given by

$$\begin{aligned} V_{XY} &= - \int_{Y(2,2,2)}^{X(0,2,2)} \vec{E} \cdot d\vec{\ell} \\ &= - \left[\int_2^0 4x dx + \int_2^2 3y dy \right] \end{aligned}$$



$$\therefore V_{XY} = - \left. 4 \frac{x^2}{2} \right|_2^0 = 8 \text{ V}$$

DISTRACTOR LOGIC


Option B: If we take $V_{xy} = - \int_X^Y \vec{E} \cdot d\vec{\ell}$

Then $V_{XY} = - 8 \text{ V}$ which is wrong answer .

Option C: $V_{XY} = - \left[\int_0^2 4x dx + \int_2^2 3y dy \right]$
 $= -4x^2 \Big|_0^2 = - 16\text{V}$, which is incorrect answer .

Option D: $V_{XY} = - \left[\int_2^0 4x dx + \int_2^2 3y dy \right]$
 $= -4x^2 \Big|_2^0 = 16\text{V}$, it is a simplification mistake in integration .

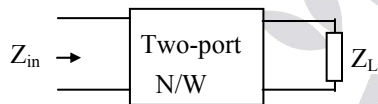32. A two port network having Z-parameters as $[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$ is terminated to a load impedance Z_L as shown. The input impedance Z_{in} of two port network is given by



(A) $Z_{11} - \frac{Z_{12}Z_{21}}{Z_{22} + Z_L}$

(B) $Z_{11} - \frac{Z_{12}(Z_{21} + Z_L)}{Z_{22}}$

(C) $Z_{11} + Z_L$

(D) $Z_{22} + Z_L$

Ans: (A)

Sol: Input impedance, $Z_{in} = \frac{V_1}{I_1}$


Z -parameter equations

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

But, $V_2 = -I_2Z_L$

So,

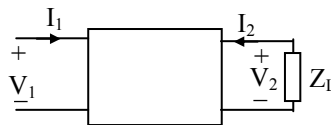



$$-I_2 Z_L = Z_{21} I_1 + Z_{22} I_2$$

$$-I_2 (Z_L + Z_{22}) = Z_{21} I_1$$

$$I_2 = -\frac{Z_{21}}{Z_L + Z_{22}} I_1$$

$$\text{So, } V_1 = Z_{11} I_1 - \frac{Z_{21} Z_{12}}{Z_L + Z_{22}} I_1$$

$$\text{So, } Z_{in} = \frac{V_1}{I_1} = \left[Z_{11} - \frac{Z_{21} Z_{12}}{Z_L + Z_{22}} \right]$$

DISTRACTOR LOGIC

Option: B Input impedance, $Z_{in} = \frac{V_1}{I_1}$

Z-parameter equations

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\text{But, } V_2 = -I_2 Z_L$$

So,


$$-I_2 Z_L = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 (Z_{21} + Z_L) = Z_{22} I_2$$

$$I_2 = \frac{Z_{21} + Z_L}{Z_{22}} I_1$$

$$\text{So, } V_1 = Z_{11} I_1 - \frac{Z_{12} \times (Z_{21} + Z_L)}{Z_{22}} I_1$$
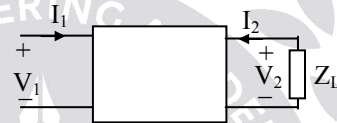
$$\text{So, } Z_{in} = \frac{V_1}{I_1} = \left[Z_{11} - \frac{Z_{12} \times (Z_{21} + Z_L)}{Z_{22}} \right]$$



Option: C If two networks are in cascade than

$$Z_{eq} = [Z_A] + [Z_B]$$

$$= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} + \begin{bmatrix} Z_L & Z_L \\ Z_L & Z_L \end{bmatrix} = \begin{bmatrix} Z_{11} + Z_L & Z_{12} + Z_L \\ Z_{21} + Z_L & Z_{22} + Z_L \end{bmatrix}$$



The input impedance is given by


$$\frac{V_1}{I_1} = Z_{11} + Z_L$$



Option: D If two networks are in cascade than

$$Z_{eq} = [Z_A] + [Z_B]$$
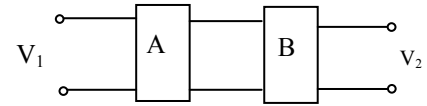
$$= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} + \begin{bmatrix} Z_L & Z_L \\ Z_L & Z_L \end{bmatrix} = \begin{bmatrix} Z_{11} + Z_L & Z_{12} + Z_L \\ Z_{21} + Z_L & Z_{22} + Z_L \end{bmatrix}$$



The input impedance of output port is given by

$$\frac{V_2}{I_2} = Z_{22} + Z_L$$

33. A 4 pole series motor has 944 wave connected armature conductors. At a certain load the flux/pole is 34.6 mWb and the total mechanical torque developed is 209 N-m. With an applied voltage of 500V, the speed of the motor will be (The total motor resistance is 1Ω.)

- (A) 422 rpm (B) 440 rpm (C) 477 rpm (D) 496 rpm

Ans: (B)

Sol: $T = \frac{1}{2\pi} \times \frac{\phi Z I_a P}{A}$

$$\Rightarrow 209 = \frac{1}{2\pi} \times \frac{34.6 \times 10^{-3} \times 944 \times I_a \times 4}{2}$$

$$I_a = 20.10 \text{ A}$$

$$E_b = V - I_a R_a = 500 - 20.10 \times 1 = 479.89 \text{ A}$$

$$E_b = \frac{\phi Z N P}{60 A} \Rightarrow 479.89$$

$$= \frac{34.6 \times 10^{-3} \times 944 \times N \times 4}{60 \times 2}$$

$$\Rightarrow N = 440.77 \text{ rpm}$$

DISTRACTOR LOGIC

Distractor logic:

Option: A $T = \frac{1}{2\pi} \times \frac{\phi Z I_a P}{A}$

$$\Rightarrow 209 = \frac{1}{2\pi} \times \frac{34.6 \times 10^{-3} \times 944 \times I_a \times 4}{4}$$

$$I_a = 40.20 \text{ A}$$



$$E_b = V + I_a R_a = 500 - 40.20 \times 1 = 459.8 \text{ A}$$

$$E_b = \frac{\phi Z N P}{60 A} = 459.8$$

$$459.8 = \frac{34.6 \times 10^{-3} \times 944 \times N \times 4}{60 \times 2}$$

$$\Rightarrow N = 422.32 \text{ rpm}$$

Option: C $T = \frac{1}{2\pi} \times \frac{\phi Z I_a P}{A}$

$$\Rightarrow 209 = \frac{1}{2\pi} \times \frac{34.6 \times 10^{-3} \times 944 \times I_a \times 4}{2}$$

$$I_a = 20.10 \text{ A}$$

$$E_b = V + I_a R_a = 500 + 20.10 \times 1 = 520.1 \text{ A}$$

$$E_b = \frac{\phi Z N P}{60 A} = 520$$

$$520 = \frac{34.6 \times 10^{-3} \times 944 \times N \times 4}{60 \times 2}$$

$$\Rightarrow N = 477.61 \text{ rpm}$$

Option: D $T = \frac{1}{2\pi} \times \frac{\phi Z I_a P}{A}$

$$\Rightarrow 209 = \frac{1}{2\pi} \times \frac{34.6 \times 10^{-3} \times 944 \times I_a \times 4}{4}$$

$$I_a = 40.20 \text{ A}$$

$$E_b = V + I_a R_a = 500 + 40.20 \times 1 = 540.2 \text{ A}$$

$$E_b = \frac{\phi Z N P}{60 A} = 540.2$$

$$540.2 = \frac{34.6 \times 10^{-3} \times 944 \times N \times 4}{60 \times 2}$$

$$\Rightarrow N = 496.16 \text{ rpm}$$



34. The below program is executed by 8085 microprocessor

```
XRA A
MOV L, A
MOV H, L
DCX H
DAD H
MOV M, A
INR M
MOV A, M
```

After execution, what will be the contents of PSW

- (A) FFFE H (B) 0101 H (C) 01FF H (D) FE01 H

Ans: (B)

Sol: (A) = 00H [∵ (A) ∨ (A) = 00H]

→ cy = 0, P = 1, AC = 0, Z = 1, S = 0

(L) ← (A) = 00H

(H) ← (L) = 00H

DCX H ⇒ 0000H - 1 = FFFFH

FFFF = 1111 1111 1111 1111

FFFF = 1111 1111 1111 1111

1111 1111 1111 1110 → FFFE H

(HL) = FFFE H with cy = 1

Other flags are remains same.

(FFFE H) ← (A) = 00H

00H + 1 = 01H

= (FFFE H)

Cy flag not affected for INR ⇒ cy remains 1

Remaining 4 flags are affected based on result

01H = 0000 0001 ⇒ P = 0, AC = 0, Z = 0, S = 0

(A) ← (FFFE H) = 01H

(A) = 01H, (flag reg) = 00 × 0 × 0 × 1


= 0000 0001

= 01H

(PSW) = 0101H



35. The output Z is

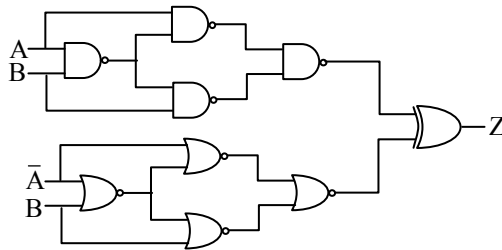

(A) $A \oplus B$


(B) $A \odot B$

(C) 1

(D) 0

Ans: (D)

Sol:

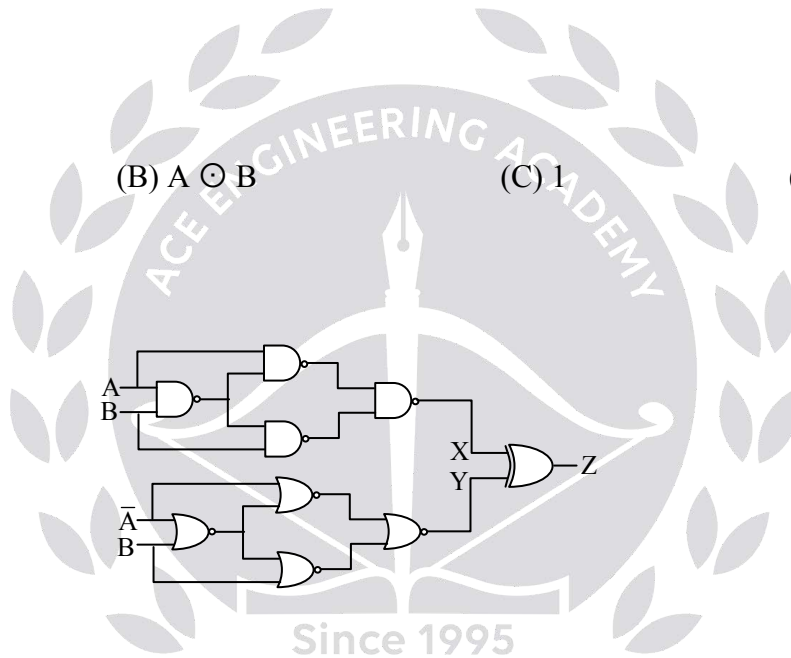

$$X = A \oplus B$$

$$Y = A \oplus B$$

$$Z = A \oplus B \oplus A \oplus B$$

$$= A \oplus A \oplus B \oplus B$$

$$= 0 \oplus 0$$

$$Z = 0$$



DISTRACTOR LOGIC

Option (C): If \bar{A} is taken as A

$$X = A \oplus B$$

$$Y = A \odot B$$

$$Z = A \oplus B \oplus A \odot B$$

$$= A \oplus A \oplus B \odot B$$

$$= 0 \oplus 1$$

$$Z = 1$$

Option (A): If XOR gate is taken OR-gate

$$Z = [A \oplus B] + [A \oplus B]$$

$$= A \oplus B$$

Option (B): If $X = A \odot B$

$$Y = A \odot B$$

And output gate considers as OR gate then

$$Z = A \odot B \oplus A \odot B$$

$$= A \odot B$$

OUR ESE 2016 TOP 10 RANKERS IN ALL STREAMS

E&T

1 E&T Haseen Bhushan	2 E&T Amir Rowat
3 E&T Aswathy	4 E&T T.Naveen
5 E&T Vishal Ranjan	6 E&T Harshit Jain
7 E&T Aash Chikara	8 E&T Vivek Jain
9 E&T J.Narayanan	10 E&T Prabhat Singh

10 IN TOP 10 RANKS

EE

2 EE B.Venkatesh	3 EE Sanj Kumar Sharma
4 EE Yasho Shakti	5 EE Ashish Yarnu
6 EE Muhammad Khan	8 EE Sri Sushil Kumar Bhatnagar
9 EE Anand Bhatnagar	10 EE Gourav Tyagi

8 IN TOP 10 RANKS

CE

2 CE Bhavik Joshi	4 CE Adish-Rishi Srivastava
6 CE Nikhil Garg	8 CE Anand Anand
9 CE Ajayesh Kumar	10 CE Manish Kumar

6 IN TOP 10 RANKS

ME

1 ME Wahid Idid Ahmad	2 ME Gourav Alam
3 ME Ching Shrivastava	8 ME JGAY Prasad
9 ME Gourav Kanti	


5 IN TOP 10 RANKS

72% OF STUDENTS IN TOP 10 ARE FROM **ACE** and many more...



Q.36 – Q.65 carry two marks each

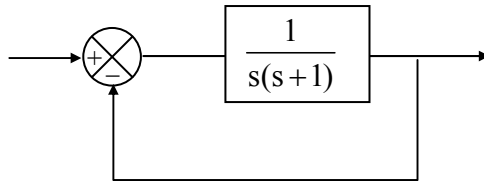36. Consider the system shown in figure below



The approximate 2% settling time of the response to a unit step input is _____ seconds.

Ans: 8 (Range 7.9 to 8.3)

Sol: $CE = 1 + \frac{1}{s(s+1)} = 0$


$$s^2 + s + 1 = 0$$

$$\omega_n = 1 \text{ and } 2\zeta\omega_n = 1$$

$$\Rightarrow \zeta\omega_n = 0.5$$

$$t_s = \frac{4}{\zeta\omega_n} = 8 \text{ sec for 2\% criterion}$$

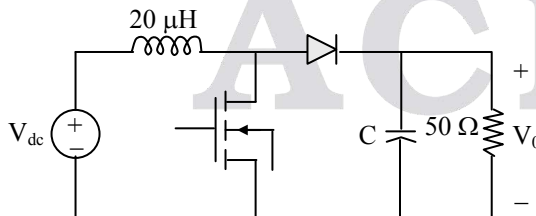
37. Input voltage to the following DC-DC converter is 20 V and output voltage is 50 V. Duty cycle ratio is 0.5. RMS value of diode current (in ampere) is ____.





Ans: 2 (Range 2 to 2)

Sol:

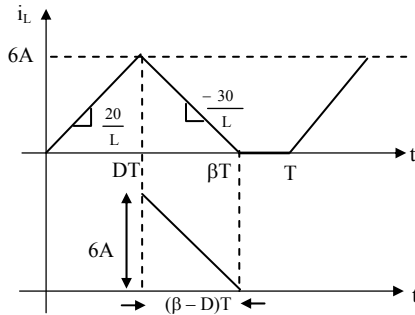

In continuous conduction mode, $V_0 = \frac{V_{dc}}{1-D} = \frac{20}{1-0.5} = 40V$

But given $V_0 > 40 V$, so it is discontinuous mode of operation.

Power balance equation $P_0 = P_{in}$

$$\Rightarrow V_{dc} \cdot I_s = 50 \times \left(\frac{50}{50}\right)$$

$$I_s = \frac{50}{20} = 2.5 A$$

$$\frac{V_0}{V_{dc}} = \frac{\beta}{\beta - D} = \frac{50}{20} = 2.5$$

$$\Rightarrow \beta = 2.5 \times \beta - (2.5 \times 0.5)$$

$$\beta = 0.833$$

$$I_L = \frac{1}{2} \times I_{LMax} \times \beta T = 2.5$$

$$I_{LMax} = 6 A$$


$$I_{D,rms} = \left[\frac{6^2}{3} \times \left(\frac{5}{6} - \frac{1}{2} \right) \times \frac{T}{T} \right]^{\frac{1}{2}}$$

$$= \left[\frac{6^2}{3} \times \frac{2}{6} \right]^{\frac{1}{2}}$$

$$I_{D,rms} = 2 A$$



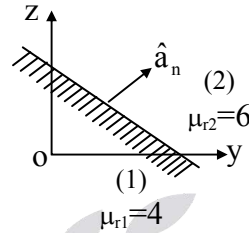38. Region 1, where $\mu_{r1} = 4$, is the side of the plane $y + z = 1$ containing the origin (shown in figure). In region 2, $\mu_{r2} = 6$. If the magnetic flux density in region 1 is $\vec{B}_1 = 2\hat{a}_x + \hat{a}_y$ (Tesla), then the magnitude of magnetic flux density (in T) in region 2 is _____.



Ans: 3.2 (Range: 3 to 3.5)

Sol: The unit vector normal to the plane $y + z = 1$ is given by

$$\hat{a}_n = \frac{\hat{a}_y + \hat{a}_z}{\sqrt{2}}$$

$$B_{n1} = \vec{B}_1 \cdot \hat{a}_n = (2\hat{a}_x + \hat{a}_y) \cdot \left(\frac{\hat{a}_y + \hat{a}_z}{\sqrt{2}} \right)$$

$$B_{n1} = \frac{1}{\sqrt{2}}$$

$$\vec{B}_{n1} = B_{n1} \hat{a}_n = \frac{1}{\sqrt{2}} \left(\frac{\hat{a}_y + \hat{a}_z}{\sqrt{2}} \right)$$

$$\vec{B}_{n1} = 0.5\hat{a}_y + 0.5\hat{a}_z$$

$$\vec{B}_{n2} = \vec{B}_{n1} = 0.5\hat{a}_y + 0.5\hat{a}_z$$

$$\vec{B}_{t1} = \vec{B}_1 - \vec{B}_{n1}$$

$$= (2\hat{a}_x + \hat{a}_y) - (0.5\hat{a}_y + 0.5\hat{a}_z)$$

$$\vec{B}_{t1} = 2\hat{a}_x + 0.5\hat{a}_y - 0.5\hat{a}_z$$

$$\frac{B_{t1}}{\mu_1} = \frac{B_{t2}}{\mu_2} \Rightarrow \vec{B}_{t2} = \left(\frac{\mu_2}{\mu_1} \right) \vec{B}_{t1} = \left(\frac{3}{2} \right) [2\hat{a}_x + 0.5\hat{a}_y - 0.5\hat{a}_z]$$


$$\vec{B}_{t2} = 3\hat{a}_x + 0.75\hat{a}_y - 0.75\hat{a}_z$$

$$\vec{B}_2 = 3\hat{a}_x + 1.25\hat{a}_y - 0.25\hat{a}_z \quad [\because \vec{B}_2 = \vec{B}_{t2} + \vec{B}_{n2}]$$

$$\therefore |\vec{B}_2| = \sqrt{(3)^2 + (1.25)^2 + (-0.25)^2} = 3.259 \text{ Tesla}$$



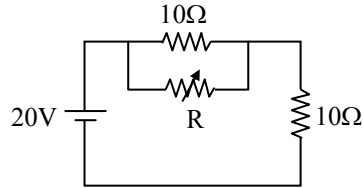39. The maximum power transferred to R is _____ (in watts).




Ans: 5

Sol: $R_{th} = 10 || 10 = 5\Omega$

$V_{th} = 10V$

$$P_{max} = \frac{V_s^2}{4.R_L} = \frac{10^2}{4 \times 5} = \frac{100}{20} = 5W$$

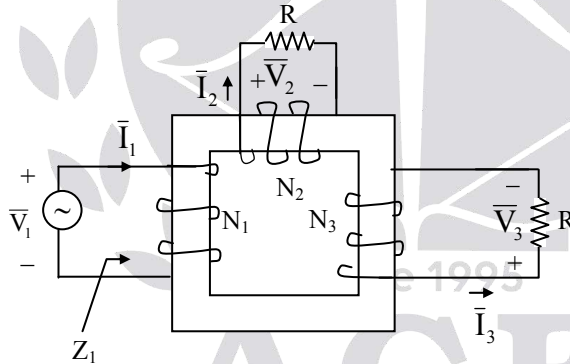40. The three-winding ideal transformer in the following figure has $N_1 = N_2 = 2N_3$ and identical load resistors (R) connected across coils 2 and 3. The input impedance Z_1 as indicated in the figure is _____ $\times R \Omega$.



Ans: 0.8 (Range 0.8 to 0.8)

Sol: MMF balance requires that

$$N_1 \bar{I}_1 = N_2 \bar{I}_2 + N_3 \bar{I}_3$$

$$N_1 \bar{I}_1 = N_1 \bar{I}_2 + \frac{1}{2} N_1 \bar{I}_3$$

Or

$$\bar{I}_1 = \bar{I}_2 + \frac{1}{2} \bar{I}_3 \dots \dots \dots (1)$$

Since the value of flux through all three coils is identical, $\bar{V}_1 = \bar{V}_2 = 2\bar{V}_3$.



By Ohm's law, $\bar{I}_2 = \frac{\bar{V}_2}{R} = \frac{\bar{V}_1}{R}$ (2)

$\bar{I}_3 = \frac{\bar{V}_3}{R} = \frac{\bar{V}_1}{2R}$ (3)


Use (2) and (3) in (1) to find

$\bar{I}_1 = \frac{\bar{V}_1}{R} + \frac{\bar{V}_1}{4R} = \frac{5\bar{V}_1}{4R}$

Hence,

$Z_1 = \frac{\bar{V}_1}{\bar{I}_1} = \frac{4}{5}R$

41. The current I (in Amp) is _____.

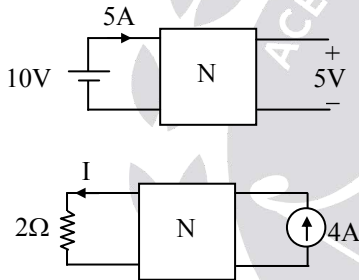

Ans: 1


Sol: $\frac{V_2^1}{V_1} = \frac{I_2^1}{I_1}$

$\frac{5}{10} = \frac{I_2^1}{4}$

$I_2^1 = \frac{20}{10} = 2A$

$R_{th} = \frac{10}{5} = 2\Omega$

$I = 1Amp$

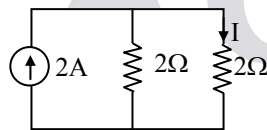



42. Synchronous generator is connected to an infinite bus by a transformer and lossless network. Infinite bus voltage is 1.0 pu and a voltage of generator is 1.2 pu. The transfer admittance is 2.0 pu. The power transfer by the generator is 1.0 pu. A 3-phase fault is taking place in the lossless network so that the power transfer is zero. The fault is cleared by circuit breaker and the original network is restored. The critical clearing angle made by the rotor at the time fault gets cleared by circuit breaker is _____ (in degrees)

Ans: 87.6 (Range: 86 to 88)

Sol: $P_s = P_e = 1.0$

$$P_{M_1} = \frac{EV}{X_{l_{eq}}} = (EV)y_{eq} = 2.0 (1.2 \times 1.0) = 2.4$$

$$\delta_0 = \sin^{-1} \left(\frac{P_s}{P_{M_1}} \right)$$

$$= \sin^{-1} \left(\frac{1.0}{2.4} \right) \text{ele. deg ree} = 24.62^\circ$$

$$\delta_{0(\text{rad})} = \delta_0 \times \frac{\pi}{180} = 0.429$$

Fault: $P_{e_2} = 0, P_{m_2} = 0$

$$\delta_m = 180^\circ - \sin^{-1} \left(\frac{P_s}{P_{m_3}} \right)$$

$$P_{m_3} = P_{m_1}$$

$$\delta_m = 180^\circ - \sin^{-1} \left(\frac{1.0}{2.4} \right) = 180^\circ - 24.62^\circ = 155.38^\circ$$

$$\delta_{m(\text{rad})} = \delta_m \times \frac{\pi}{180} = 2.711$$

$$\delta_c = \cos^{-1} \left[\frac{P_s (\delta_m - \delta_e) + P_{m_3} \cos \delta_m}{P_{m_3}} \right]$$

$$\delta_c = \cos^{-1} \left[\frac{1.0(\delta_m - \delta_0) + 2.4 \cos \delta_m}{2.4} \right] \text{ele. deg ree}$$

$$\delta_c = \cos^{-1} \left[\frac{1.0(2.711 - 0.429) + 2.4 \cos(155.38)}{2.4} \right] = 87.6^\circ$$



43. A 3-phase synchronous motor has a reactance of 0.8 pu with negligible resistance. When connected to busbar at rated voltage and the excitation adjusted to an emf of 1.2 pu, the machine draws rated input kVA. The mechanical power developed by the motor is _____ pu.

Ans: 0.992 (Range: 0.8 to 1)

Sol: $X_s = 0.8$ pu, $E = 1.2$ pu, $V = 1.0$ pu, $I_a = 1$ pu

$$|I_a Z_s| = \sqrt{E^2 + V^2 - 2VE \cos \delta}$$

$$\Rightarrow 1 \times 0.8 = \sqrt{1.2^2 + 1^2 - 2 \times 1 \times 1.2 \cos \delta}$$

$$\Rightarrow \delta = 41.4^\circ$$

$$P = \frac{EV}{X_s} \sin \delta \Rightarrow \frac{1.2 \times 1}{0.8} \sin 41.4^\circ$$

$$= 0.992 \text{ pu}$$

44. A 250 V shunt motor has an armature resistance of 0.5 Ω and field resistance of 250 Ω . When driving a load at 600 rpm, the torque of which is constant, the armature takes 20 A current. If it is desired to raise the speed from 600 to 800 rpm, then the resistance to be inserted in the shunt field circuit is _____ Ω .

Ans: 88.0 to 88.5 Ω

Sol: Torque constant $T_2 = T_1$

$$\phi_2 I_{a_2} = \phi_1 I_{a_1}$$

$$\Rightarrow I_{sh_2} I_{a_2} = I_{sh_1} I_{a_1}$$

$$I_{sh_1} = \frac{V}{R_{sh}} = \frac{250}{250} = 1 \text{ A}$$

$$I_{sh_2} I_{a_2} = 1 \times 20$$

$$I_{a_2} = \frac{20}{I_{sh_2}}$$

$$E_{b_1} = V - I_{a_1} R_a = 250 - 20 \times 0.5 = 240 \text{ A}$$

$$E_{b_2} = V - I_{a_2} R_a = 250 - \frac{20}{I_{sh_2}} \times 0.5 = 250 - \frac{10}{I_{sh_2}}$$



$$\frac{E_{b_2}}{E_{b_1}} = \frac{I_{sh_2} \times N_2}{I_{sh_1} \times N_1} \Rightarrow \frac{250 - \frac{10}{I_{sh_2}}}{240} = \frac{I_{sh_2} \times 800}{1 \times 600}$$

$$= 250 - \frac{10}{I_{sh_2}} = 320 I_{sh_2}$$

$$\Rightarrow 32 I_{sh_2}^2 - 25 I_{sh_2} + 1 = 0$$

$$I_{sh_2} = \frac{25 \pm \sqrt{25^2 - 4 \times 32 \times 1}}{2 \times 32}$$

$$I_{sh_2} = 0.739 \text{ A or } (0.0422 \text{ A is too low})$$

$$I_{sh_2} = 0.739 \text{ A} = \frac{V}{R_{sh_2}} = \frac{250}{R_{sh_2}}$$

$$R_{sh_2} = \frac{250}{0.739} = 338.29 \Omega$$

Resistance to be added

$$= 338.29 - 250 = 88.29 \Omega$$

45. In a power system network Thevenin's impedance and voltage with respect to a bus are given as 0.9 pu and $j0.2$ pu respectively. The load kept at that bus consumes constant complex power of $1 + j1$ pu. A shunt capacitor bank is connected at that bus to increase voltage magnitude to 1 pu. The power factor of load capacitor combination is _____ (lag)

Ans: 0.894 (Range: 0.85 to 0.92)


Sol: From given data $V_{th} = 0.9$ pu; $Z_{th} = j0.2$ pu. To increase voltage magnitude to 1 pu, a shunt capacitor bank was connected.

$$V_c = 1 \text{ pu}$$

$$V_c = V_{th} \frac{Z_c}{Z_c + Z_{th}}$$

$$1 = 0.9 \frac{Z_c}{j0.2 + Z_c}$$

$$\text{So, } Z_c = -j2 \text{ pu}$$

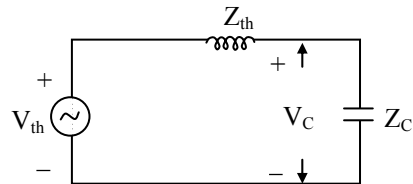

Load at that bus is $1 + j1$ pu




From this, $Q_{sh\ cap} = \frac{|V|^2}{X_c} = \frac{1}{2} = 0.5\ pu$

So, $P_s = P_{load} = 1\ pu$


$Q_s = Q_{load} - Q_{sh\ cap} = 0.5\ pu$

Overall power factor
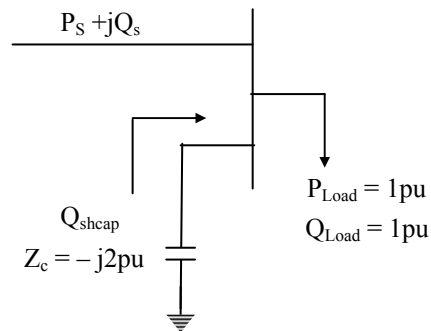
$$\begin{aligned} \cos\phi_s &= \frac{P_s}{\sqrt{P_s^2 + Q_s^2}} \\ &= \frac{1}{\sqrt{1 + (0.5)^2}} \text{ lag} \\ &= 0.894 \text{ lag} \end{aligned}$$




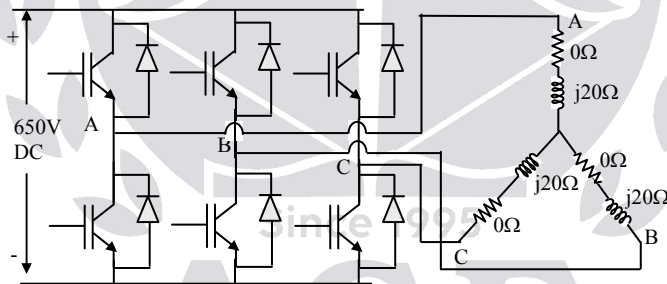46. A three phase voltage source inverter (VSI) as shown in figure is feeding a star connected inductive load of $(0 + j20)\ \Omega/\text{ph}$. If it is fed from a 650 V battery and operates with 180° conduction mode with fundamental frequency of output as 50 Hz, the peak value of per phase load current in ampere is _____.



Ans: 22.69 (Range 22.6 to 22.8)

Sol:

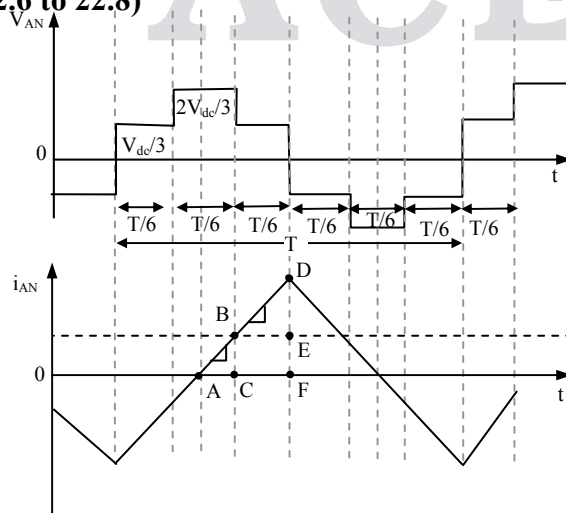



$$\Delta ABC, \frac{2V_{dc}}{3L} = \frac{BC}{AC} \Rightarrow BC = \frac{2V_{dc}}{3L} \times \frac{T}{12} = \frac{V_{dc}}{18Lf}$$

$$\text{Is } \Delta BDE, \frac{V_{dc}}{3L} = \frac{DE}{BE} \Rightarrow DE = \frac{V_{dc}}{3L} \times \frac{T}{6} = \frac{V_{dc}}{18Lf}$$

$$i_{0(\text{peak})} = BC + DE = \frac{V_{dc}}{18Lf} + \frac{V_{dc}}{18Lf}$$


$$= \frac{V_{dc}}{9Lf}$$

But $2\pi Lf = 20$

so $Lf = \left(\frac{20}{2\pi}\right)$

$$i_{0, \text{peak}} = \frac{650 \times 2\pi}{9 \times 20} = 22.69 \text{ A}$$

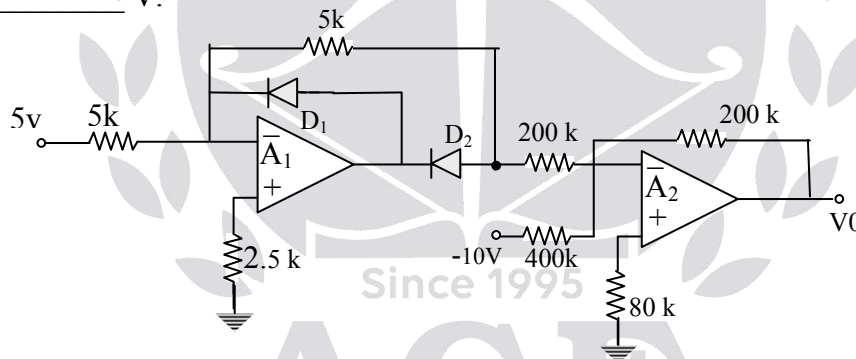47. The output voltage V_0 of op-amp circuit shown in figure assuming op-amp & diodes as ideal, is _____ V.




Ans: $V_0 = 10$ (Range: 10 to 10)

Sol: Step (1): For the given input of 5v, D1 is off & D2 is ON

$$V_0^1 = \frac{-5k}{5k} \times 5v = -5v$$

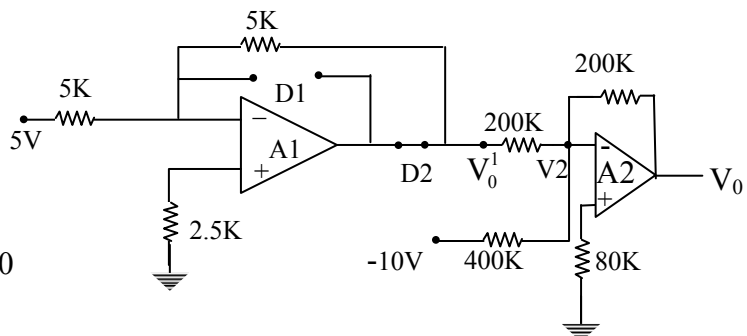Step (2): KCL at the inverting input, V_2 of op-amp2(A_2)



Op-amp 2 (A_2)

$$\frac{V_0^1}{200k} - \frac{10v}{400k} + \frac{V_0}{200k} = 0$$



$$V_0 = 200k \left[\frac{5V}{200k} + \frac{10V}{400k} \right] = 5V + 5V$$

$$\therefore V_0 = 10V$$

48. By changing the order of interaction $\int_1^4 \int_{\sqrt{y}}^2 (x^2 + y^2) dx dy$ becomes

(A) $\int_1^2 \int_1^{x^2} (x^2 + y^2) dy dx$

(B) $\int_1^4 \int_1^{x^2} (x^2 + y^2) dy dx$


(C) $\int_1^2 \int_{x^2}^1 (x^2 + y^2) dy dx$

(D) $\int_1^4 \int_{x^2}^1 (x^2 + y^2) dy dx$

Ans: (A)

Sol: In the given double integral the limits of $x : \sqrt{y} \rightarrow 2$ and $y : 1 \rightarrow 4$

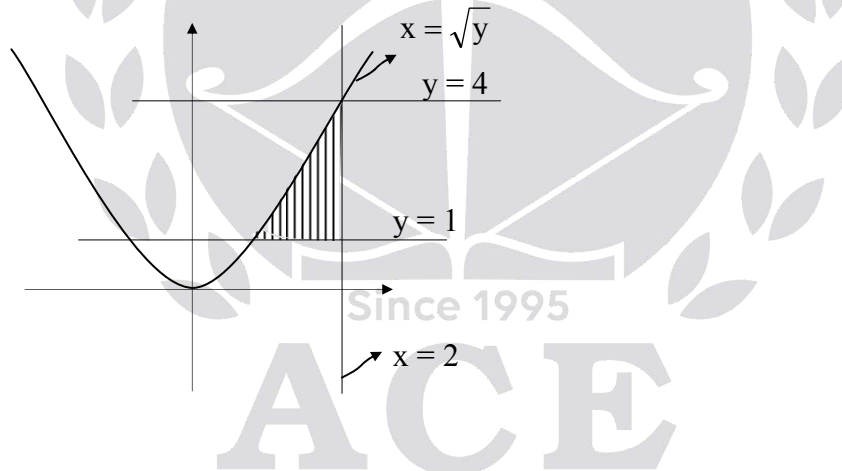
\therefore The required area is shaded below



$$\therefore \int_1^4 \int_{\sqrt{y}}^2 (x^2 + y^2) dx dy \text{ becomes } \int_1^2 \int_1^{x^2} (x^2 + y^2) dy dx$$



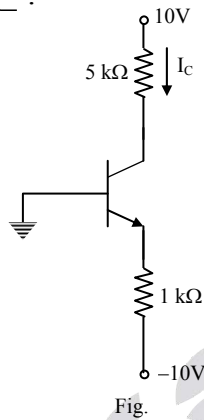49. In the circuit shown in figure , a silicon transistor with $V_{BE} = 0.7V$, $\beta = 100$ is used. The transistor is biased at _____ ?



- (A) 9.2 mA (B) 2.1 mA (C) 1.86 mA (D) 0

Ans: (B)

Sol: Step (1): KVL for BE loop of BJT

$$0 - 0.7V - I_E \cdot 1K + 10V = 0 \dots\dots (1)$$

$$\Rightarrow I_E = \frac{9.3V}{1K} = 9.3mA \dots\dots (2) \text{ [i.e } I_E \text{ is FB]}$$

$$\Rightarrow I_C = \left(\frac{\beta}{1+\beta} \right) I_E = 9.2mA \dots\dots (3)$$

Step (2): KVL for C-loop

$$10V - I_C \times 5K - V_C = 0 \dots\dots (4)$$

$$V_C = 10V - 9.2mA \times 5K = -36V \dots\dots (5)$$

$$\Rightarrow V_{CB} = V_C - V_B = -36V - 0 = -36V \dots\dots (6)$$

NOTE: $\because V_{CB}$ is $-V_e$, collector junctions is F.B



\therefore BJT is operated in saturation region

Step (3): \because BJT is in saturation, $V_{CE_{sat}} = 0.2V$

$$\Rightarrow V_C = V_{CE_{sat}} + V_E = -0.5V \dots\dots (1)$$

KVL for collector -loop:
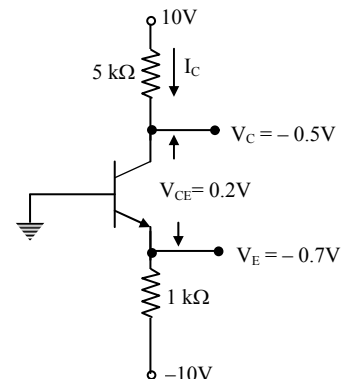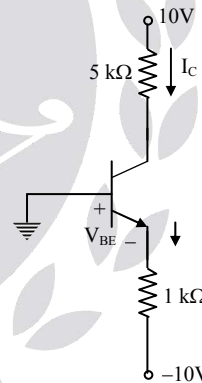
$$I_C = \frac{10V - (-0.5V)}{5K} = 2.1mA \dots\dots (2)$$





DISTRACTOR LOGIC

Option: A: If the device(BJT) is in forward active region, KVL for BE loop of BJT

$$0 - 0.7V - I_E 1K + 10V = 0$$

$$I_E = \frac{9.3V}{1K} = 9.3mA$$

$$\therefore I_c = \left(\frac{\beta}{1+\beta} \right) I_E = \frac{100}{101} \times 9.3mA$$

$$I_c = 9.2mA$$

Option: B: $I_c = 2.1mA$ (1) (\because Device is actually biased in saturation region)

Option:C: If the device is in inverse (or reverse) active region,

(i.e) E-B junction is R.B & C.B junction is F.B


Assuming $V_{CB} = 0.7V \Rightarrow V_c = 0.7V$ (1)

$$[\because V_{CB} = V_C - V_B = V_C]$$

KVL for collector loop of BJT

$$10V - I_c 5K - 0.7V = 0 \dots\dots (1)$$
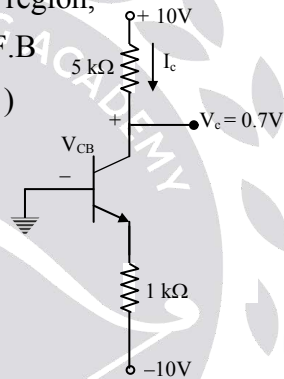
$$I_c = \frac{9.3V}{5K} = 1.86mA \dots\dots (2)$$



Option: D If the device is in cutoff region

$$I_B = 0 \Rightarrow I_C = 0 \dots\dots (1)$$

50. The incidence matrix of a graph is given below

$$A = \begin{bmatrix} -1 & 0 & 1 & 1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 & -1 \\ 0 & 1 & -1 & -1 & 1 & 0 \end{bmatrix}$$

The number of possible Trees are

- (a) 3 (b) 7 (c) 11 (d) 14

Ans: (b)

Sol: Given is reduced incidence matrix, so, Number of trees = $\det|[A_r][A_r]^T|$

$$[A_r][A_r]^T = \begin{bmatrix} -1 & 0 & 1 & 1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 & -1 \\ 0 & 1 & -1 & -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} -1 & 1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \\ 1 & 0 & -1 \\ -1 & 0 & 1 \\ 0 & -1 & 0 \end{bmatrix}$$



$$[A_r][A_r]^T = \begin{bmatrix} 4 & -1 & -3 \\ -1 & 3 & -1 \\ -3 & -1 & 4 \end{bmatrix}$$

$$\det [A_r][A_r]^T = 4[12-1] + 1[-4-3] - 3[1+9]$$
$$= 44 - 7 - 30 = 7 \text{ trees only}$$

GATE / PSUs-2018

MORNING BATCH

HYDERABAD

Batches Starting
From

22

JAN 2017

GATE / PSUs-2018

WEEKEND BATCH

VIZAG

Batches Starting
From

28

JAN 2017

ESE / GATE / PSUs-2018

WEEKEND BATCH

TIRUPATI

Batches Starting
From

28

JAN 2017

ESE / GATE / PSUs-2018

MORNING BATCH

BHOPAL

Batches Starting
From

27

JAN 2017

ESE / GATE / PSUs-2018

MORNING BATCH

KUKATPALLY

Batches Starting
From

22

JAN 2017

GATE / PSUs-2018

WEEKEND BATCH

VIJAYAWADA


Batches Starting
From

22

JAN 2017



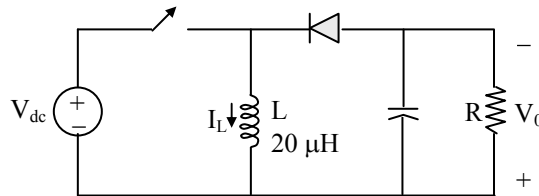
51. Input voltage to the following Buck-Boost converter is 20 V. Assume that the capacitor is large to treat output voltage is constant of 60 V. The switch is operating at 50 kHz with a duty ratio of 0.6. Average value of inductor current is _____.



- (A) 12 A (B) 7.2 A (C) 4.8 A (D) insufficient data


Ans: (C)

Sol:

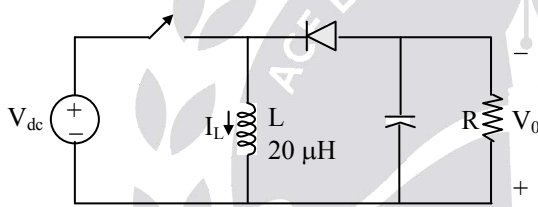

In CCM Buck Boost, $V_0 = V_{dc} \left[\frac{D}{1-D} \right] = 20 \times \frac{0.6}{0.4} = 30 \text{ V}$

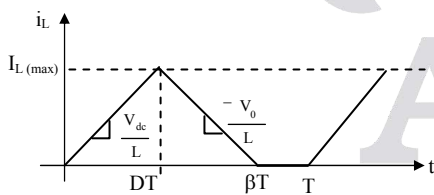But given $V_0 > 30 \text{ V}$, so it is discontinuous mode of operation.



From i_L waveform

$$\frac{20}{L} DT = \frac{60}{L} (\beta T - DT)$$

$$\Rightarrow 4DT = 3\beta T \Rightarrow \beta = \frac{4}{3} \times D = 0.8$$

$$\therefore I_{L \max} = \frac{V_{dc}}{L} \times DT = \frac{20}{20\mu} \times 0.6 \times 20\mu = 12 \text{ A}$$




$$I_{L (avg)} = \frac{\frac{1}{2} \times 12 \times 0.8 \times 20\mu}{20\mu} = 4.8 \text{ A}$$

DISTRACTOR LOGIC

Option (A) : $V_0 = V_{dc} \left[\frac{D}{1-D} \right] = 20 \times \frac{0.6}{0.4} = 30 \text{ V}$

$$\frac{20}{L} DT = \frac{30}{L} (\beta T - DT)$$

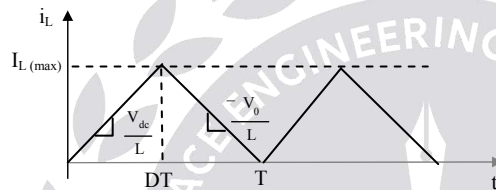
$\beta = 1$ so it is continuous conduction mode



$$\begin{aligned} i_{L \text{ peak}} &= \frac{V_{dc}}{L} \times DT \\ &= \frac{20}{20\mu} \times 0.6 \times 20\mu \\ &= 12 \text{ A} \end{aligned}$$

$$\therefore i_{L (avg)} = 12 \text{ A}$$

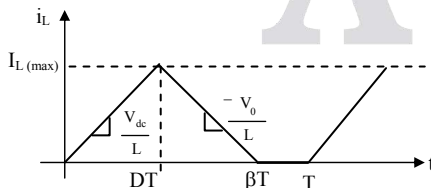Option B: $V_0 = V_{dc} \left[\frac{D}{1-D} \right] = 20 \times \frac{0.6}{0.4} = 30 \text{ V}$



From wave form

$$\frac{20}{L} DT = \frac{60}{L} (\beta T - DT)$$

$$\Rightarrow 4DT = 3\beta T \Rightarrow \beta = \frac{4}{3} \times D = 0.8$$



$$\therefore I_{L \max} = \frac{V_o}{L} \times DT = \frac{30}{20\mu} \times 0.6 \times 20\mu = 18 \text{ A}$$

$$I_{L \text{ (avg)}} = \frac{\frac{1}{2} \times 18 \times 0.8 \times 20\mu}{20\mu} = 7.2 \text{ A}$$

Option D: To check whether it is continuous or discontinuous condition, R value is required. But it is not given in the problem, so it is insufficient data.

52. The solution of $\frac{d^2 y}{dx^2} = y$ which passes through the origin and $\left(\ln 2, \frac{3}{4}\right)$ is _____

- (A) $y = \frac{e^x}{2} - e^{-x}$ (B) $\frac{3}{8}(e^x + e^{-x})$ (C) $y = \frac{1}{2}(e^x - e^{-x})$ (D) $\frac{e^x}{2} + e^{-x}$

Ans: (C)

Sol: The given equation is $(D^2 - 1)y = 0$

i.e., $D = \pm 1$ are the roots of A. E

$$\therefore y = (C_1 e^x + C_2 e^{-x})$$

If it passes through the origin i.e. $x = 0, y = 0$

$$\text{then } C_1 + C_2 = 0 \dots\dots\dots (1)$$

Similarly if passes through $\left(\ln 2, \frac{3}{4}\right)$

$$\text{then } \frac{3}{4} = (2C_1 + 0.5C_2) \dots\dots\dots (2) \text{ Since 1995}$$

By solving (1) & (2) for $C_1 ; C_2$

$$\text{We get } C_1 = \frac{1}{2} \text{ \& } C_2 = \frac{-1}{2}$$

$$\therefore y = \frac{1(e^x - e^{-x})}{2} \text{ is the required solution.}$$




53. The four arms of a wheatstone bridge are as follows: Arm AB = 100 Ω, BC = 10Ω, CD = 4Ω and DA = 50Ω. The galvanometer has a resistance of 20Ω and is connected across BD. A source of 10V DC is connected across AC, then the current through the galvanometer is
 (A) zero (B) 13.3mA (C) 5.18mA (D) 39mA

Ans: (C)

Sol: $V_{th} = V_B - V_D$

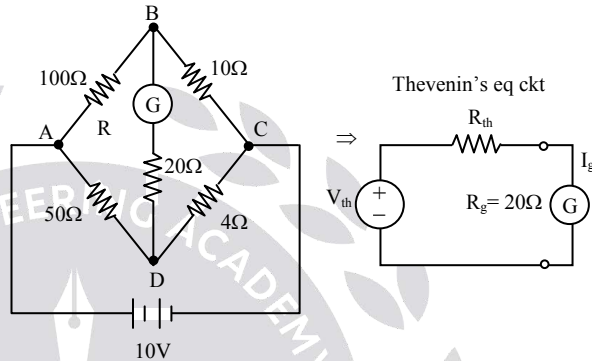
$$\begin{aligned}
 &= \left(10 \times \frac{10}{10+100} - 10 \times \frac{4}{4+50} \right) \\
 &= 0.9091 - 0.7407 \\
 &= 0.17V \\
 R_{th} &= \frac{100 \times 10}{100+10} + \frac{50 \times 4}{50+4} \\
 &= 9.09091 + 3.7037 \\
 &= 12.7946\Omega \\
 I_g &= \frac{V_{th}}{R_{th} + 20} = \frac{0.17}{12.7946 + 20} = 5.18mA
 \end{aligned}$$



DISTRACTOR LOGIC

Option: (A) if bridge is balanced, $i_g = 0$

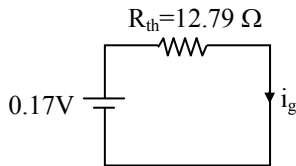Option: (B) if galvanometer resistance is neglected



$$i_g = \frac{0.17}{12.179} = 0.01329 \text{ A} = 13.3 \text{ mA}$$

Option: (D) if AB & AD branches are interchanged

$$\begin{aligned}
 V_{th} &= \frac{10 \times 10}{10+50} - \frac{10 \times 4}{4+100} \\
 &= 1.28 \text{ Volts}
 \end{aligned}$$

$$R_{th} = \frac{10 \times 50}{10+50} + \frac{4 \times 100}{104}$$



55. The synchronous speed of an induction motor is 900 rpm. Under a blocked rotor condition, the input power to the motor is 45 kW at 193.6A. The stator resistance per phase is 0.2Ω and the transformation ratio is $a = 2$. The ohmic value of the rotor resistance per phase is

- (A) 0.05Ω (B) 0.1Ω (C) 0.25Ω (D) 0.8Ω

Ans: (A)

Sol: $P_{BR} = 3I_{BR}^2 (R_1 + R_2^1)$
 $= 3I_{BR}^2 (R_1 + a^2R_2)$

$$0.2 + 4 \times R_2 = \frac{45 \times 10^3}{3 \times 193.6^2}$$

$$R_2 = 0.05\Omega$$

DISTRACTOR LOGIC

Option:B $P_{BR} = 3I_{BR}^2 (R_1 + R_2^1)$
 $= 3I_{BR}^2 (R_1 + aR_2)$
 $0.2 + 2 \times R_2 = \frac{45 \times 10^3}{3 \times 193.6^2}$

$$R_2 = 0.1\Omega$$

Option:C $P_{BR} = I_{BR}^2 (R_1 + R_2^1)$
 $= I_{BR}^2 (R_1 + a^2R_2)$
 $0.2 + 4 \times R_2 = \frac{45 \times 10^3}{193.6^2}$
 $R_2 = 0.25 \Omega$

Option:D $P_{BR} = 3I_{BR}^2 (R_1 + R_2^1)$
 $= 3I_{BR}^2 \left(R_1 + \frac{R_2}{a^2} \right)$

$$0.2 + \frac{R_2}{4} = \frac{45 \times 10^3}{3 \times 193.6^2}$$

$$R_2 = 0.8 \Omega$$




56. A protection system is installed with $1\frac{1}{2}$ cycle circuit breaker. If the relay issued TRIP signal to breaker at voltage zero instant, the breaker operating time is
 (A) 30ms (B) 35ms (C) 25 ms (D) 40ms

Ans (B)

Sol: Voltage zero means current is peak

For 50Hz,
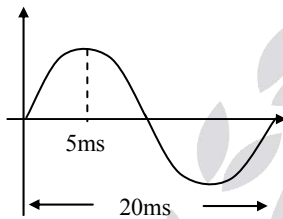
$$\text{Time period (T)} = \frac{1}{50} \text{ m sec} = 20 \text{ m sec}$$



$1\frac{1}{2}$ cycle circuit breaker \Rightarrow circuit breaker opening time = $20 + 10 = 30\text{ms}$

Arcing time = 5ms

Circuit breaker operating time


$$= \text{opening time} + \text{arcing time}$$

$$= 30 + 5 = 35\text{ms}$$

DISTRACTOR LOGIC

Option-A: Voltage zero means current is peak for 50Hz,
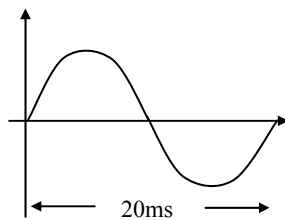
$$\text{Time period (T)} = \frac{1}{50} \text{ m sec} = 20 \text{ m sec}$$




$1\frac{1}{2}$ cycle circuit breaker \Rightarrow circuit breaker opening time = $20 + 10 = 30\text{ms}$



Option-C: Voltage zero means current is peak

For 50Hz,
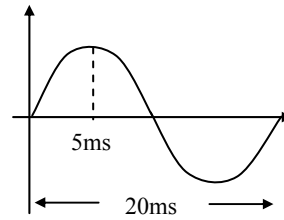
$$\text{Time period (T)} = \frac{1}{50} \text{ m sec} = 20 \text{ m sec}$$



$1\frac{1}{2}$ cycle circuit breaker \Rightarrow circuit breaker opening time = 20 + 10 = 30ms

Arcing time = 5ms

Circuit breaker operating time


$$= \text{opening time} - \text{arcing time}$$

$$= 30 - 5 = 25 \text{ ms}$$

Option-D: Voltage zero means current is peak

For 50Hz,
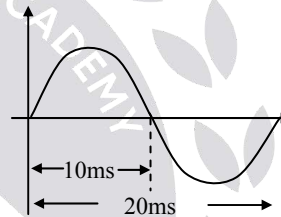
$$\text{Time period (T)} = \frac{1}{50} \text{ m sec} = 20 \text{ m sec}$$



$1\frac{1}{2}$ Cycle circuit breaker \Rightarrow circuit breaker opening time = 20 + 10 = 30ms

Arcing time = 10 ms

Circuit breaker operating time

$$= \text{opening time} - \text{arcing time}$$

$$= 30 + 10 = 40 \text{ ms}$$

57. The input signal $x(t) = 4 + \cos(4\pi t) - \sin(8\pi t)$ is passed through a filter with impulse response $h(t) = \text{Sinc}^2(t) \cos(16\pi t)$. Then the output is _____

(A) $\frac{1}{4} \cos(4\pi t)$

(B) $-0.5 \sin(8\pi t)$

(C) 0

(D) $4 + \cos(4\pi t) - \sin(8\pi t)$




Ans: (C)

Sol: The input frequencies are $f_1 = 0$, $f_2 = 2\text{Hz}$, $f_3 = 4\text{Hz}$

$$\text{Sinc}^2(t) \leftrightarrow \text{Tri}(f)$$

$$H(f) = \frac{\text{Tri}(f - 8) + \text{Tri}(f + 8)}{2}$$

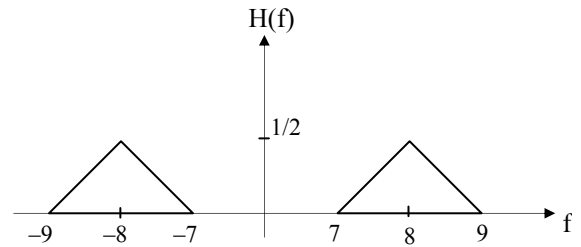So no input frequencies are passed through the filter



Distractor Logic:

Option A: If you feel filter spectrum covers the frequency range from 1 – 3Hz misinterpretation of

Ans(A)

Option B: If you feel filter spectrum covers the frequency range from 3 – 5Hz misinterpretation of


Ans(B)

Option C: Correct option

Option D: If you feel that $h(t)$ is ideal all pass filter with pass band gain of 1, that passes all frequencies.

misinterpretation of Ans(D)

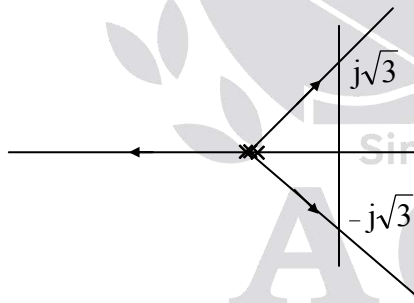58. The root loci diagram of a unity feedback system is given below. The closed loop transfer function for $K = 2$, is



(A) $\frac{2}{s^3 + 3s^2 + 3s + 1}$

(B) $\frac{1}{s^3 + 3s^2 + 3s + 1}$

(C) $\frac{1}{s^3 + 3s^2 + 3s + 2}$

(D) $\frac{2}{s^3 + 3s^2 + 3s + 3}$



Ans: (D)

Sol: $\tan 60^\circ = \frac{\sqrt{3}}{x} \Rightarrow x = 1$


Pole is at $s = -1$

Open loop TF $G(s) = \frac{K}{(s+1)^3}$

Closed loop TF = $\frac{G(s)}{1+G(s)H(s)}$

$H(s) = 1, K = 2$
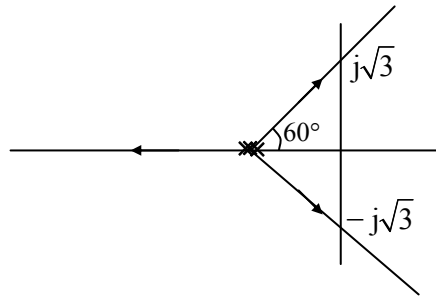
$$\text{CLTF} = \frac{\frac{2}{(s+1)^3}}{1 + \frac{2}{(s+1)^3}} = \frac{2}{s^3 + 3s^2 + 3s + 3}$$



DISTRACTOR LOGIC:

Option A: Three poles are at $s = -1$

$$\therefore \text{TF} = \frac{K}{(s+1)^3} = \frac{2}{(s+1)^3} = \frac{2}{s^3 + 3s^2 + 3s + 1}$$

Option B: Three poles are at $s = -1$

$$\text{TF} = \frac{1}{(s+1)^3} = \frac{1}{s^3 + 3s^2 + 3s + 1}$$


Option C: Three poles at $s = -1$

$$\text{OLTF} = \frac{1}{(s+1)^3}$$

$$\text{CLTF} = \frac{\frac{1}{(s+1)^3}}{1 + \frac{1}{(s+1)^3}} = \frac{1}{s^3 + 3s^2 + 3s + 2}$$



59. The following counter is a

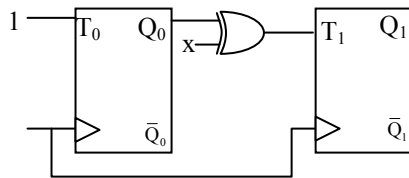


- (A) up counter when $x = 0$
(C) up counter when $x = 1$

- (B) down counter when $x = 0$
(D) always up counter

Ans: (A)


Sol: If $x = 0 \Rightarrow T_1 = Q_0$

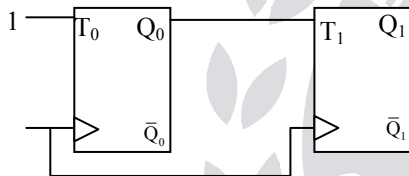

Present state		T ₁	T ₀	Next state	
Q ₁	Q ₀			Q ₁	Q ₀
0	0	0	1	0	1
0	1	1	1	1	0
1	0	0	1	1	1
1	1	1	1	0	0

\therefore If $x = 0$ given counter is up counter

If $x = 1 \Rightarrow T_1 = \bar{Q}_0$

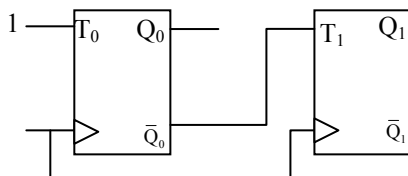



Present state		T ₁	T ₀	Next state	
Q ₁	Q ₀			Q ₁	Q ₀
0	0	1	1	1	1
0	1	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	0

∴ If x = 1 given counter is down counter.

60. Two identical generators are connected in parallel to a common bus. Sequence reactances of each generator are $X_1 = X_2 = j0.2$ pu and $X_0 = j0.05$ pu. The neutral of one of the generator is connected to ground by reactance of $j0.05$ pu and other generator neutral is isolated from ground. A most common short circuit fault is taking place at the common busbar with a fault reactance of $j0.05$ pu. If the operating voltage of busbar is 13.2 kV, then the voltage of zero sequence network in kV is
 (A) 2.77 (B) 3.54 (C) 6.66 (D) 4.42

Ans: (A)

Sol: $X_{1eq} = \frac{j0.2}{2} = j0.1$

$X_{2eq} = \frac{j0.2}{2} = j0.1$

$X_{0eq} = X_0 + 3X_n + 3X_F$
 $= 0.05 + 3 \times 0.05 + 3 \times 0.05$
 $= 0.35$


$I_{R_0} = I_{R_1} = \frac{E_{R_1}}{Z_{1eq} + Z_{2eq} + Z_{0eq}}$
 $= \frac{1.0}{j0.1 + j0.1 + j0.35}$

$I_{R_0} = I_{R_1} = \frac{1.0}{j0.55} = 1.82 \angle -90^\circ$

$V_{R_0} = -I_{R_0} X_{0eq} = -1.82 \angle -90^\circ \times 0.2 \angle 90^\circ$

$V_{R_0} = -0.364 = 0.364$ pu

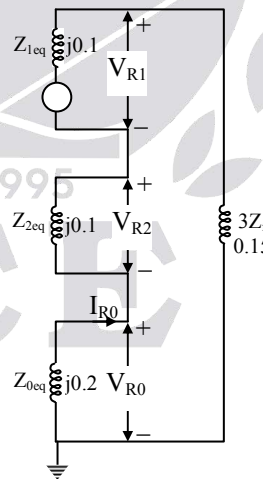$V_{R_0} = 0.364 \times \frac{13.2}{\sqrt{3}} = 2.77$ kV





DISTRACTOR LOGIC

Option B: $X_{1eq} = j0.2$

$$X_{2eq} = j0.2$$

$$\begin{aligned} X_{0eq} &= X_0 + 3X_n + 3X_f \\ &= 0.05 + 3 \times 0.05 + 3 \times 0.05 \\ &= 0.35 \end{aligned}$$


$$I_{R_0} = I_{R_1} = \frac{E_{R_1}}{Z_{1eq} + Z_{2eq} + Z_{0eq}} = \frac{1.0}{j0.2 + j0.2 + j0.35}$$

$$I_{R_0} = I_{R_1} = \frac{1.0}{j0.75} = 1.33 \angle -90^\circ$$

$$V_{R_0} = -I_{R_0} X_{0eq} = -1.33 \angle -90^\circ \times 0.35 \angle 90^\circ$$

$$V_{R_0} = -0.465 = 0.465 \text{ pu}$$
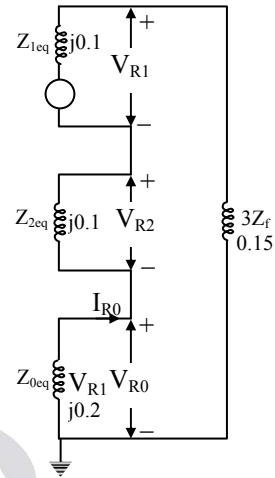
$$V_{R_0} = 0.465 \times \frac{13.2}{\sqrt{3}} = 3.54 \text{ kV}$$



Option C:

$$X_{1eq} = \frac{j0.2}{2} = j0.1$$

$$X_{2eq} = \frac{j0.2}{2} = j0.1$$

$$\begin{aligned} X_{0eq} &= X_0 + 3X_n + 3X_f \\ &= 0.05 + 3 \times 0.05 + 3(0.05) \\ &= 0.35 \end{aligned}$$


$$I_{R_0} = I_{R_1} = \frac{E_{R_1}}{Z_{1eq} + Z_{2eq} + Z_{0eq}} = \frac{1.0}{j0.1 + j0.1 + j0.2}$$

$$I_{R_0} = I_{R_1} = \frac{1.0}{j0.4} = 2.5 \angle -90^\circ$$

$$V_{R_0} = -I_{R_0} X_{0eq} = -2.5 \angle -90^\circ \times 0.35 \angle 90^\circ$$

$$V_{R_0} = -0.875 = 0.875 \text{ pu}$$
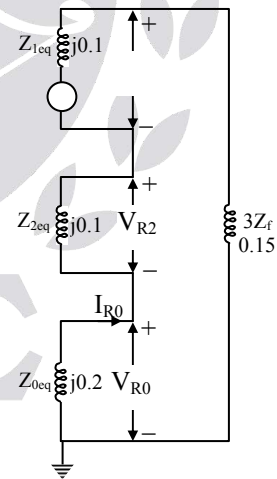
$$V_{R_0} = 0.875 \times \frac{13.2}{\sqrt{3}} = 6.66 \text{ kV}$$





Option D: $X_{1eq} = j0.2$

$$X_{2eq} = j0.2$$

$$\begin{aligned} X_{0eq} &= X_0 + 3X_n + 3X_f \\ &= 0.05 + 3 \times 0.05 + 3 \times 0.05 \\ &= 0.35 \end{aligned}$$


$$I_{R_0} = I_{R_1} = \frac{E_{R_1}}{Z_{1eq} + Z_{2eq} + Z_{0eq}} = \frac{1.0}{j0.2 + j0.2 + j0.2}$$

$$I_{R_0} = I_{R_1} = \frac{1.0}{j0.6} = 1.66 \angle -90^\circ$$

$$V_{R_0} = -I_{R_0} X_{0eq} = -1.66 \angle -90^\circ \times 0.35 \angle 90^\circ$$

$$V_{R_0} = -0.581 = 0.581 \text{ pu}$$
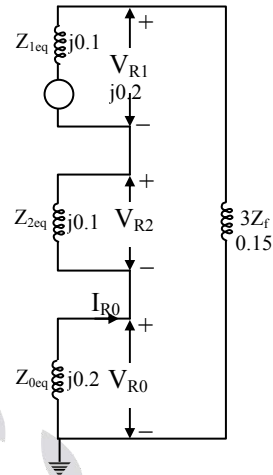
$$V_{R_0} = 0.581 \times \frac{13.2}{\sqrt{3}} = 4.42 \text{ kV}$$



61. $\int_C \frac{z \cos z}{\left(z - \frac{\pi}{2}\right)^2} dz = ?$ where 'C' is $|z - 1| = 1$

- (A) $i\pi$ (B) $-i\pi$ (C) $i\pi^2$ (D) $-i\pi^2$

Ans: (D)

Sol: $z = \frac{\pi}{2} = \frac{3.14}{2} = 1.57$ is a pole of order '2' lies inside 'C'

$$\therefore \int_C \frac{z \cos z}{\left(z - \frac{\pi}{2}\right)^2} dz = 2\pi i f' \left(\frac{\pi}{2} \right) \text{ (where } f(z) = z \cos z \text{)}$$

$$= 2\pi i \left(\frac{-\pi}{2} \right)$$

$$= -\pi^2 i$$



62. $f(x, y) = (x^2 + y^2 + 6x + 12)$ has
 (A) maximum value at $(-3, 0)$ (B) minimum value at $(-3, 0)$
 (C) maximum value at $(0, -3)$ (D) minimum value at $(0, -3)$

Ans: (B)

Sol: $\frac{\partial f}{\partial x} = (2x + 6) = 0 \dots\dots\dots (1)$

$\frac{\partial f}{\partial y} = 2y = 0 \dots\dots\dots (2)$


By solving (1) & (2) for $(x, y) = (-3, 0)$ is the stationary point

$r = \frac{\partial^2 f}{\partial x^2} = 2, s = \frac{\partial^2 f}{\partial x \partial y} = 0, t = \frac{\partial^2 f}{\partial y^2} = 2$

\therefore At $(-3, 0); (rt - s^2) = 4$ & $r = 2$

\therefore we get minimum value of $f(x, y)$

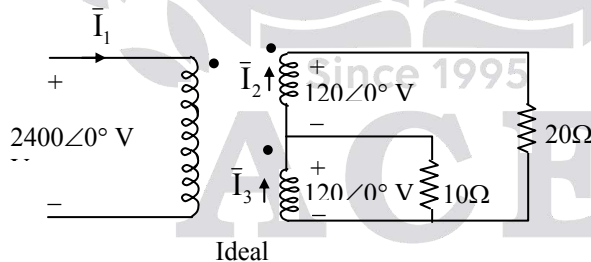63. An ideal residential distribution transformer is connected as shown in the Fig. Assume that the two series-connected secondary windings are identical. Determine the primary current and minimum kVA rating of a 2400:240/120V transformer required to sustain this load without risk of winding over-temperature.



- (A) 1.8 A, 5.76 kVA (B) 1.03 A, 4.07 kVA
 (C) 1.8 A, 2.88 kVA (D) 1.03 A, 2.03 kVA

Ans: (A)

Sol: $\bar{I}_2 = \frac{240\angle 0^\circ}{20} = 12\angle 0^\circ \text{ A}$

$\bar{I}_3 = \frac{120\angle 0^\circ}{10} + \bar{I}_2 = 12\angle 0^\circ + 12\angle 0^\circ = 24\angle 0^\circ \text{ A}$

$\bar{I}_1 = \frac{120}{2400} \bar{I}_2 + \frac{120}{2400} \bar{I}_3 = \frac{120}{2400} (36\angle 0^\circ) = 1.8\angle 0^\circ \text{ A}$



Since \bar{I}_3 is the larger secondary current, the rating is dictated by the lower secondary winding; thus,

$$S_R = 2V_3I_3 = 2(120)(24) = 5.76 \text{ kVA}$$

DISTRACTOR LOGIC

Option B: $\bar{I}_2 = \frac{240\angle 0^\circ}{20} = 12\angle 0^\circ \text{ A}$

$$\bar{I}_3 = \frac{120\angle 0^\circ}{10} + \bar{I}_2 = 12\angle 0^\circ + 12\angle 0^\circ = 16.97\angle 0^\circ \text{ A}$$

$$\bar{I}_1 = \frac{120}{2400} \bar{I}_2 + \frac{120}{2400} \bar{I}_3 = \frac{120}{2400} (36\angle 0^\circ) = 1.03\angle 0^\circ \text{ A}$$

$$S_R = 2V_3I_3 = 2(120)(16.97) = 4.072 \text{ kVA}$$

Option C: $\bar{I}_2 = \frac{240\angle 0^\circ}{20} = 12\angle 0^\circ \text{ A}$

$$\bar{I}_3 = \frac{120\angle 0^\circ}{10} + \bar{I}_2 = 12\angle 0^\circ + 12\angle 0^\circ = 24\angle 0^\circ \text{ A}$$

$$\bar{I}_1 = \frac{120}{2400} \bar{I}_2 + \frac{120}{2400} \bar{I}_3 = \frac{120}{2400} (36\angle 0^\circ) = 1.8\angle 0^\circ \text{ A}$$

$$S_R = 2V_3I_3 = (120)(24) = 2.88 \text{ kVA}$$

Option D: $\bar{I}_2 = \frac{240\angle 0^\circ}{20} = 12\angle 0^\circ \text{ A}$

$$\bar{I}_3 = \frac{120\angle 0^\circ}{10} + \bar{I}_2 = 12\angle 0^\circ + 12\angle 0^\circ = 16.97\angle 0^\circ \text{ A}$$

$$\bar{I}_1 = \frac{120}{2400} \bar{I}_2 + \frac{120}{2400} \bar{I}_3 = \frac{120}{2400} (36\angle 0^\circ) = 1.03\angle 0^\circ \text{ A}$$

$$S_R = 2V_3I_3 = (120)(16.97) = 2.036 \text{ kVA}$$

64. If the probability that a man aged 'X' years will die within a year be 'P' then the chance that out of 5 men A, B, C, D and E each aged 'X' years, 'A' will die during the year and be the first person to die is _____

(A) $\frac{P(1-P)^4}{5}$

(B) $\frac{1-(1-P)^5}{5}$

(C) $1 - (1 - P)^5$

(D) $P(1 - P)^4$



Ans: (B)

Sol: The probability that a man aged 'X' year will not die within a year is $(1 - P)$

\therefore The chance that none of the five persons die within a year is $(1 - P)^5$

$\therefore 1 - (1 - P)^5$ gives atleast one of the five dies within a year

\therefore Anyone has the same chance of being dead first, hence the required probability = $\frac{1 - (1 - P)^5}{5}$.

NO-DISTRACTOR LOGIC

65. An RC low pass filter has the impulse response $h(t) = e^{-t} u(t)$. The response of the system due to the input $x(t) = e^{2t} u(-t)$ is _____

(A) $\frac{1}{3} e^{2t} u(-t) + \frac{1}{3} e^{-t} u(t)$

(B) $\frac{-1}{3} e^{2t} u(t) - \frac{1}{3} e^{-t} u(-t)$

(C) $-\frac{1}{3} e^{2t} u(-t) - \frac{1}{3} e^{-t} u(t)$

(D) $e^{2t} u(-t) + e^{-t} u(t)$

Ans: (A)

Sol: $H(s) = \frac{1}{s+1}; \sigma > -1$

$X(s) = \frac{-1}{s-2}; \sigma < 2$

Output ROC = $(\sigma > -1) \cap (\sigma < 2) = -1 < \sigma < 2$

$Y(s) = X(s)H(s) = \frac{-1}{(s-2)(s+1)} = \frac{-1/3}{s-2} + \frac{1/3}{s+1}$

Based on the output ROC, take inverse Laplace transform

$y(t) = \frac{1}{3} e^{2t} u(-t) + \frac{1}{3} e^{-t} u(t)$

Distractor Logic:

Option A: Correct Answer

Option B: In the partial fraction if we feel pole '2' is right sided & pole '-1' is left sided

Option C: In the partial fraction expansion if we take negative sign of Y(s) as it is

Option D: In the partial fraction expansion if we miss $\frac{1}{3}$ multipliers