



ACE

Engineering Academy
Leading Institute for ESE/GATE/PSUs

*Hyderabad | Kukatpally | Delhi | Bhopal | Pune | Bhubaneswar | Bengaluru
Lucknow | Patna | Chennai | Vijayawada | Vizag | Tirupathi | Kolkata*

GATE 2017

Electrical Engineering

Questions with Detailed Solutions

FORENOON SESSION

All Queries related to GATE - 2017 key are to be send to the following email address
hyderabad@aceenggacademy.com | Contact Us : 040 - 23234418, 19, 20


01. The following measurements are obtained on a single phase load: $V = 220 \text{ V} \pm 1\%$. $I = 5.0 \text{ A} \pm 1\%$ and $W = 555 \text{ W} \pm 2\%$. If the power factor is calculated using these measurements, the worst case error in the calculated power factor in percent is _____. (Give answer up to one decimal place.)

01. Ans: 4

Sol: Power factor $\cos\phi = \frac{P}{VI} = \frac{2\%}{1\% \times 1\%} \Rightarrow \frac{2\%}{2\%} = 4\%$

In multiplication and division percentage values will be added up.

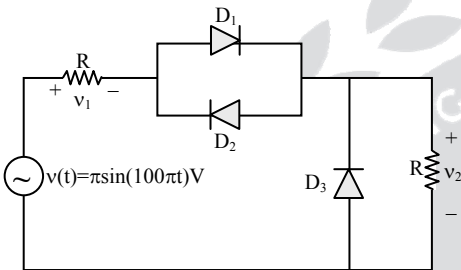02. For the circuit shown in the figure below, assume that diodes D_1 , D_2 and D_3 are ideal.




The DC components of voltages v_1 and v_2 , respectively are

- (a) 0 V and 1 V
- (b) -0.5 V and 0.5 V
- (c) 1 V and 0.5 V
- (d) 1 V and 1 V

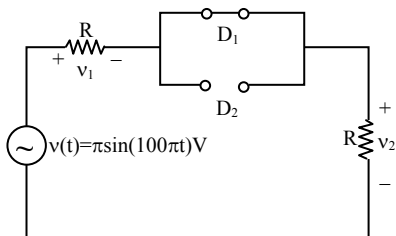02. Ans: (b)

Sol: During +ve cycle input:


$D_1 \rightarrow \text{ON}$, D_2 and $D_3 \rightarrow \text{OFF}$



$$v_1 = v_2 = \frac{v(t)}{2}$$

During – ve cycle input:

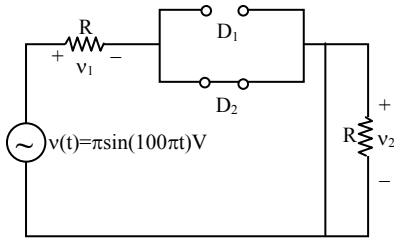$D_1 \rightarrow \text{OFF}$, D_2 and $D_3 \rightarrow \text{ON}$




$$v_2 = 0 \text{ and } v_1 = v(t)$$

The voltage waveforms are shown in below figure.

$$\begin{aligned} \text{DC component of } v_1 \text{ is} &= \frac{V_{m1}}{\pi} + \frac{V_{m2}}{\pi} \\ &= \frac{\pi/2}{\pi} + \frac{-\pi}{\pi} \Rightarrow -0.5 \text{ V} \end{aligned}$$
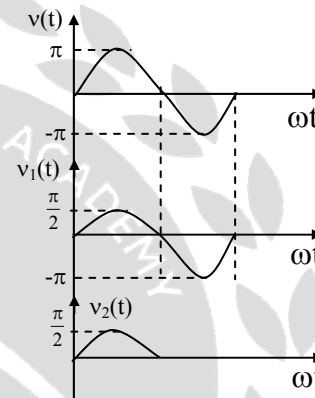
$$\text{DC component of } v_2 \text{ is } \frac{\pi/2}{\pi} \Rightarrow 0.5 \text{ V}$$



- 03 The transfer function of a system is given by $\frac{V_0(s)}{V_i(s)} = \frac{1-s}{1+s}$

Let the output of the system be $v_0(t) = v_m \sin(\omega t + \phi)$ for the input $v_i(t) = V_m \sin(\omega t)$. Then the minimum and maximum values of ϕ (in radians) are respectively

- (a) $\frac{-\pi}{2}$ and $\frac{\pi}{2}$ (b) $\frac{-\pi}{2}$ and 0 (c) 0 and $\frac{\pi}{2}$ (d) $-\pi$ and 0

03. Ans: (d)

$$\text{Sol: } \angle \left(\frac{1-j\omega}{1+j\omega} \right) = \angle (-\tan^{-1} \omega - \tan^{-1} \omega)$$

At $\omega = 0$, $\phi = 0^\circ$ (Maximum)

At $\omega = \infty$, $\phi = -180^\circ$ (Minimum)

04. Consider the system with following input-output relation $y[n] = (1+(-1)^n)x[n]$

Where, $x[n]$ is the input and $y[n]$ is the output. The system is

- (a) invertible and time invariant
(b) invertible and time varying

- (c) non-invertible and time invariant
- (d) non-invertible and time varying

04. Ans: (D)

Sol: $y(n) = [1 + (-1)^n] x(n)$

$y_1(n) = [1 + (-1)^n] x(n - n_0)$

$y(n - n_0) = [1 + (-1)^{n-n_0}] x(n - n_0)$

$y_1(n) \neq y(n - n_0)$; so, time variant

if $x_1(n) = u(n)$

$\Rightarrow y_1(n) = [1 + (-1)^n] u(n)$

$= [2, 0, 2, 0, 2, 0, 2, \dots]$


$x_2(n) = [1, 0, 1, 0, 1, 0, \dots]$

$\Rightarrow y_2(n) = [1 + (-1)^n] x_2(n) = [2, 0, 2, 0, \dots]$

Non-invertible,


The system is time variant and non-invertible.

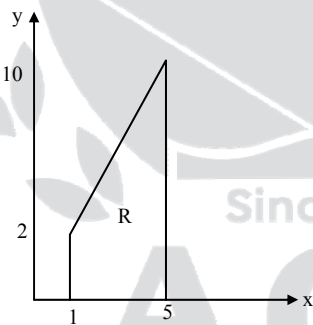05. Let $I = c \iint_{RXY} y^2 dx dy$, where R is the region shown in the figure and $c = 6 \times 10^{-4}$. The value of I equals _____. (Give the answer up to two decimal places)



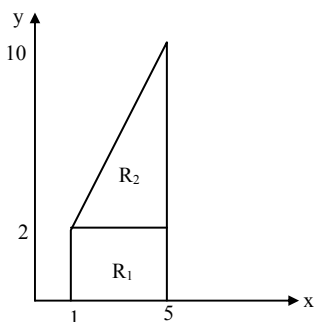05. Ans: 0.99

Sol: Let $I = c \iint_{RXY} y^2 dx dy$ ----- (1)





Now ,

$$\begin{aligned} \iint_R xy^2 dx dy &= \iint_{R_1} xy^2 dx dy + \iint_{R_2} xy^2 dx dy \\ &= \int_0^2 \int_1^5 xy^2 dx dy + \int_2^{10} \int_{y/2}^5 xy^2 dx dy \\ &= \int_0^2 \left(\frac{x^2}{2} \right)_1^5 y^2 dy + \int_2^{10} \left(\frac{x^2}{2} \right)_{y/2}^5 y^2 dy \\ &= \int_0^2 \left(\frac{25}{2} - \frac{1}{2} \right) y^2 dy + \int_2^{10} \left(\frac{25}{2} - \frac{y^2}{8} \right) y^2 dy \\ &= 12 \int_0^2 y^2 dy + \int_2^{10} \left(\frac{25y^2}{2} - \frac{y^4}{8} \right) dy \\ &= 12 \left(\frac{y^3}{3} \right)_0^2 + \int_2^{10} \left(\frac{25y^2}{2} - \frac{y^4}{8} \right) dy \\ &= 32 + \left(\frac{25y^3}{6} - \frac{y^5}{40} \right)_2^{10} \\ &= 32 + \left(\frac{25000}{6} - \frac{10^5}{40} \right) - \left(\frac{200}{6} - \frac{32}{40} \right) \\ &= 1666.13 \\ \therefore I &= 0.9996 \end{aligned}$$

06. Consider $g(t) = \begin{cases} t - \lfloor t \rfloor, & t \geq 0 \\ t - \lceil t \rceil, & \text{otherwise} \end{cases}$,


where $t \in \mathbb{R}$

Here, $\lfloor t \rfloor$ represent the largest integer less than or equal to t and $\lceil t \rceil$ denotes the smallest integer greater than or equal to t . The coefficient of the second harmonic component of the Fourier series representing $g(t)$ is _____

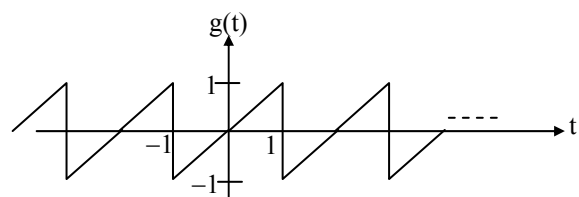06. Ans: -0.3183

Sol: $g(t) = \begin{cases} t - \lfloor t \rfloor, & t \geq 0 \\ t - \lceil t \rceil, & \text{otherwise} \end{cases}$

From the given data we can draw the signal as



The above signal shows odd symmetry, so calculate b_n ?

$$T = 2 \Rightarrow \omega_0 = \pi$$

$$b_n = \frac{2}{T} \int_0^T g(t) \sin \omega_0 t dt = \frac{4}{T} \int_0^{T/2} g(t) \sin \omega_0 t dt$$

$$= \frac{4}{2} \int_0^1 t \sin \pi t dt$$

$$= 2 \left[\frac{-t \cos n\pi t}{n\pi} + \frac{\sin(n\pi t)}{(n\pi)^2} \right]_0^1$$

$$= 2 \left[\frac{-\cos n\pi}{n\pi} \right] = \frac{-2(-1)^n}{\pi n}$$

Coefficient of II harmonic is

$$b_2 = \frac{-2}{2\pi} = \frac{-1}{\pi} = -0.3183$$


07. For the power semiconductor devices IGBT, MOSFET, Diode and Thyristor, which one of the following statements is TRUE?

- (a) All the four are majority carrier devices
- (b) All the four are minority carrier devices
- (c) IGBT and MOSFET are majority carrier devices, whereas Diode and Thyristor are minority carrier devices.
- (d) MOSFET is majority carrier device, whereas IGBT, Diode, Thyristor are minority carrier devices.

07. **Ans: (d)**

Sol: Only MOSFET is majority carrier device. And remaining all other devices belongs to minority carrier devices

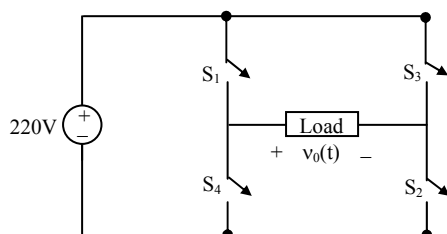08. In the converter circuit shown below, the switches are controlled such that the load voltage $v_0(t)$ is a 400 Hz square wave.



The RMS value of the fundamental component of $v_0(t)$ in volts is _____ .

08. Ans: 198.07

Sol: Given circuit is 1 – phase full bridge voltage source inverter. It is mentioned that output voltage is a square wave and its amplitude will be 220 V

Therefore, RMS value of fundamental component of output voltage

$$= \frac{2\sqrt{2}}{\pi} V_{dc} = \frac{2\sqrt{2}}{\pi} \times 220 = 198.07 \text{ V}$$

09. A solid iron cylinder is placed in a region containing a uniform magnetic field such that the cylinder axis is parallel to the magnetic field direction. The magnetic field lines inside the cylinder will

- (a) bend closer to the cylinder axis
- (b) bend farther away from the axis
- (c) remain uniform as before
- (d) cease to exist inside the cylinder

09. Ans: (c)

Sol: Iron is a ferrromagnetic material.

In such a material, there will be magnetic dipoles associated with the spins of unpaired electrons, just like in a paramagnetic material.

In the absence of any external magnetic field:

In a paramagnetic material these dipoles are oriented in all possible directions, and so their dipole moments are cancelled out, and the material as a whole is non-magnetic.

In a ferromagnetic material, all the dipoles point in only one direction. (This can be explained using quantum mechanics).

But in that case, every nail, every piece of iron, must be a powerful permanent magnet; why is it not so?

The alignment occurs in small patches, called domains. Each domain has several billions of dipoles, all pointing in one direction; but in any small piece of iron, there are billions of such domains, dipoles of each domain oriented randomly in some direction. The net magnetization of all these dipoles is zero.

When an external magnetic field \vec{B}_{ext} is applied, domains with the same direction as \vec{B}_{ext} grow, others shrink; the material is magnetized in the direction of \vec{B}_{ext} .

So when a solid iron cylinder is placed in a uniform \vec{B}_{ext} with the axis of the cylinder along the direction of \vec{B}_{ext} , the field lines in the cylinder remain parallel and uniform as before, but their density increases.

10. Let $z(t) = x(t)*y(t)$. where “*” denotes convolution. Let c be a positive real-valued constant. Choose the correct expression for $z(ct)$.
- (a) $c.x(ct) * y(ct)$ (b) $x(ct) * y(ct)$
 (c) $c.x(t) * y(ct)$ (d) $c. x(ct) * y(t)$

10. **Ans: (a)**

Sol: $z(t) = x(t) * y(t)$ as per property of convolution

$$x(ct) * y(ct) = \frac{1}{|c|} z(ct)$$

$$z(ct) = |c| x(ct) * y(ct)$$

Given ‘ c ’ is a positive integer, so

$$z(ct) = c x(ct) * y(ct)$$

11. The Boolean expression $AB + A\bar{C} + BC$ simplifies to
- (a) $BC + A\bar{C}$ (b) $AB + A\bar{C} + B$ (c) $AB + A\bar{C}$ (d) $AB + BC$

11. **Ans: (A)**

Sol: $AB + A\bar{C} + BC$

$$= AB(C + \bar{C}) + A\bar{C} + BC$$

$$= ABC + AB\bar{C} + A\bar{C} + BC$$

$$= BC(A + 1) + A\bar{C}(B+1)$$

$$= A\bar{C} + BC$$

12. For a complex number z , $\lim_{z \rightarrow i} \frac{z^2 + 1}{z^3 + 2z - i(z^2 + 2)}$ is
- (a) $-2i$ (b) $-i$ (c) i (d) $2i$

12. **Ans: (D)**

Sol: $\lim_{z \rightarrow i} \frac{z^2 + 1}{z^3 + 2z - i(z^2 + 2)}$ $\left(\frac{0}{0} \text{ form} \right)$

Applying L’Hospital rule

$$= \lim_{z \rightarrow i} \frac{2z}{3z^2 + 2 - i(2z)}$$

$$= \frac{2(i)}{3(-1) + 2 - i(2i)} = \frac{2i}{-3 + 2 + 2} = 2i$$

13. A source is supplying a load through a 2-phase, 3-wire transmission system as shown in figure below. The instantaneous voltage and current in phase-a are $v_{an} = 220\sin(100\pi t)$ V and $i_a =$

15. A 10 bus power system consists of four generator buses indexed as G1, G2, G3, G4 and six load buses indexed as L1, L2, L3, L4, L5, L6. The generator-bus G1 is considered as slack bus, and the load buses L3 and L4 are voltage controlled buses. The generator at bus G2 cannot supply the required reactive power demand, and hence it is operating at its maximum reactive power limit. The number of non-linear equations required for solving the load flow problem using Newton-Raphson method in polar form is _____.

15. Ans: 14

Sol: G₁ - Slack bus

G₂ – having reactive power

$$Q_2 \min \leq Q_2 \leq Q_2 \max$$

When it is operating at Q₂ max means there is a reactive power divergent. Hence it is working as load bus.

G₂ → 2 equations

G₃ → 1 equation

G₄ → 1 equation

L₁ → 2 equations

L₂ → 2 equations

L₅ → 2 equations

L₆ → 2 equations

L₃ → 1 equation

L₄ → 1 equation

Total No.of equations are 14

16. The slope and level detector circuit in a CRO has a delay of 100 ns. The start-stop sweep generator has a response time of 50 ns. In order to display correctly, a delay line of
- (a) 150 ns has to be inserted into the y-channel
 - (b) 150 ns has to be inserted into the x-channel
 - (c) 150 ns has to be inserted into both x and y channels
 - (d) 100 ns has to be inserted into both x and y channels

16. Ans: (a)

Sol: In order to display correctly, a delay line of 150 ns has to be inserted in to the Y-channel between output of vertical amplifier and Y-input of CRT.



USEFUL BOOKS FOR ESE(IES), GATE, PSUs

GATE (Previous Questions & Solutions)	IES (Previous Questions & Solutions)	
Electronics & Communication Engineering	Electronics & Telecommunication Engineering (Volume-I Obj)	Civil Engineering (Volume-I Obj)
Electrical Engineering	Electronics & Telecommunication Engineering (Volume-II Obj)	Civil Engineering (Volume-II Obj)
Mechanical Engineering	Electronics & Telecommunication Engineering (Paper-I Conv)	Civil Engineering (Paper-I Conv)
Civil Engineering	Electronics & Telecommunication Engineering (Paper-II Conv)	Civil Engineering (Paper-II Conv)
Computer Science & Information Engineering	Electrical Engineering (Volume-I Obj)	Mechanical Engineering (Volume-I Obj)
Instrumentation Engineering	Electrical Engineering (Volume-II Obj)	Mechanical Engineering (Volume-II Obj)
General Aptitude (Numerical & Verbal)	Electrical Engineering (Paper-I Conv)	Mechanical Engineering (Paper-I Conv)
GATE Practice Booklet (Vol-I),(Vol-II)	Electrical Engineering (Paper-II Conv)	Mechanical Engineering (Paper-II Conv)
Engineering Mathematics Solutions	General Studies & Engineering Aptitude	

Special Books For ISRO / PSUs (Previous Years Questions With Solutions & Useful for BARC, SAIL, BEL, NPCIL, AAI & OTHER PSUs)
Special Books For GENCO TRANSCO & DISCOMS (Previous Questions & Solutions of Various Exams Useful for SSC JE, SAIL, AEE, STEEL PLANT, ISRO, BARC and Other PSUs)

- * **GATE** Solutions for more than **30 years**
- * **IES** Solutions for more than **32 years**
- * Solutions, **Chapterwise and Subjectwise**
- * You can **Buy Online** also



040 - 2323 4437 / 011 - 2953 3467



+91 93976 99966



TEST SERIES

IES (Prelims & Mains)

Streams : **EC, EE, ME, CE**

Test Type	Prelims		Mains
	Online	Offline	Offline
Chapter-wise Tests	43	-	-
Subject-wise Grand Tests	31	20	08
Revision Tests	-	-	04
Full Lenth Mock Tests	08	04	04

GATE

Streams : **EC, EE, ME, CE, CS, IN, PI**

Test Type	No. Of Tests (Online)
Chapter-wise Tests	20
Subject-wise Grand Tests	40
Full Lenth Mock Tests	12

Pre-GATE Exam (Center Based Test)

ACE uses technology powered by TCS iON for conducting Pre-GATE 2018 (Center based MOCK Test) on PAN India basis with Analytics.




Video Solutions are available for

Selected Objective Questions for Online Exams



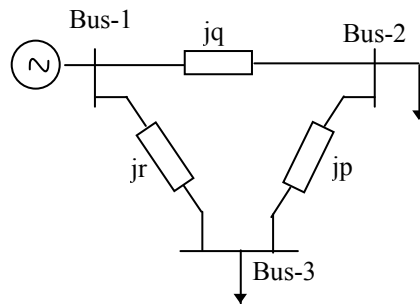17. A 3-bus power system is shown in the figure below, where the diagonal elements of Y-bus matrix are: $Y_{11} = -j12$ pu, $Y_{22} = -j15$ pu and $Y_{33} = -j7$ pu.



The per unit values of the line reactances p, q and r shown in the figure are

- (a) $p = -0.2, q = -0.1, r = -0.5$ (b) $p = 0.2, q = 0.1, r = 0.5$
 (c) $p = -5, q = -10, r = -2$ (d) $p = 5, q = 10, r = 2$

17. Ans: (b)

Sol: $\frac{1}{jr} + \frac{1}{jq} = -j12$ (1)

$\frac{1}{jq} + \frac{1}{jp} = -j15$ (2)

$\frac{1}{jp} + \frac{1}{jr} = -j7$ (3)

(1) $\Rightarrow \frac{1}{r} + \frac{1}{q} = 12$ (4)

$\frac{1}{q} + \frac{1}{p} = 15$ (5)

$\frac{1}{p} + \frac{1}{r} = 7$ (6)

(4) + (5) + (6) $\Rightarrow 2\left(\frac{1}{p} + \frac{1}{q} + \frac{1}{r}\right) = 34$

$\Rightarrow \left(\frac{1}{p} + \frac{1}{q} + \frac{1}{r}\right) = 17$

(7) - (4) $\Rightarrow \frac{1}{p} = 5 \Rightarrow p = 0.2$ pu

(7) - (5) $\Rightarrow \frac{1}{r} = 2 \Rightarrow r = 0.5$ pu

(7) - (6) $\Rightarrow \frac{1}{q} = 10 \Rightarrow q = 0.1$ pu

18. A three-phase, 50 Hz, star-connected cylindrical-rotor synchronous machine is running as a motor. The machine is operated from a 6.6 kV grid and draws current at unity power factor (UPF). The synchronous reactance of the motor is 30 Ω per phase. The load angle is 30°. The power delivered to the motor in kW is _____ (Give the answer up to one decimal place)

18. 838.31

Sol: By neglecting armature resistance the active power drawn by a synchronous motor is

$$P = 3 \times \frac{E_t V_t}{X_s} \sin \delta$$


$$\Rightarrow E_t = \sqrt{V_t^2 + (I_a X_s)^2}; V_t = \frac{6600}{\sqrt{3}} \text{ V/ph}$$

$$\cos \delta = \frac{V_t}{E_t} \Rightarrow E_t = \frac{V_t}{\cos \delta} = \frac{(6.6/\sqrt{3}) \times 1000}{\cos(30)}$$

$$E_t = 4400 \text{ V/ph}$$

$$\Rightarrow P = (3) \left[\frac{4400 \times \frac{6600}{\sqrt{3}}}{30} \right] \sin(30)$$

$$P = 838.31 \text{ kW}$$

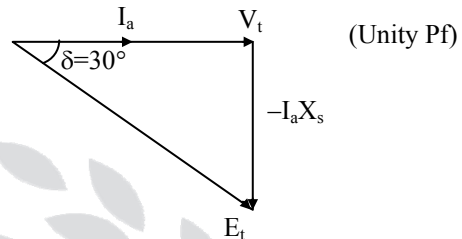


19. Consider an electron, a neutron and a proton initially at rest and placed along a straight line such that the neutron is exactly at the center of the line joining the electron and proton. At $t = 0$, the particles are released but are constrained to move along the same straight line. Which of these will collide first?

- (a) The particles will never collide (b) all will collide together
(c) proton and neutron (d) electron and neutron

19. Ans: (d)

Sol:

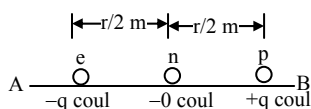

$t < 0$: The particles are at rest. No ext. field is mentioned in the problem. So the only force is that acting on e & p. This has a magnitude $\frac{q^2}{4\pi\epsilon_0 r^2}$, (attractive). No force on n. (Gravitational force neglected).

$t \geq 0$: The particles are allowed to move in the straight line AB. Electron and proton both start travelling towards neutron. Electron being lighter, has more acceleration; and reaches the neutron first and collides with it.

20. The matrix $A = \begin{bmatrix} \frac{3}{2} & 0 & \frac{1}{2} \\ 0 & -1 & 0 \\ \frac{1}{2} & 0 & \frac{3}{2} \end{bmatrix}$ has three distinct eigen values and one of its eigen vectors is $\begin{bmatrix} 1 \\ 0 \\ 1 \end{bmatrix}$.

Which one of the following can be another eigen vector of A?

(a) $\begin{bmatrix} 0 \\ 0 \\ -1 \end{bmatrix}$ (b) $\begin{bmatrix} -1 \\ 0 \\ 0 \end{bmatrix}$ (c) $\begin{bmatrix} 1 \\ 0 \\ -1 \end{bmatrix}$ (d) $\begin{bmatrix} 1 \\ -1 \\ 1 \end{bmatrix}$

20. **Ans: (C)**

Sol: Since eigen values are distinct and the matrix is symmetric then the corresponding eigen vectors are orthogonal

Then $X_1^T X_2 = 0$

By verification from options,

Given $X_1 = \begin{bmatrix} 1 \\ 0 \\ 1 \end{bmatrix}$, Let $X_2 = \begin{bmatrix} 1 \\ 0 \\ -1 \end{bmatrix}$

$\therefore X_1^T X_2 = 0$

21. A closed loop system has the characteristic equation given by $s^3 + Ks^2 + (K+2)s + 3 = 0$. For this system to be stable, which one of the following conditions should be satisfied?

(a) $0 < K < 0.5$ (b) $0.5 < K < 1$ (c) $0 < K < 1$ (d) $K > 1$

21. **Ans: (d)**


Sol:

$$\begin{array}{l|l} s^3 & 1 & K+2 \\ s^2 & K & 3 \\ s^1 & \frac{K^2 + 2K - 3}{K} & \\ s^0 & 3 & \end{array}$$

For stability $K > 0$ and $K^2 + 2K - 3 > 0$


So, $K^2 + 2K - 3 > 0 \Rightarrow$ i.e $K > 1$

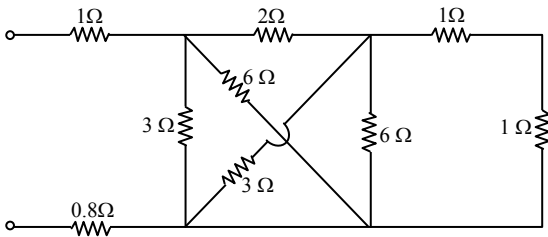22. The equivalent resistance between the terminals A and B is _____ Ω .



22. Ans: 3

Sol:

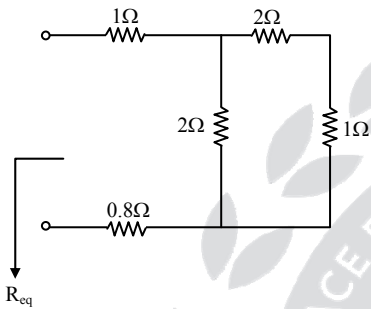

$$R_{eq} = 1.8 + [2//3] = 1.8 + \frac{6}{5} = 3 \Omega$$

SHORT TERM BATCHES FOR **GATE+PSUs -2018** STARTING FROM

HYDERABAD


29th APRIL 2017 onwards

GENERAL STUDIES BATCHES FOR **ESE-2018** STARTING FROM

HYDERABAD & DELHI

1st week of July 2017

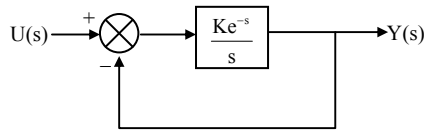23. Consider the unity feedback control system shown. The value of K that results in a phase margin of the system to be 30° is _____. (Give the answer up to two decimal places).



23. Ans: 1.05

Sol: $PM = 180^\circ + \angle \frac{Ke^{-j\omega_{gc}}}{j\omega_{gc}} = 30^\circ$

and $\left| \frac{Ke^{-j\omega_{gc}}}{j\omega_{gc}} \right| = 1$


$\Rightarrow \frac{K}{\omega_{gc}} = 1$

$\Rightarrow \omega_{gc} = K$

$PM = 180^\circ - \omega_{gc} - 90^\circ = 30^\circ$

$\Rightarrow \omega_{gc} = 60^\circ = \frac{\pi}{3} = 1.05$

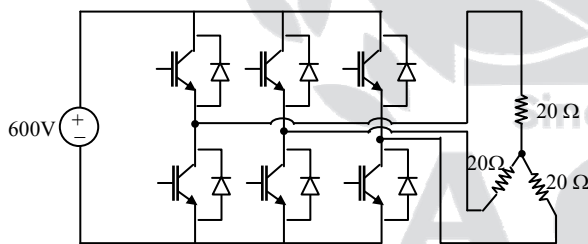24. A 3-phase voltage source inverter is supplied from a 600 V DC source as shown in the figure below. For a star connected resistive load of 20Ω per phase, the load power for 120° device conduction, in kW, is _____.



24. Ans: 9


Sol:

RMS value of phase voltage for 120° conduction mode is $V_{ph} = \frac{V_{dc}}{\sqrt{6}} = \frac{600}{\sqrt{6}}$ V

Power delivered to load $P_o = 3 \times \frac{V_{ph}^2}{R}$

$$= 3 \times \frac{\left(\frac{600}{\sqrt{6}}\right)^2}{20} = 9 \text{ kW}$$

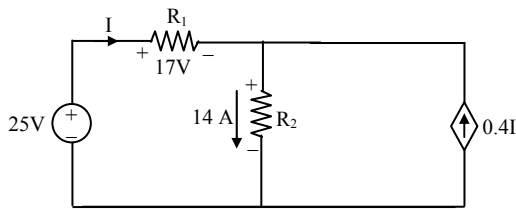25. The power supplied by the 25 V source in the figure shown below is _____ W.



25. **Ans: 250**

Sol: From KCL,


$$I + 0.4I = 14$$

$$1.4I = 14$$

$$\Rightarrow I = 10 \text{ A}$$

$$\text{So, power supplied} = 25 \times 10 = 250 \text{ W}$$

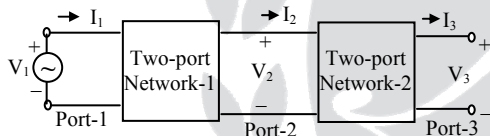26. Two passive two-port networks are connected in cascade as shown in figure. A voltage source is connected at port 1.



Given: $V_1 = A_1 V_2 + B_1 I_2$

$$I_1 = C_1 V_2 + D_1 I_2$$

$$V_2 = A_2 V_3 + B_2 I_3$$

$$I_2 = C_2 V_3 + D_2 I_3$$

$A_1, B_1, C_1, D_1, A_2, B_2, C_2$ and D_2 are the generalized circuit constants. If the Thevenin equivalent circuit at port 3 consists of a voltage source V_T and an impedance Z_T , connected in series, then

(a) $V_T = \frac{V_1}{A_1 A_2}, Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$

(b) $V_T = \frac{V_1}{A_1 A_2 + B_1 C_2}, Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2}$

(c) $V_T = \frac{V_1}{A_1 + A_2}, Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 + A_2}$

(d) $V_T = \frac{V_1}{A_1 A_2 + B_1 C_2}, Z_T = \frac{A_1 B_2 + B_1 D_2}{A_1 A_2 + B_1 C_2}$

26. **Ans: (d)**

Sol:
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ C_1 A_2 + D_1 C_2 & C_1 B_2 + D_1 D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

For Z_{Th} , $V_1 = 0$

$$\Rightarrow Z_{th} = \frac{V_3}{(-I_3)}$$

$$(A_1A_2 + B_1C_2)V_3 + (A_1B_2 + B_1D_2)I_3 = 0$$

$$\frac{V_3}{I_3} = \frac{-(A_1B_2 + B_1D_2)}{A_1A_2 + B_1C_2}$$






$$Z_{Th} = \frac{A_1B_2 + B_1D_2}{A_1A_2 + B_1C_2}$$

For V_{Th} , $V_3 = V_{Th}$ and $I_3 = 0$

$$V_1 = (A_1A_2 + B_1C_2)V_{Th}$$


$$\Rightarrow V_T = \frac{V_1}{A_1A_2 + B_1C_2}$$

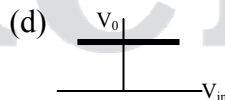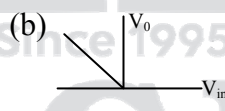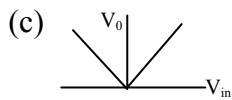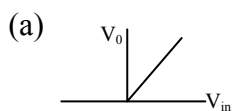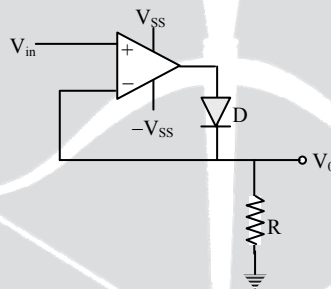27. The approximate transfer characteristic for the circuit shown below with an ideal operational amplifier and diode will be




27. Ans: (a)


Sol: The given circuit is redrawn as

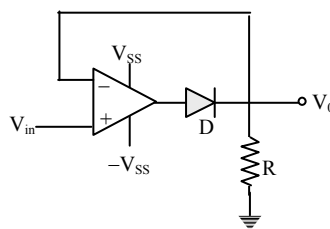

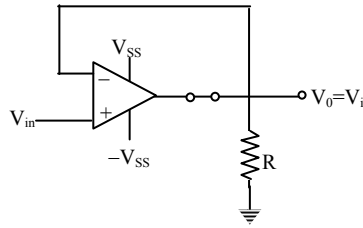
When $V_{in} > 0$, Diode is ON, then replaced by SC



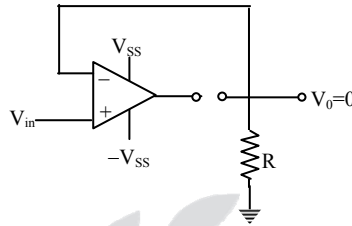When $V_{in} < 0$, Diode OFF, then replaced by OC



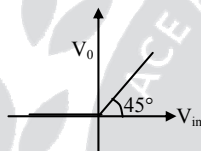The output characteristic is shown below.



ESE - 2017 MAINS (STAGE - II)

Exclusive Postal Coaching Offer for Prelims Qualified Students

For **E&T / EE / CE / ME**

FREE DOUBT CLEARING SESSIONS

Through



Through



Live Video Classes.

28. Only one of the real roots of $f(x) = x^6 - x - 1$ lies in the interval $1 \leq x \leq 2$ and bisection method is used to find its value. For achieving an accuracy of 0.001, the required minimum number of iterations is _____.

28. Ans: 10

Sol: $f(x) = x^6 - x - 1$ in $[1, 2]$ we know that $\frac{|b-a|}{2^n} \leq \epsilon$

$$\Rightarrow \frac{1}{2^n} \leq 0.001$$

$$\Rightarrow 2^n \geq \frac{1}{0.001}$$

$$\Rightarrow 2^n \geq 1000$$

$$\Rightarrow \ln 2^n \geq \ln(1000)$$


$$\Rightarrow n \ln 2 \geq \ln(1000)$$

$$\Rightarrow n \geq \frac{\ln(1000)}{\ln 2}$$

$$\Rightarrow n \geq 9.966$$

$$n \approx 10$$

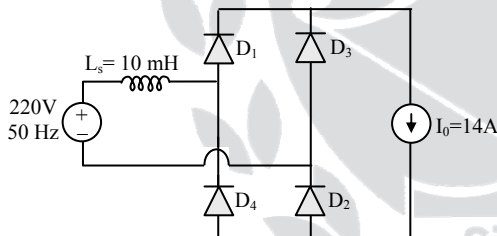29. The figure below shows an uncontrolled diode bridge rectifier supplied from a 220 V, 50 Hz, 1-phase ac source. The load draws a constant $I_0 = 14$ A. The conduction angle of the diode D_1 in degrees (rounded off to two decimal places) is _____.



29. Ans: 224.17

Sol: When source inductance is not taken into account, each diode will conduct for 180°
When source inductance is taken into account, each diode will conduct for $(180 + \mu)^\circ$

Where μ is overlap angle and can be determined as follows:


$$\cos \mu = 1 - \frac{2\omega L_s I_0}{V_m}$$

$$\Rightarrow \cos \mu = 1 - \frac{2 \times 100\pi \times 10 \times 10^{-3} \times 14}{220\sqrt{2}} \times 14 = 0.71727$$

$$\Rightarrow \mu = 44.17^\circ$$

$$\therefore \text{Conduction angle for } D_1 \text{ is } 180 + 44.17 = 224.17^\circ$$

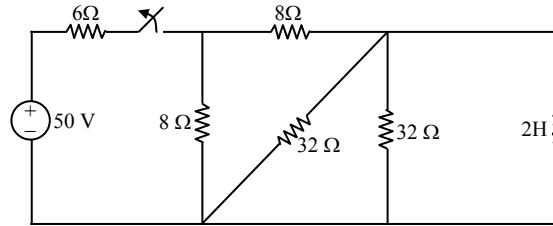30. The switch in the figure below was closed for a long time. It is opened at $t = 0$. The current in the inductor of 2 H for $t \geq 0$, is




- (a) $2.5e^{-4t}$ (b) $5e^{-4t}$ (c) $2.5e^{-0.25t}$ (d) $5e^{-0.25t}$

30. Ans: (a)


Sol: This is source free, first order R-L circuit

$$i(t) = I_0 e^{-t/\tau}$$

$$I_0 \rightarrow t = 0^-$$

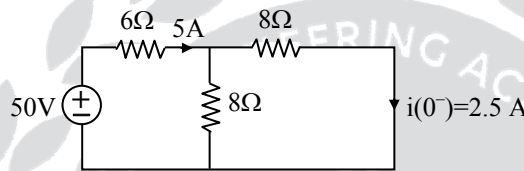

$$\tau = \frac{L}{R_{eq}}$$

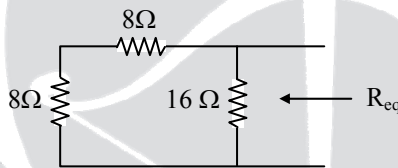


$$R_{eq} = 8\Omega \rightarrow \tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4}$$

$$i(t) = 2.5 e^{-t/4}$$

$$i(t) = 2.5 e^{-4t}$$

31. Consider the line integral $I = \int_c (x^2 + iy^2) dz$, where $z = x + iy$. The line c is shown in the figure

below.

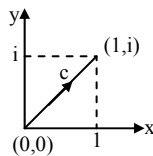

The value of I is

- (a) $\frac{1}{2}i$ (b) $\frac{2}{3}i$ (c) $\frac{3}{4}i$ (d) $\frac{4}{5}i$

31. Ans: (b)

Sol: Given C is $y = x$

$$\Rightarrow dy = dx$$

Then x varies from 0 to 1

$$I = \int_C (x^2 + iy^2) dz$$

$$= \int_0^1 (x^2 + ix^2)(dx + idx)$$

$$= (1+i)^2 \int_0^1 x^2 dx = (1+2i+i^2) \left[\frac{x^3}{3} \right]_0^1$$

$$= (1+2i-1) \left(\frac{1}{3} \right) = \frac{2i}{3}$$

32. Consider the differential equation $(t^2 - 81) \frac{dy}{dt} + 5ty = \sin(t)$ with $y(1) = 2\pi$. There exists a unique solution for this differential equation when t belongs to the interval

- (a) $(-2, 2)$ (b) $(-10, 10)$ (c) $(-10, 2)$ (d) $(0, 10)$

32. Ans: (a)

Sol: $(t^2 - 81) \frac{dy}{dt} + 5ty = \sin t$ with $y(1) = 2\pi$

$$\frac{dy}{dt} + \frac{5t}{(t^2 - 81)} y = \frac{\sin t}{(t^2 - 81)}$$

The given differential equation has no solution when $t = \pm 9$. These values do not lie in the interval $(-2, 2)$.

The solution of the given differential equation lies in the interval $(-2, 2)$.

\therefore Option (a) is correct

33. For a system having transfer function $G(s) = \frac{-s+1}{s+1}$, a unit step input is applied at time $t = 0$. The value of the response of the system at $t = 1.5$ sec (rounded off to three decimal places) is

33. Ans: 0.554

Sol: TF = $\frac{1-s}{1+s}$ Input = $\frac{1}{s}$ (unit step)

Output = (TF) (input)

$$= \left(\frac{1-s}{1+s} \right) \frac{1}{s}$$

$$\text{Output} = L^{-1} \left[\frac{1}{s} \times \frac{1-s}{1+s} \right]$$

$$= 1 - 2e^{-t}$$


$$\text{Output at } (t = 15) = 1 - 2e^{-1.5}$$

$$= 0.554$$

34. Two parallel connected, three-phase, 50 Hz, 11 kV, star-connected synchronous machines A and B, are operating as synchronous condensers. They together supply 50 MVAR to a 11 kV grid. Current supplied by both the machines are equal. Synchronous reactances of machine A and machine B are 1Ω and 3Ω , respectively. Assuming the magnetic circuit to be linear, the ratio of excitation current of machine A to that of machine B is _____. (Give the answer up to two decimal places).

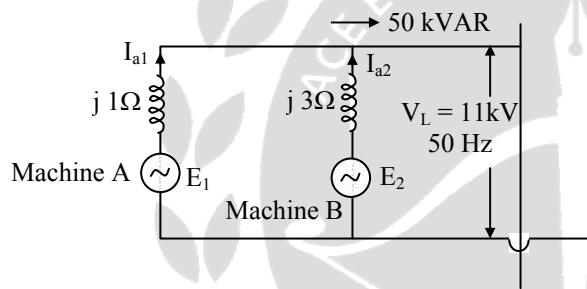34. **Ans: 0.74**

Sol: Two parallel connected 3- ϕ , 50 Hz, 11kV, star-connected synchronous machines A & B are operating as synchronous condensers.



The total reactive power supplied to the grid = 50 MVAR

$$3VI_{a1}\sin\phi_1 + 3VI_{a2}\sin\phi_2 = 50 \text{ MVAR}$$

$$3VI_{a1}\sin 90 + 3VI_{a2}\sin 90 = 50 \quad (\because \text{only reactive power } \text{pf} = \cos\phi = 0 \Rightarrow \phi = 90^\circ)$$

$$6VI_a = 50 \times 10^6 \quad (\because I_{a1} = I_{a2} = I_a)$$

$$I_a = \frac{50 \times 10^6}{6 \times \frac{11 \times 10^3}{\sqrt{3}}} = 1312.16 \text{ A}$$

$$\begin{aligned} \therefore E_1 &= V \angle 0 - I_{a1} \angle 90 \times X_{s1} \angle 90 \\ &= \frac{11 \times 10^3}{\sqrt{3}} \angle 0 - 1312.16 \angle 90 \times 1 \angle 90 \end{aligned}$$

$$\begin{aligned} &= 6350.8 \angle 0 - 1312.16 \angle 180 \\ &= 7662.96 \text{ V} \end{aligned}$$

$$\begin{aligned} E_2 &= V \angle 0 - I_{a2} \angle 90 \times X_{s2} \angle 90 \\ &= 6350.8 \angle 0 - 1312.16 \angle 90 \times 3 \angle 90 \\ &= 6350.8 \angle 0 - 3936.48 \angle 180 \\ &= 10,287.28 \text{ V} \end{aligned}$$

\therefore The ratio of excitation current of machine A to machine B is same as the ratio of the excitation emfs

$$\text{i.e., } \frac{E_1}{E_2} = \frac{7662.96}{10,287.28} = 0.7448$$



COAL INDIA LIMITED (CIL)

Management Trainee & Other PSUs

Classroom coaching

(General Knowledge / Awareness, Reasoning, Numerical Ability & General English)

Starts on

15th Feb 2017 @ Delhi

Online Test Series (EE | ME | CE)

Total Tests : 20

Starts from 17th Feb 2017

ESE - 2017

Mains (Stage - II)

Classroom Coaching Starts from 15th Feb 2017

at Hyderabad, Delhi & Pune

Offline Test Series : Starts from - 18th March 2017

Number of Tests : 16

Will Conduct at all Our centers

35. The positive, negative, and zero sequence reactances of a wye-connected synchronous generator are 0.2 pu, 0.2 pu, and 0.1 pu, respectively. The generator is on open circuit with a terminal voltage of 1 pu. The minimum value of the inductive reactance, in pu, required to be connected between neutral and ground so that the fault current does not exceed 3.75 pu if a single line to ground fault occurs at the terminals is _____ (assume fault impedance to be zero). (Give the answer up to one decimal place)

35. Ans: 0.1

Sol: $X_1 = j0.2$

$$X_2 = j0.2$$

$$X_0 = j0.1$$

$$X_F = 0 \text{ (zero fault reactance)}$$

$$X_n = ?$$

$$\text{L-G Fault: } I_F = \frac{3E_{R_1}}{Z_1 + Z_2 + Z_0 + 3Z_n}$$

$$Z_1 + Z_2 + Z_0 + 3Z_n = \frac{3 \times 1.0}{3.75}$$

$$0.2 + 0.2 + 0.1 + 3Z_n = \frac{3.0}{3.75}$$

$$3Z_n = 0.8 - 0.5$$


$$3Z_n = 0.3$$

$$Z_n = 0.1 \text{ pu}$$

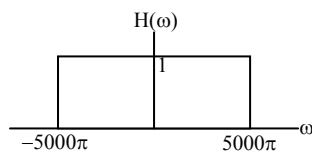36. Let the single

$$x(t) = \sum_{k=-\infty}^{+\infty} (-1)^k \delta\left(t - \frac{k}{2000}\right)$$

Be passed through an LTI system with frequency response $H(\omega)$, as given in the figure below.



The Fourier series representation of the output is given as

(a) $4000 + 4000\cos(2000\pi t)$
 $+ 4000\cos(4000\pi t)$

(b) $2000 + 2000\cos(2000\pi t)$
 $+ 2000\cos(4000\pi t)$




(c) $4000\cos(2000\pi t)$

(d) $2000\cos(2000\pi t)$

36. Ans: (c)

Sol:

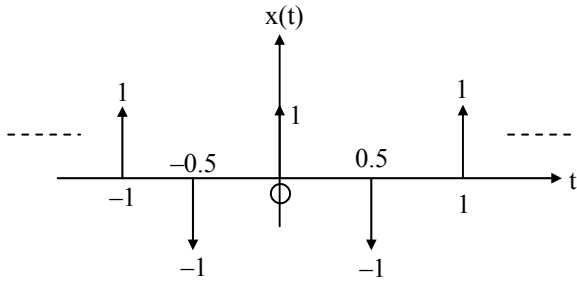

$$C_n = \frac{1}{T_0} \int_0^{T_0} x(t) e^{-jn\omega_0 t} dt$$

$$C_n = \frac{1}{1 \times 10^{-3}} \left[\int_0^1 x(t) e^{-jn\omega_0 t} dt \right]$$

$$C_n = 10^3 \left[1 - e^{-jn\omega_0 (0.5 \times 10^{-3})} \right]$$

$$C_n = 10^3 \left[1 - e^{-jn \left(\frac{2\pi}{1 \times 10^{-3}} \right) (0.5 \times 10^{-3})} \right]$$

$$C_n = 10^3 \left[1 - e^{-jn\pi} \right] = 1000 \left[1 - (-1)^n \right]$$


$$X(\omega) = 2\pi \sum_{n=-\infty}^{\infty} C_n \delta(\omega - n\omega_s)$$

$$X(\omega) = 2000\pi \sum_{n=-\infty}^{\infty} \left(1 - (-1)^n \right) \delta(\omega - 2000n\pi)$$

$$X(\omega) = 2000\pi \left[\dots 2\delta(\omega + 2000\pi) + 2\delta(\omega - 2000\pi) + \dots \right]$$

$$X(\omega) = 4000 \left[\delta(\omega + 2000\pi) + \delta(\omega - 2000\pi) + \dots \right]$$
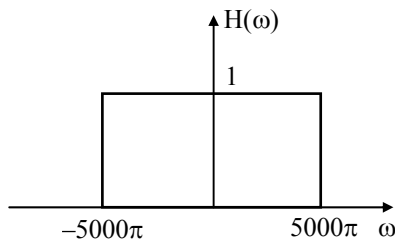
$$X(\omega) = 4000 \left[\cos(2000\pi t) + \cos(6000\pi t) + \dots \right]$$



The output of low part filter is

$$y(t) = 4000 \cos(2000\pi t)$$

37. A 220 V DC series motor runs drawing a current of 30 A from the supply. Armature and field circuit resistances are 0.4Ω and 0.1Ω , respectively. The load torque varies as the square of the speed. The flux in the motor may be taken as being proportional to the armature current. To reduce the speed of the motor by 50% the resistance in ohms that should be added in series with the armature is _____. (Give the answer up to two decimal places)

37. Ans: 10.75

Sol: Given a DC series motor

$$V_t = 220 \text{ V}$$

Before adding extra resistor

$$I_{a1} = 30 \text{ A}$$

$$\begin{aligned} E_{b1} &= V_t - I_{a1} (r_a + r_f) \\ &= 220 - (30) (0.4 + 0.1) \\ &= 205 \text{ V} \end{aligned}$$

After adding extra resistor speed reduced by 50%

$$T \propto N^2 ; N_2 = 0.5 N_1$$

$$\frac{T_1}{T_2} = \left(\frac{N_1}{N_2} \right)^2$$

$$\frac{T_1}{T_2} = \left(\frac{1}{0.5} \right)^2$$

$$\frac{T_1}{T_2} = 4$$

$$T = K_a \phi I_a ; \phi \propto I_a$$

$$\Rightarrow T \propto I_a^2$$

$$\frac{T_1}{T_2} = 4 = \left(\frac{30}{I_{a2}} \right)^2$$

$$I_{a2} = 30 / \sqrt{4} = 15 \text{ A}$$


$$\Rightarrow E_{b2} = V_t - I_{a2} (r_a + r_f + r_{ex})$$

$$E_{b2} = 220 - 15 (0.4 + 0.1 + r_{ex}) \dots\dots\dots(1)$$

$$\frac{E_{b1}}{E_{b2}} = \frac{I_{a1}}{I_{a2}} \times \frac{N_1}{N_2}$$

$$\frac{205}{E_{b2}} = \left(\frac{30}{15} \right) \left(\frac{N_1}{0.5 N_1} \right)$$
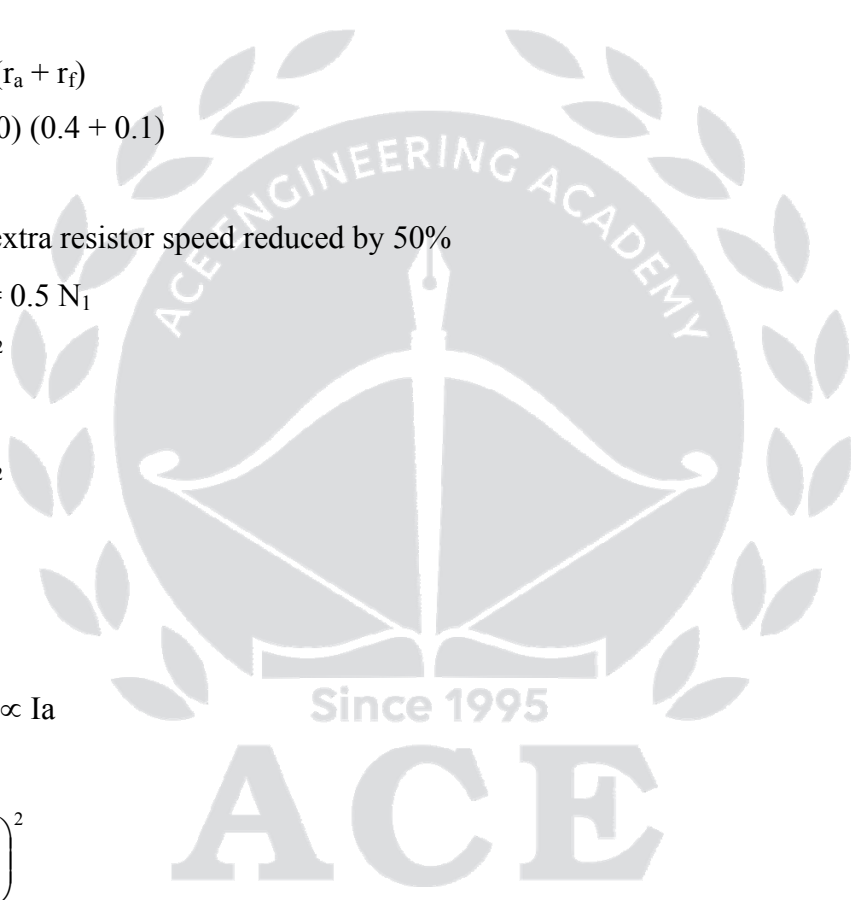
$$E_{b2} = 51.25 \text{ Volts} \dots\dots\dots(2)$$



Replace E_{b2} in equation (1)

$$51.25 = 220 - (15)(0.4 + 0.1 + r_{ex})$$

$$\Rightarrow r_{ex} = 10.75 \Omega$$

38. The transfer function of the system $Y(s)/U(s)$ whose state-space equations are given below is:

$$\begin{bmatrix} \dot{x}_1(t) \\ \dot{x}_2(t) \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 2 & 0 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} + \begin{bmatrix} 1 \\ 2 \end{bmatrix} u(t)$$

$$y(t) = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$$

(a) $\frac{(s+2)}{(s^2-2s-2)}$

(b) $\frac{(s-2)}{(s^2+s-4)}$

(c) $\frac{(s-4)}{(s^2+s-4)}$

(d) $\frac{(s+4)}{(s^2-s-4)}$

38. **Ans: (d)**

Sol: TF = $C[SI - A]^{-1}B$

$$SI - A = \begin{bmatrix} s-1 & -2 \\ -2 & s \end{bmatrix}$$

$$TF = \frac{\begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} s & 2 \\ 2 & s-1 \end{bmatrix} \begin{bmatrix} 1 \\ 2 \end{bmatrix}}{(s-1)(s)-4}$$

$$TF = \frac{s+4}{s^2-s-4}$$

39. Consider a causal and stable LTI system with rotational transfer function $H(z)$, whose corresponding impulse response begins at $n = 0$. Further more, $H(1) = \frac{5}{4}$. The poles of $H(z)$ are $P_k =$

$\frac{1}{\sqrt{2}} \exp\left(j \frac{(2k-1)\pi}{4}\right)$ for $k = 1, 2, 3, 4$. The zeros of $H(z)$ are all at $z = 0$. Let $g(n) = j^n h(n)$. The value of $g(8)$ equals _____. (Give the answer up to three decimal places).

39. **Ans: 0.097**

Sol: The poles of $H(z)$ are $P_k = \frac{1}{\sqrt{2}} \exp\left(j \frac{(2k-1)\pi}{4}\right)_{k=1,2,3,4}$

$$P_1 = \frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}} = \frac{1}{2} + \frac{j}{2} = \frac{1+j}{2}$$



$$P_2 = \frac{1}{\sqrt{2}} e^{\frac{j3\pi}{4}} = \frac{-1}{2} + \frac{j}{2}$$

$$P_3 = \frac{1}{\sqrt{2}} e^{\frac{j5\pi}{4}} = -\frac{1}{2} - \frac{j}{2}$$

$$P_4 = \frac{1}{\sqrt{2}} e^{\frac{j7\pi}{4}} = \frac{1}{2} - \frac{j}{2}$$

$$H(z) = \frac{kz^4}{(z - P_1)(z - P_2)(z - P_3)(z - P_4)} = \frac{kz^4}{z^4 + \frac{1}{4}}$$

Given $H(1) = 5/4$

$$\frac{5}{4} = \frac{k}{5/4}$$

$$k = \frac{25}{16}$$

$$H(z) = \frac{\frac{25}{16}z^4}{z^4 + \frac{1}{4}}$$

Given $g(x) = (j)^4 n(x)$

$G(t) = H(z/j)$

$$G(z) = \frac{\frac{25}{16} \left(\frac{z}{j}\right)^4}{\left(\frac{z}{j}\right)^4 + \frac{1}{4}} = \frac{\frac{25}{16}z^4}{z^4 + \frac{1}{4}}$$

$$G(z) = \frac{25}{16} - \frac{25}{64}z^{-4} + \frac{25}{256}z^{-8} + \dots$$

$$g(8) = \frac{25}{256} = 0.097$$

40. A three-phase, three winding $\Delta/\Delta/Y$ (1.1 kV/6.6 kV/400 V) transformer is energized from AC mains at the 1.1 kV side. It Supplies 900 kVA load at 0.8 power factor lag from the 6.6 kV winding and 300 kVA load at 0.6 power factor lag from the 400 V winding. The RMS line current in ampere drawn by the 1.1 kV winding from the mains is _____ .

40. Ans: 623

Sol: Given transformer is $\Delta/\Delta/Y$

Wdg (1) / wdg (2) / wdg (3)



$\Delta / \Delta / Y$

1.1 kV / 6.6 kV / 400 V

By applying superposition theorem

(a) Load on 6.6 kV (Δ) side is 900 kVA, 0.8 Pf lag

$$\Rightarrow 900 \times 10^3 = \sqrt{3} \times 6.6 \times 10^3 \times I_L$$

$$I_L = 78.72 \text{ A}$$

$$I_{ph}(\text{load}) = \frac{78.72}{\sqrt{3}} = 45.46 \text{ A/ph}$$

$$= 45.46 \angle -36.86 \text{ A/ph}$$

\Rightarrow The current on 1.1 kV side will be

$$I_{ph}(\text{source}) = 45.46 \times \left(\frac{6.6}{1.1} \right)$$

$$= 272.76 \angle -36.86 \text{ A/ph}$$

(b) Load on 400 V (Y) is 300 kVA, 0.6 pf lag

$$\Rightarrow 300 \times 10^3 = \sqrt{3} \times 400 \times I_L$$

$$I_L = \frac{300 \times 10^3}{\sqrt{3} \times 400} = 433.01 \text{ A}$$

$$\Rightarrow I_{ph} = 433.01 \angle -53.13 \text{ A/ph}$$

\therefore The current of source side (1.1 kV) will be


$$I_{ph}(\text{source}) = \frac{400/\sqrt{3}}{[1100]} \times 433.01$$

$$= 90.90 \angle -53.13 \text{ A/ph}$$

\therefore Total source phase current will be

$$= 272.76 \angle -36.86 + 90.90 \angle -53.13$$
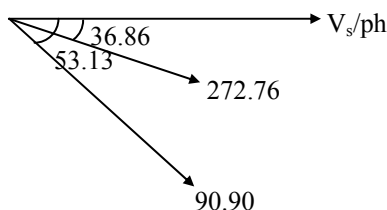
$$= 360.88 \text{ A/ph ; Pf} = 0.65 \text{ lag}$$



\therefore The line current will be = 623 A

41. A function $f(x)$ is defined as $f(x) = \begin{cases} e^x, & x < 1 \\ \ln x + ax^2 + bx, & x \geq 1 \end{cases}$, where $x \in \mathbb{R}$. Which one of the following statements is TRUE?
- (a) $f(x)$ is NOT differentiable at $x = 1$ for any values of a and b .
 (b) $f(x)$ is differentiable at $x = 1$ for the unique values of a and b .
 (c) $f(x)$ is differentiable at $x = 1$ for all values of a and b such that $a + b = e$.
 (d) $f(x)$ is differentiable at $x = 1$ for all values of a and b .

41. Ans: (b)

Sol: $f(x) = \begin{cases} e^x, & x < 1 \\ \log x + ax^2 + bx, & x \geq 1 \end{cases}$

$$f'(x) = \begin{cases} e^x, & x < 1 \\ \frac{1}{x} + 2ax + b, & x \geq 1 \end{cases}$$

At $x = 1$,

L H D = e , R H D = $1 + 2a + b$

Since $f(x)$ is differentiable at $x = 1$,

$$1 + 2a + b = e \Rightarrow 2a + b = e - 1 \dots\dots\dots(1)$$

Since $f(x)$ is continuous at $x = 1$,

At $x = 1$,

L H L = e

R H L = $a + b$

$$\Rightarrow a + b = e \dots\dots\dots(2)$$

Solving (1) and (2)

$$a = -1$$


$$b = e + 1$$

$\therefore a$ and b have unique values.

42. A 375 W, 230 V, 50 Hz, capacitor start single-phase induction motor has the following constants for the main and auxiliary windings (at starting): $Z_m = (12.50 + j15.75)\Omega$ (main winding), $Z_a = (24.50 + j12.75)\Omega$ (auxiliary winding). Neglecting the magnetizing branch, the value of the capacitance (in μF) to be added in series with the auxiliary winding to obtain maximum torque at starting is _____.

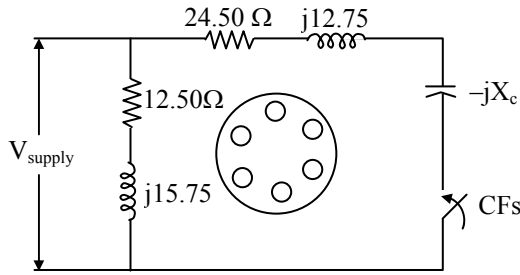42. Ans: 98.8

Sol: Given a single-phase capacitor start induction motor



To obtain maximum torque of starting, the main and auxiliary winding currents must have 90° electrical

$$-\tan^{-1}\left(\frac{X_m}{r_m}\right) + \tan^{-1}\left(\frac{X_a - X_c}{r_a}\right) = 90^\circ$$

$$-\tan^{-1}\left(\frac{15.75}{12.5}\right) + \tan^{-1}\left(\frac{12.75 - X_c}{24.50}\right) = 90^\circ$$


$$+ 12.75 - X_c = -0.79 \times 24.50$$

$$X_c = 32.19 \Omega$$

$$\Rightarrow \frac{1}{2\pi fc} = 32.19$$


$$C = \frac{1}{2\pi \times 50 \times 32.19} = 98.8 \mu\text{F}$$

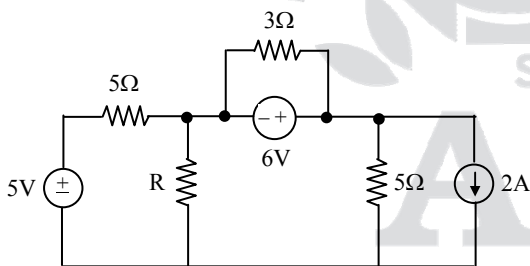43. In the circuit shown below, the maximum power transferred to the resistor R is _____ W.



43. Ans: 3.025

Sol: To find V_{Th} :

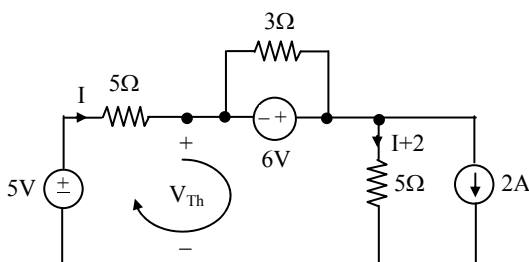




By applying KVL to the above loop

$$-5 + 5I - 6 + 5(I + 2) = 0$$

$$I = 2.1$$

$$V_{Th} = 5 - 2.1 \times 5 = -5.5$$

To find R_{Th} :

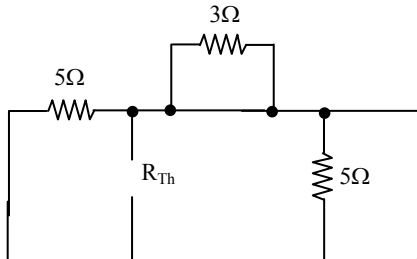


$$R_{Th} = 2.5$$

maximum power transferred is

$$\frac{V_{Th}^2}{4R_{Th}} = \frac{(5.5)^2}{4(2.5)} = 3.025$$

∴ Maximum power transferred = 3.025

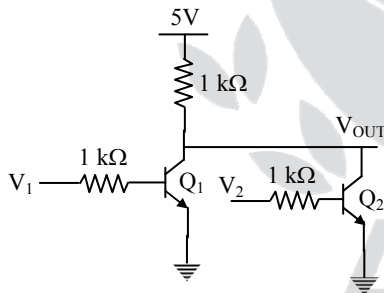44. The logical gate implemented using the circuit shown below where V_1 and V_2 are inputs (with 0 V as digital 0 and 5 V as digital 1) and V_{OUT} is the output is



- (a) NOT (b) NOR
(c) NAND (d) XOR


44. **Ans: (b)**

Sol:

V_1	V_2	Q_1	Q_2	V_{out}
0	0	OFF	OFF	1
0	1	OFF	ON	0
1	0	ON	OFF	0
1	1	ON	ON	0


$$V_{out} = \overline{V_1 + V_2} \Rightarrow \text{It is a NOR gate.}$$

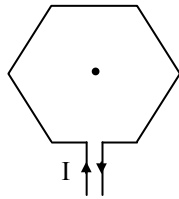45. The magnitude of magnetic flux density (B) in micro Teslas (μT), at the center of a loop of wire wound as a regular hexagon of side length 1 m carrying a current ($I = 1 A$) and placed in vacuum as shown in the figure is _____ .



45. Ans: 0.693


Sol:

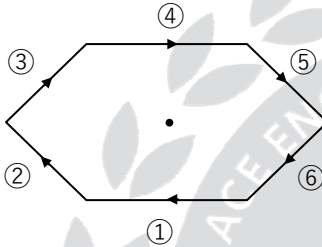

$$H = H_1 + H_2 + H_3 + H_4 + H_5 + H_6$$

Since the figure is regular hexagon, the field magnitude is same and is in the same direction.

$$\text{So, } H = 6H_1$$

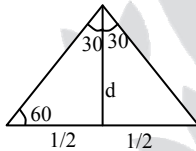

$$\tan 60 = \frac{d}{1/2}$$

$$\sqrt{3} = 2d$$

$$d = \frac{\sqrt{3}}{2}$$

$$H_1 = \frac{I}{4\pi d} (\sin \alpha_1 + \sin \alpha_2)$$

$$H_1 = \frac{1}{4\pi \left(\frac{\sqrt{3}}{2}\right)} \left(\frac{1}{2} + \frac{1}{2}\right)$$

$$H_1 = \frac{1}{2\sqrt{3}\pi}$$

$$H = 6H_1 = \frac{\sqrt{3}}{\pi}$$

$$B = \mu_0 H = 4\pi \times 10^{-7} \frac{\sqrt{3}}{\pi} = 4\sqrt{3} \times 10^{-7}$$

$$B = 0.693 \mu\text{T}$$

46. The output expression for the Karnaugh map shown below is

	CD			
	00	01	11	10
AB				
00	0	0	0	0
01	1	0	0	1
11	1	0	1	1
10	0	0	0	0

(a) $B\bar{D} + BCD$

(b) $B\bar{D} + AB$

(c) $\bar{B}D + ABC$

(d) $B\bar{D} + ABC$

46. Ans: (d)


Sol:

	CD			
	00	01	11	10
AB				
00	0	0	0	0
01	1	0	0	1
11	1	0	1	1
10	0	0	0	0

$$\Rightarrow F = B\bar{D} + A.B.C$$

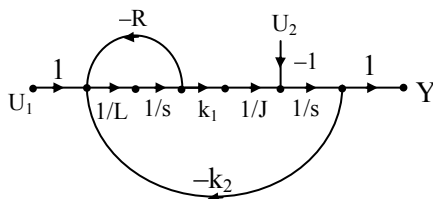47. In the system whose signal flow graph is shown in the figure. $U_1(s)$ and $U_2(s)$ are inputs. The

transfer function $\frac{Y(s)}{U_1(s)}$ is





$$(a) \frac{k_1}{JLs^2 + JRs + k_1k_2}$$

$$(b) \frac{k_1}{JLs^2 - JRs - k_1k_2}$$

$$(c) \frac{k_1 - U_2(R + sL)}{JLs^2 + (JR - U_2L)s + k_1k_2 - U_2R}$$

$$(d) \frac{k_1 - U_2(sL - R)}{JLs^2 - (JR + U_2L)s - k_1k_2 + U_2R}$$

47. Ans: (a)

$$\begin{aligned} \text{Sol: } \frac{Y(s)}{U_1(s)} &= \frac{\frac{1}{L} \cdot \frac{1}{s} \cdot K_1 \cdot \frac{1}{J} \cdot \frac{1}{s}}{1 - \left[\left(\frac{1}{L} \right) \left(\frac{1}{s} \right) (K_1) \left(\frac{1}{J} \right) \left(\frac{1}{s} \right) (-K_2) \right] - \left[\frac{-R}{LS} \right]} \\ &= \frac{K_1}{JLs^2 + JRs + K_1K_2} \end{aligned}$$

48. A separately excited DC generator supplies 150 A to a 145 V DC grid. The generator is running at 800 RPM. The armature resistance of the generator is 0.1Ω . If the speed of the generator is increased to 1000 RPM, the current in amperes supplied by the generator to the DC grid is _____.

48. Ans: 550

Sol: $V_t = 145$ V (Grid)

$$I_{a_1} = 150 \text{ A}; N_1 = 800 \text{ rpm}$$

$$R_a = 0.1 \Omega$$

$$N_2 = 1000 \text{ rpm}; V_{t_2} = 145 \text{ V (Grid)}$$

$$I_{a_2} = ?$$

$$\Rightarrow E_{g_1} = V_t + I_{a_1} r_a$$

$$= 145 + (150)(0.1) = 160 \text{ V}$$

$$\frac{E_{g_1}}{E_{g_2}} = \frac{N_1}{N_2} \quad [\because E_g = K_a \phi \omega, \phi = \text{const}]$$

$$E_{g_2} = \left(\frac{1000}{800} \right) (160)$$


$$= 200 \text{ V}$$

$$\Rightarrow I_{a_2} = \frac{200 - 145}{0.1} = 550 \text{ A}$$

$$I_{a_2} = 550 \text{ A}$$

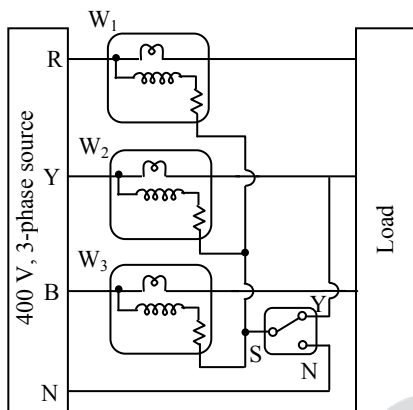49. The load shown in the figure is supplied by a 400 V (line-to-line) 3-phase source (RYB sequence). The load is balanced and inductive, drawing 3464 VA. When the switch S is in position N, the three

watt-meters W_1 , W_2 and W_3 read 577.35 W each. If the switch is moved to position Y, the readings of the watt-meters in watts will be:



- (a) $W_1 = 1732$ and $W_2 = W_3 = 0$ (b) $W_1 = 0$, $W_2 = 1732$ and $W_3 = 0$
 (c) $W_1 = 866$, $W_2 = 0$, $W_3 = 866$ (d) $W_1 = W_2 = 0$ and $W_3 = 1732$

49. Ans: (d)

Sol: $P = W_1 + W_2 + W_3 = 1732.05$

Power factor, $\cos \phi = \frac{1732.05}{3464} = 0.5 \text{ lag}$

$\sqrt{3} \times 400 \times I_L \times 0.5 = 1732.05$

$I_L = \frac{1732.05}{\sqrt{3} \times 400 \times 0.5} = 5 \text{ A}$

When switch is in position N

$W_1 = W_2 = W_3 = 577.35 \text{ W} \Rightarrow$ balanced load

\therefore total power consumed by load is

$W = W_1 + W_2 + W_3$

$W = 1732.05 \text{ W}$

Given load is inductive


And VA draw from source = 3464 VA

$$\begin{aligned} \therefore \text{power factor} &= \frac{W}{VA} \\ &= \frac{1732.05}{3464} \\ &= 0.5 \text{ lag} \end{aligned}$$

\Rightarrow power factor angle = -60° (\because lag)

When switch is connected in Y position pressure coil of W_2 is shorted

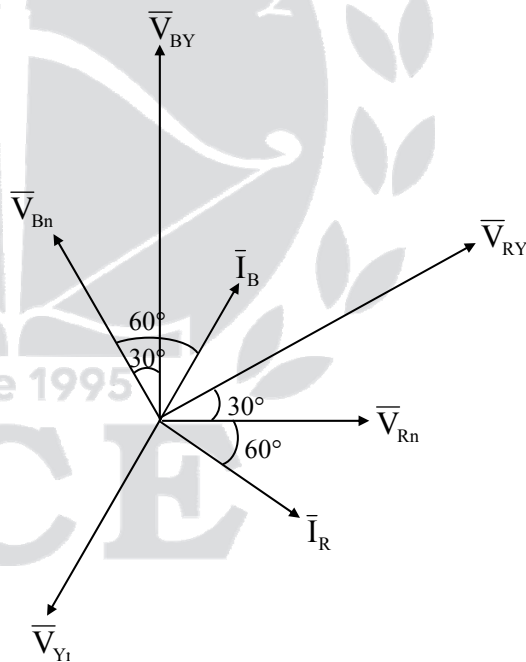So $W_2 = 0$ and phasor diagrams for other two are as follows



$$W_1 = V_{RY} I_R \cos(\text{angle between } \bar{V}_{RY} \text{ and } \bar{I}_R)$$

$$= 400 \times 5 \times \cos(90^\circ)$$

$$= 0 \text{ W}$$

$$W_3 = V_{BY} I_B \cos(\text{angle between } \bar{V}_{BY} \text{ and } \bar{I}_B)$$


$$= 400 \times 5 \times \cos(30^\circ)$$

$$= 400 \times 5 \times \frac{\sqrt{3}}{2}$$

$$= 1732 \text{ W}$$

$$W_1 = 0, W_2 = 0, W_3 = 1732 \text{ W}$$

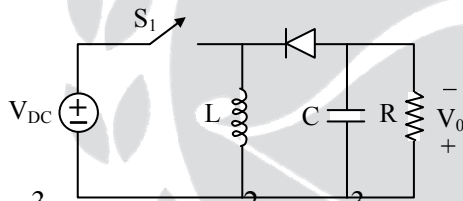50. The input voltage V_{DC} of the buck-boost converter shown below varies from 32 V to 72 V. Assume that all components are ideal, inductor current is continuous, and output voltage is ripple free. The range of duty ratio D of the converter for which the magnitude of the steady-state output voltage remains constant at 48 V is



(a) $\frac{2}{5} \leq D \leq \frac{3}{5}$

(b) $\frac{2}{5} \leq D \leq \frac{3}{4}$

(c) $0 \leq D \leq 1$

(d) $\frac{1}{3} \leq D \leq \frac{2}{3}$

50. **Ans: (a)**

Sol:

In Buck boost converter, $V_o = \frac{D}{1-D} V_{dc}$


When $V_{dc} = 32 \text{ V}$, $\frac{D}{1-D} = \frac{48}{32} \Rightarrow D = \frac{3}{5} = 0.6$

When $V_{dc} = 72 \text{ V}$, $\frac{D}{1-D} = \frac{48}{72} \Rightarrow D = \frac{2}{5} = 0.4$

\therefore The range of D will be $\frac{2}{5} < D < \frac{3}{5}$ or $0.4 < D < 0.6$

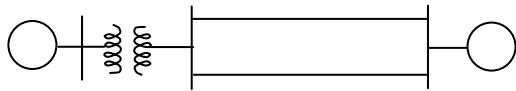51. The figure shows the single line diagram of a power system with a double circuit transmission line. The expression for electrical power is $1.5 \sin \delta$, where δ is the rotor angle. The system is operating at the stable equilibrium point with mechanical power equal to 1 pu. If one of the transmission line circuits is removed, the maximum value of δ , as the rotor swings is 1.221 radian. If the expression

for electrical power with one transmission line circuit removed is $P_{\max} \sin\delta$, the value of P_{\max} , in pu is _____.



51. Ans: 1.22

Sol: $\delta_2 = \delta_m = 70$

With two lines


$$P_s = P_{e1} = P_{m1} \sin\delta_0$$

$$\delta_0 = \sin^{-1}\left(\frac{P_s}{P_{m1}}\right) = \sin^{-1}\left(\frac{1.0}{1.5}\right)$$

$$\delta_0 = 41.75^\circ = 0.728 \text{ rad}$$

$$\delta_m = 1.221 \text{ rad}$$

$$= 1.221 \times \frac{180}{3.14} = 70$$

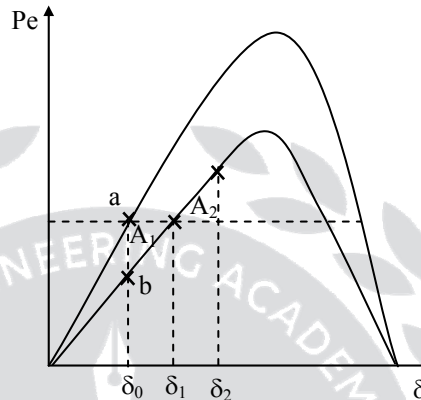

$$A_1 + A_2 = 0$$

$$\int_{\delta_0}^{\delta_1} (P_s - P_{e2}) d\delta + \int_{\delta_1}^{\delta_2} (P_s - P_{e2}) d\delta = 0$$

$$[P_s \delta + P_{m2} \cos \delta]_{\delta_0}^{\delta_1} + [P_s \delta + P_{m2} \cos \delta]_{\delta_1}^{\delta_2} = 0$$

$$P_s \delta_1 - P_s \delta_0 + P_{m2} \cos \delta_1 - P_{m2} \cos \delta_0 + P_s \delta_2 - P_s \delta_1 + P_{m2} \cos \delta_2 - P_{m2} \cos \delta_1 = 0$$

$$P_s (\delta_2 - \delta_0) + P_{m2} (\cos \delta_2 - \cos \delta_0) = 0$$

$$1.0 (1.221 - 0.728) + P_{m2} (\cos 70 - \cos 41.75) = 0$$

$$0.493 + P_{m2} (0.342 - 0.746) = 0$$

$$P_{m2} = \frac{0.493}{0.404} = 1.22$$

$$P_{m2} = 1.22$$

52. Let a causal LTI system be characterized by the following differential equation, with initial rest condition

$$\frac{d^2 y}{dt^2} + 7 \frac{dy}{dt} + 10y(t) = 4x(t) + 5 \frac{dx(t)}{dt}$$

Where, $x(t)$ and $y(t)$ are the input and output respectively. The impulse response of the system is ($u(t)$ is the unit step function)



(a) $2e^{-2t} u(t) - 7e^{-5t} u(t)$

(b) $-2e^{-2t} u(t) + 7e^{-5t} u(t)$

(c) $7e^{-2t} u(t) - 2e^{-5t} u(t)$

(d) $-7e^{-2t} u(t) + 2e^{-5t} u(t)$


52. Ans: (b)

Sol: Taking the laplace transform

$$\begin{aligned} \text{TF} &= \frac{Y(s)}{X(s)} = \frac{5s+4}{s^2+7s+10} \\ &= \frac{5s+4}{(s+2)(s+5)} = \frac{-2}{s+2} + \frac{7}{s+5} \end{aligned}$$


$$\text{IR} = \mathcal{L}^{-1} [\text{TF}] = -2e^{-2t} u(t) + 7e^{-5t} u(t)$$

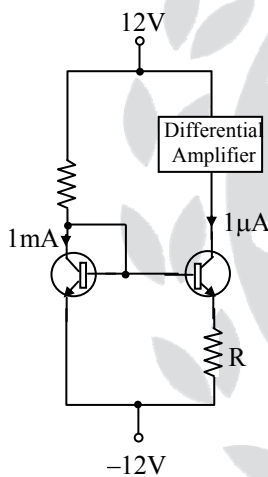53. The circuit shown in the figure uses matched transistors with a thermal voltage $V_T = 25 \text{ mV}$. The base currents of the transistors are negligible. The value of the resistance R in $\text{k}\Omega$ that is required to provide $1 \mu\text{A}$ bias current for the differential amplifier block shown is _____.



53. Ans: 172.7

Sol:

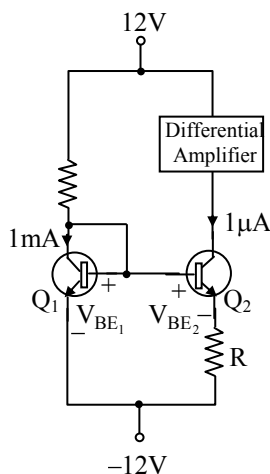

$$I_{C1} = 1\text{mA}, I_{C2} = 1\mu\text{A}$$

As B&C shorted, Transistor behaves as diode.



$$I_B = 0, I_C = I_E$$

Then,

$$I_{C_1} = I_0 \cdot e^{V_{BE_1}/V_T}$$

$$I_{C_2} = I_0 \cdot e^{V_{BE_2}/V_T}$$

$$\frac{I_{C_1}}{I_{C_2}} = \frac{I_0 \cdot e^{V_{BE_1}/V_T}}{I_0 \cdot e^{V_{BE_2}/V_T}}$$

$$\frac{I_{C_1}}{I_{C_2}} = e^{(V_{BE_1} - V_{BE_2})/V_T}$$

$$V_{BE_1} - V_{BE_2} = V_T \ln \left(\frac{I_{C_1}}{I_{C_2}} \right)$$

And $V_{BE_1} = V_{BE_2} + I_{C_2} \cdot R$

$$V_{BE_1} - V_{BE_2} = I_{C_2} \cdot R$$

$$R = \frac{V_{BE_1} - V_{BE_2}}{I_{C_2}} = \frac{V_T}{I_{C_2}} \ln \left(\frac{I_{C_1}}{I_{C_2}} \right)$$

$$R = \frac{25 \times 10^{-3}}{10^{-6}} \ln \left(\frac{10^{-3}}{10^{-6}} \right)$$

$$= 25 \times 10^3 \ln(10^3)$$

$$= 172.693 \text{ k}\Omega$$

$$R = 172.7 \text{ k}\Omega$$

54. A load is supplied by a 230 V, 50 Hz source. The active power P and the reactive power Q consumed by the load are such that $1 \text{ kW} \leq P \leq 2 \text{ kW}$ and $1 \text{ kVAR} \leq Q \leq 2 \text{ kVAR}$. A capacitor connected across the load for power factor correction generates 1 kVAR reactive power. The worst case power factor after power factor correction is

- (a) 0.447 lag (b) 0.707 lag
(c) 0.894 lag (d) 1

54. Ans: (b)

Sol: Worst power factor corresponding to P_{\min} and Q_{\max}

$$P_{\min} = 1 \text{ KW}$$

$$Q_{\max} = 2 \text{ KVAR}$$


$$Q_c = 1 \text{ KVAR}$$

$$P = 1 \text{ KW}, Q = 1 \text{ KVAR}$$

$$\text{Power factor} = \cos \left[\tan^{-1} \left(\frac{Q}{P} \right) \right] = 0.707 \text{ lag}$$

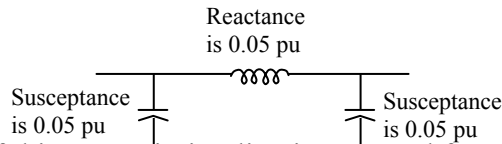55. The bus admittance matrix for a power system network is $\begin{bmatrix} -j39.9 & j20 & j20 \\ j20 & -j39.9 & j20 \\ j20 & j20 & -j39.9 \end{bmatrix}$ pu.

There is a transmission line connected between buses 1 and 3, which is represented by the circuit shown in figure.



If this transmission line is removed from service what is the modified bus admittance matrix?

- (a) $\begin{bmatrix} -j19.9 & j20 & 0 \\ j20 & -j39.9 & j20 \\ 0 & j20 & -j19.9 \end{bmatrix}$ pu
- (b) $\begin{bmatrix} -j39.95 & j20 & 0 \\ j20 & -j39.9 & j20 \\ 0 & j20 & -j39.95 \end{bmatrix}$ pu
- (c) $\begin{bmatrix} -j19.95 & j20 & 0 \\ j20 & -j39.9 & j20 \\ 0 & j20 & -j29.95 \end{bmatrix}$ pu
- (d) $\begin{bmatrix} -j19.95 & j20 & j20 \\ j20 & -j39.9 & j20 \\ j20 & j20 & -j19.95 \end{bmatrix}$ pu

55. Ans: (c)

Sol: When the line is removed from buses 1 and 3

$$z_{13} = j0.05$$

$$y_{13} = -j20$$

$$Y_{13} = Y_{31} = 0$$

$$\frac{y'_{13}}{2} = j0.05 \text{ - Half line shunt susceptance.}$$

$$Y_{11\text{mod}} = Y_{11\text{old}} - y_{13} - \frac{y'_{13}}{2} = -j39.9 - (-j20) - j0.05 = -j19.95$$

$$Y_{33\text{mod}} = Y_{33\text{old}} - y_{31} - \frac{y'_{13}}{2} = -j39.9 - (-j20) - j0.05 = -j19.95$$



HEARTY CONGRATULATIONS TO OUR GATE 2016 RANKERS

1 Ankita Jain CS	1 Agam Kumar Garg EC	1 Harshvardhan Sinha IN	2 K.K Srinivas EC
2 Arvind Biswal EE	3 Jayanta Deka EC	3 P. Shri Vastava PI	4 Sayeesh Tm ME
4 Ali Zafar Khan IN	4 Akash Ghosh PI	5 Amit Rawat EC	5 Raghav Chaudhary IN
5 Harshit Gupta PI	6 Pillai Muthuraj EC	6 Roopak Jain CE	6 Amarjeet Kumar ME
6 Prashant Singh J. IN	7 Rajat Chaudhary EE	7 B.krishna Murthy CS	7 Rajesh IN
8 K V S Sai Sushanth EC	8 Sudarshan EE	8 Sumit Kumar ME	8 Shubham Tiwari IN
9 Piyush Kumar EC	9 Sreyans Nahata CS	10 S. Chakraverty EC	10 Stuti Arya EE
10 Nilesh Agrawal CS	10 Saket Saurabh IN	10 Palak Bansal IN	10 Nagesh Verma PI




General Aptitude

01. The probability that a k-digit number does NOT contain the digits 0, 5, or 9 is
 (A) 0.3^k (B) 0.6^k
 (C) 0.7^k (D) 0.9^k

01. Ans: (C)

Sol:

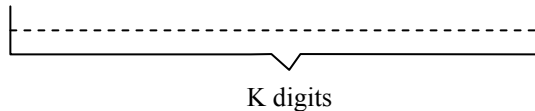

Each digit can be filled in 7 ways as 0, 5 and 9 is not allowed so, each of these places can be filled by 1, 2, 3, 4, 6, 7, 8.

So, required probability = $\left(\frac{7}{10}\right)^k = (0.7)^k$

02. Find the smallest number y such that $y \times 162$ is a perfect cube.
 (A) 24 (B) 27
 (C) 32 (D) 36

02. Ans: (D)

Sol: Factorisation of 162 is $2 \times 3 \times 3 \times 3 \times 3$

$y \times 162$ is a perfect cube

$y \times 2 \times 3 \times 3 \times 3 \times 3 = \text{Perfect cube}$

For perfect cube 2's and 3's are two more required each

(i.e.,) $2 \times 2 \times 2 \times 3 \times 3 \times 3 \times 3 \times 3$

$y = 2 \times 2 \times 3 \times 3 = 4 \times 9 = 36$

\therefore The smallest number of $y = 36$.

2	162
3	81
3	27
3	9
3	3

03. Research in the workplace reveals that people work for many reasons _____.
 (A) money beside (B) beside money
 (C) money besides (D) besides money


03. Ans: (D)

Sol: 'besides' means in addition to.

04. Rahul, Murali, Srinivas and Arul are seated around a square table. Rahul is sitting to the left of Murali. Srinivas is sitting to the right of Arul. Which of the following pairs are seated opposite each other?
- (A) Rahul and Murali (B) Srinivas and Arul
(C) Srinivas and Murali (D) Srinivas and Rahul

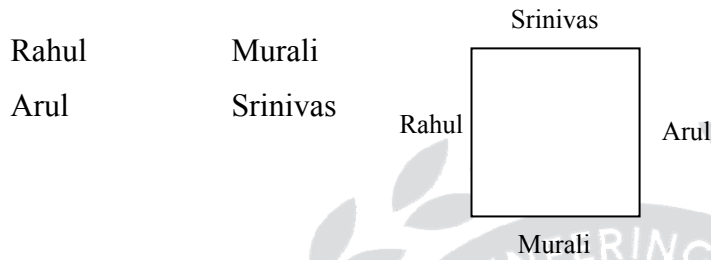04. Ans: (C)

Sol: From the given data, the following seated arrangement is possible around a square table.



∴ Srinivas and Murali are opposite to each other

05. After Rajendra Chola returned from his voyage to Indonesia, he _____ to visit the temple in Thanjavur.
- (A) was wishing (B) is wishing
(C) wished (D) had wished

05. Ans: (c)

Sol: If the main clause is in the past the past tense, the subordinate clause also should be in the past tense.

06. Arun, Gulab, Neel and Shweta must choose one shirt each from a pile of four shirts coloured red, pink, blue and white respectively. Arun dislikes the colour red and Shweta dislike the colour white. Gulab and Neel like all the colours. In how many different ways can they choose the shirts so that no one has a shirt with a colour he or she dislikes?
- (A) 21 (B) 18
(C) 16 (D) 14

06. Ans; (D)

Sol: Persons are Arun, Gulab, Neel and Shweta shirt colours are red, pink, blue and while

- Arun dislike red colour means he like remaining three other colours
- Shweta dislike white colour means he like remaining three other colours
- Gulab and Neel are likes all the four colours

∴ The total Number of ways to choose shifts = 3 + 3 + 4 + 4 = 14

07. Six people are seated around a circular table. There are at least two men and two women. There are at least three right-handed persons. Every woman has a left-handed person to her immediate right. None of the women are right-handed. The number of women at the table is
- (A) 2 (B) 3
(C) 4 (D) Cannot be determined

07. Ans: (A)

Sol: The total Number of peoples are sitting around a circular table is 6, in which atleast 2 men, atleast 2 women and atleast three right handed persons are compulsory. From this data, the following circular form is possible.


M = Male

W = Women

L = Left hand

R = Right hand

∴ The number of women on the table is 2.

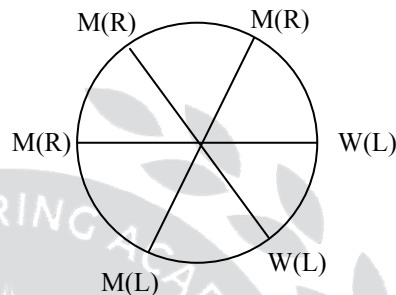


08. “The hold of the nationalist imagination on our colonial past is such that anything inadequately or improperly nationalist is just not history.”
- Which of the following statements best reflects the author’s opinion?
- (A) Nationalists are highly imaginative
(B) History is viewed through the filter of nationalism
(C) Our colonial past never happened
(D) Nationalism has to be both adequately and properly imagined

08. Ans: (B)

Sol: To refer is to reach an opinion. The right opinion of the author is ‘History is viewed through the filter of nationalism’ so (B) is the right opinion of the author. The key words in the statement are ‘history and nationalist imagination’.

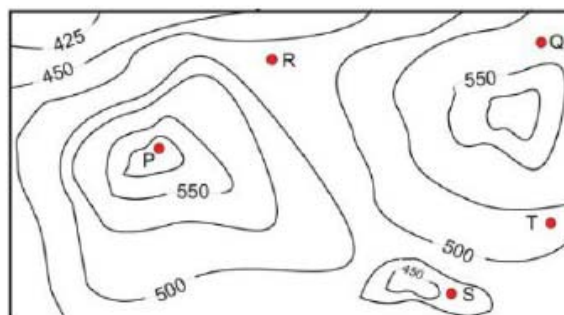09. A contour line joins locations having the same height above the mean sea level. The following is a contour plot of a geographical region. Contour lines are shown at 25m intervals in this plot. If in a flood the water level rises to 525 m, which of the villages P, Q, R, S, T get submerged?





(A) P, Q

(B) P, Q, T

(C) R, S, T

(D) Q, R, S

09. Ans: (C)

Sol: The given contour is a hill station, the peak point of this hill station is P, it is under a contour of 550. At floods, the water level is 525 m. So, the village of R, S and T are under a contour of 500. Therefore these villages are submerged.

10. The expression $\frac{(x+y)-|x-y|}{2}$ is equal to

(A) the maximum of x and y

(B) the minimum of x and y

(C) 1

(D) none of the above

10. Ans: (B)

Sol: $\frac{(x+y)+|x-y|}{2}$ (i)

$|x-y| = \pm(x-y)$, if $(x-y)$ when $x > y$

if $-(x-y) = (y-x)$ when $y > x$

$$\frac{(x+y)+(x-y)}{2} = \frac{x+y-x+y}{2}$$

$$= \frac{2y}{2} = y$$

= minimum of (x, y)

as $(x > y)$

$$\frac{(x+y)+(y-x)}{2} = \frac{x+y-y-x}{2}$$

$$= \frac{2x}{2} = x$$

= minimum of (x, y)

as $x < y$

∴ Option (B) is correct.



ACE

Engineering Academy
Leading Institute for ESE/GATE/PSUs



To win the race join ACE

HEARTY CONGRATULATIONS TO OUR ESE 2016 RANKERS

1 ME Mohammad Idul Ahmed	1 E&T Naveen Bhushan Sharma	2 E&T Amit Rawat	2 EE Bhallamudi Venkatesh	2 CE Bivek Joishi
2 ME Gaush Alam	3 E&T Aswathy Sivanandan	3 EE Tanuj Kumar Sharma	3 ME Chirag Srivastav	4 EE Varsha Shukla
4 CE Adarsh Rishi Srivastav	4 E&T Thaduri Naveen	5 E&T Vinit Ranjan	5 EE Ashish Verma	6 E&T Harshit Jain
6 EE Mufeed Khan	6 CE Nitish Garg	7 E&T Akash Chhikara	8 E&T Vivek Jain	8 EE Sk Taushifur Rehman
8 CE Amrit Anand	8 ME JGMV Pramod	9 E&T Jadugurta Narayanarao	9 EE Arvind Biswal	9 CE Avdresh Meena
9 ME Gaurav Kant	10 E&T Prabhakar Sinha	10 EE Gaurav Tyagi	10 CE Himanshu Tiwari	