



ACE Engineering Academy



Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Bengaluru | Lucknow | Patna | Chennai | Vijayawada | Visakhapatnam | Tirupati | Kukatpally | Kolkata

H.O: 204, II Floor, Rahman Plaza, Opp. Methodist School, Abids, Hyderabad-500001,
Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437


ESE- 2018 (Prelims) - Offline Test Series **Test- 9**
ELECTRONICS & TELECOMMUNICATION ENGINEERING

**SUBJECT: MATERIAL SCIENCE + NETWORK THEORY
SOLUTIONS**

01. Ans: (a)

Sol: The dots indicate that when current entering the dotted terminal of one coil, voltage induced is positive at the dotted terminal of other coil.

Given circuit,

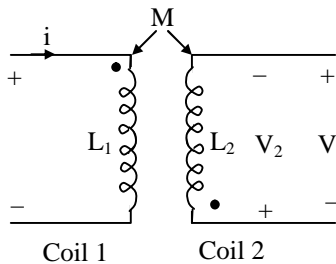

Here current entering the dotted terminal of coil 1.


⇒ induced voltage is positive at the dotted terminal of coil2.

$$\therefore V_2 = M \frac{di}{dt}$$

$$\text{But, } V = -V_2 = -M \frac{di}{dt}$$

02. Ans: (c)

Sol: Given circuit,

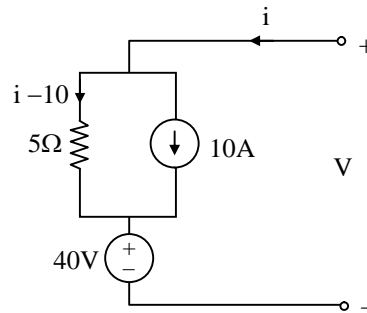


Applying KVL,

$$\Rightarrow -V + 5(I - 10) + 40 = 0$$

$$\Rightarrow V = 5i - 10$$

03. Ans: (c)

Sol: Given graph

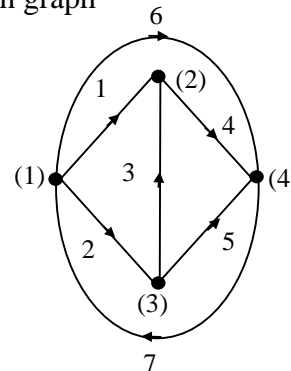



Number of possible trees = $|[A_r][A_r]^T|$

Where,

$[A_r]$ is the reduced incidence matrix

Incidence matrix, for the given graph is

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} (1) \\ (2) \\ (3) \\ (4) \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & -1 & 1 \end{bmatrix} \end{matrix}$$

By taking the (4) node as reference,

Reduced incidence matrix,

$$[A_r] = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \end{bmatrix}$$

$[A_r][A_r]^T$

$$= \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ -1 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 4 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$\therefore |[A_r][A_r]^T| = \begin{vmatrix} 4 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}$$

$$= 4(9 - 1) + 1(-3 - 1) - 1(1 + 3)$$

$$= 32 - 4 - 4 = 24$$

\therefore Number of possible trees = 24

04. Ans: (a)

Sol: Given networks,

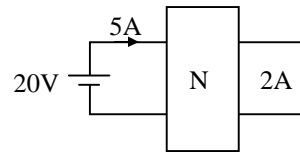


Fig.1


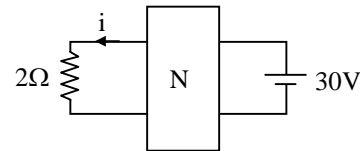


Fig.2

Applying reciprocity theorem to Fig (1)

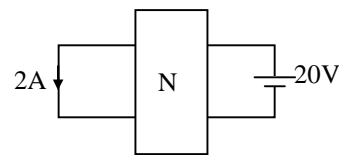

By using linearity principle,

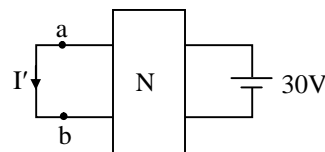


Fig.3

$$I' = \frac{30}{20} \times 2 = 3 \text{ A}$$

With respect to the terminals a and b the short circuit current $I_{SC} = I' = 3 \text{ A}$

Similarly with respect to the terminals a and b the Norton's equivalent resistance R_N is

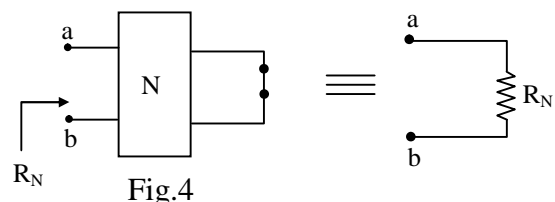
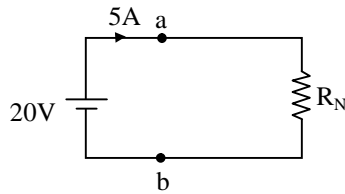


Fig.4

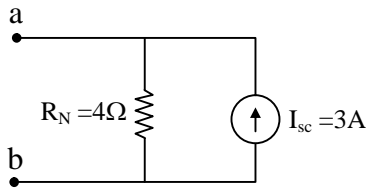


Fig (1) is the energized version of Fig. (4)




$$\Rightarrow R_N = \frac{20}{5} = 4 \Omega$$

The Norton's equivalent of Fig. (3) with respect to terminals a and b is



Then the Fig. (2) becomes

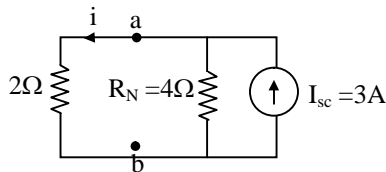


$$\Rightarrow i = I_{sc} \times \frac{4}{2+4}$$


$$\Rightarrow i = 3 \times \frac{4}{6} = 2 \text{ A}$$

05. Ans: (a)

Sol: Given network,

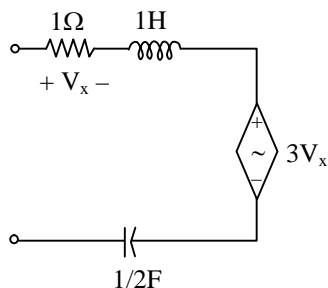

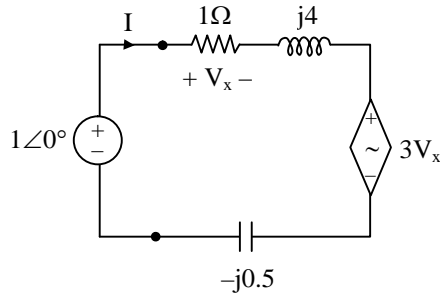Assume a voltage source of value $1 \angle 0^\circ$ having a frequency of 4 rad/sec is applied across the circuit then



$$\frac{V_x}{1} = I \Rightarrow I = V_x$$

Applying KVL in the loop,

$$\Rightarrow -1 \angle 0^\circ + V_x + j3.5I + 3V_x = 0$$


$$\Rightarrow -1 \angle 0^\circ + I + j3.5I + 3I = 0$$

$$\Rightarrow I = \frac{1 \angle 0^\circ}{4 + j3.5} = 0.1881 \angle -41.185^\circ \text{ A}$$

$$\therefore \text{Circuit power factor} = \cos(41.185) = 0.7525 \text{ lagging}$$

06. Ans: (a)


Sol: Given network,

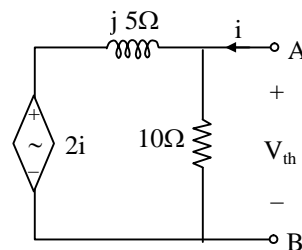

When A and B terminals are open circuited

$$\Rightarrow i = 0$$

Then the equivalent network becomes

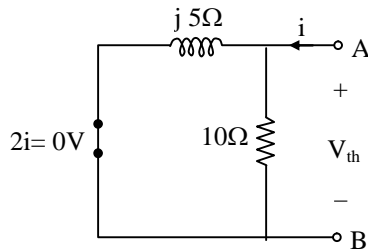


As there is no source to drive the above circuit

$$\Rightarrow V_{th} = 0V$$

07. Ans: (b)


Sol: Given network,

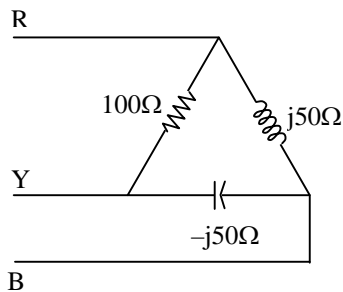

Here the power is consumed only in the 100Ω resistor and its value is

$$P_D = \frac{V_{RY}^2}{100} \dots\dots (1)$$

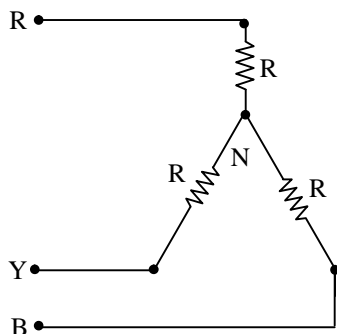Now connect a balanced star load, each of resistance value R as shown below



$$\text{Power consumed } P_s = 3 \frac{V_{RN}^2}{R}$$

$$P_s = \frac{(\sqrt{3}V_{RN})^2}{R} = \frac{V_{RY}^2}{R} \dots\dots (2)$$


$$\text{As } (1) = (2)$$

$$\Rightarrow \frac{V_{RY}^2}{100} = \frac{V_{RY}^2}{R}$$


$$\Rightarrow R = 100\Omega$$

08. Ans: (d)

Sol: Given network,

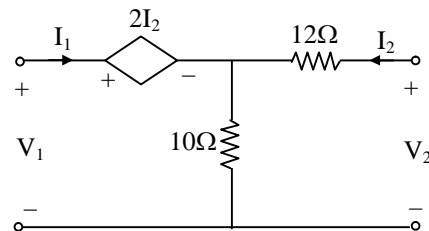

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

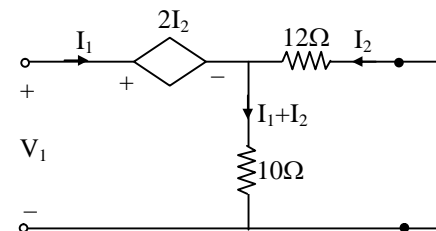

Applying KVL,

$$\Rightarrow -10(I_1+I_2) - 12I_2 = 0 \Rightarrow -10I_1 = 22I_2$$

$$\Rightarrow \frac{I_1}{-I_2} = 2.2$$

$$\therefore D = 2.2$$

Pre GATE-2018

COMPUTER BASED TEST


Date of Exam : 20th Jan 2018

Last Date To Apply : 05th Jan 2018

www.aceenggacademy.com

09. Ans: (a)

Sol: Given network,

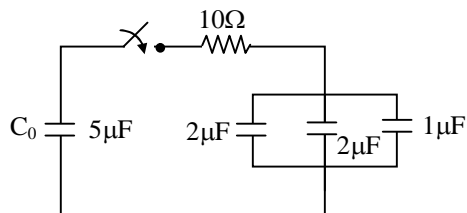


Initial charge in $C_0 = 500\mu\text{C}$


\Rightarrow Initial voltage across capacitor C_0 is

$$V_0 = \frac{q}{C_0} = \frac{500\mu}{5\mu} = 100\text{V}$$

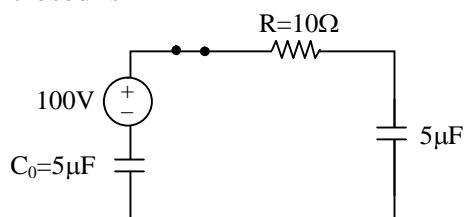The equivalent circuit after the switch is closed is



Convert into Laplace domain

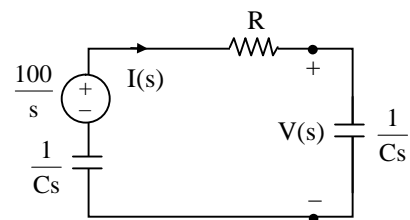

$$\Rightarrow I(s) = \frac{100/s}{R + \frac{2}{Cs}}$$

$$I(s) = \frac{100}{R \left(s + \frac{2}{RC} \right)}$$

$$\text{and } V(s) = \frac{1}{Cs} I(s)$$

$$= \frac{1}{Cs} \cdot \frac{100}{R \left(s + \frac{2}{RC} \right)}$$




$$\begin{aligned} \text{Steady state value of } v(t) \text{ is } & \lim_{s \rightarrow 0} sV(s) \\ &= \lim_{s \rightarrow 0} s \cdot \frac{100}{s(RCs + 2)} \\ &= 50V \end{aligned}$$

∴ Steady state voltage across $1\mu\text{F}$ capacitor = 50V


$$\begin{aligned} \therefore \text{Charge in the } 1\mu\text{F capacitor } q &= CV \\ &= 1\mu \times 50 \\ &= 50 \mu\text{C} \end{aligned}$$

10. Ans: (c)

Sol: Given network

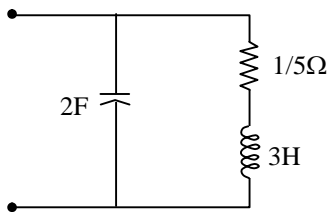


The dual of the above network is

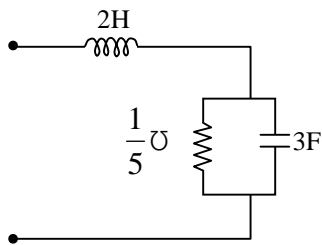

11. Ans: (b)


Sol: The wave form is as shown below

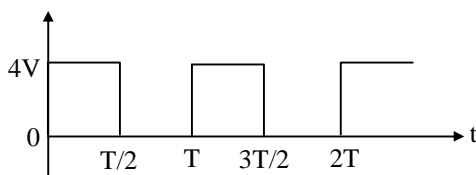




$$\begin{aligned} V_{\text{rms}}^2 &= \frac{1}{T} \int_0^{T/2} (4)^2 dt \\ \Rightarrow V_{\text{rms}}^2 &= \frac{1}{T} \times 16 \times T/2 = 8 \\ \Rightarrow V_{\text{rms}} &= 2\sqrt{2}V \end{aligned}$$

12. Ans: (b)

Sol: Given circuit

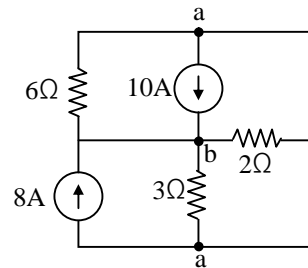

The above circuit can be redrawn as

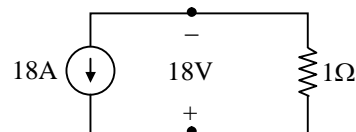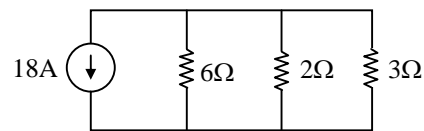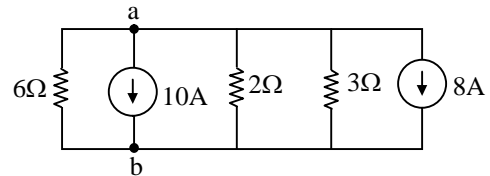

$$\begin{aligned} \Rightarrow \text{Total power delivered by the sources} \\ &= 18 \times 18 = 324W \end{aligned}$$



13. Ans: (d)

Sol: At the cut off frequency $I = \frac{I_m}{\sqrt{2}}$

$$\Rightarrow \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{V}{\sqrt{2}R}$$

$$\Rightarrow \left(\omega L - \frac{1}{\omega C}\right)^2 = R^2 \Rightarrow \left(\omega L - \frac{1}{\omega C}\right) = \pm R$$

At the lower cut off frequency ω_1 ,


$$\omega_1 L < \frac{1}{\omega_1 C}$$

$$\therefore \omega_1 L - \frac{1}{\omega_1 C} = -R$$

$$\Rightarrow \text{Net reactance} = -R$$

14. Ans: (a)

Sol:

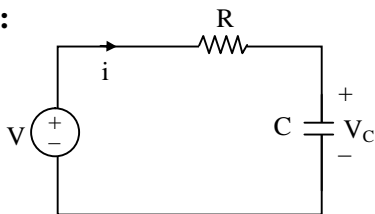

Under steady state condition $V_c = V = 100V$

$$\text{And } i(t) = \frac{V}{R} e^{-t/RC}$$

Energy dissipated by the resistor

$$E_R = \int_0^{\infty} i^2 R \, dt$$

$$E_R = \int_0^{\infty} \frac{V^2}{R^2} e^{-2t/RC} \cdot R \, dt$$

$$= \frac{V^2}{R} \left[\frac{e^{-2t/RC}}{-2/RC} \right]_0^{\infty}$$

$$= \frac{-1}{2} CV^2 [0 - 1] = \frac{1}{2} CV^2$$

$$\Rightarrow E_R = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 1 \times 10^{-6} \times (100)^2 = 5mJ$$

15. Ans: (a)

Sol: We know, when two, 2-port networks are connected in parallel, their individual Y-parameters gets added.

\therefore First, we need to convert given ABCD parameters to Y-parameters.

For 2-port network

Y-parameters are

$$\left. \begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned} \right\} (1)$$

ABCD parameters

$$\left. \begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned} \right\} (2)$$

Make $V_2 = 0$ to find Y_{11} & Y_{21}

$$\text{Equation (2) becomes } V_1 = -BI_2$$

$$I_1 = -DI_2$$

$$\therefore Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{D}{B} \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-1}{B}$$



Similarly, $V_1 = 0$, to find Y_{12} & Y_{22}

\therefore From equation (2) $AV_2 = BI_2$

$$\Rightarrow V_2 = \frac{B}{A} I_2$$

$$I_1 = CV_2 - DI_2$$

$$I_1 = C \frac{B}{A} I_2 - DI_2 = \frac{CB - DA}{A} I_2$$

$$I_1 = \frac{BC - AD}{A} I_2$$

$$\text{But } I_2 = \frac{A}{B} V_2$$

$$\Rightarrow I_1 = \frac{BC - AD}{A} \frac{A}{B} V_2$$

$$\Rightarrow I_1 = \left(\frac{BC - AD}{B} \right) V_2 \dots\dots(3)$$

$$\therefore Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{BC - AD}{B}$$

And $I_1 = \frac{BC - AD}{B} I_2$ put this value in


equation (3)

$$\frac{BC - AD}{A} I_2 = \frac{BC - AD}{B} V_2$$

$$I_2 = \frac{A}{B} V_2 \Rightarrow Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{A}{B}$$

Y-parameter matrix in terms of ABCD parameter is
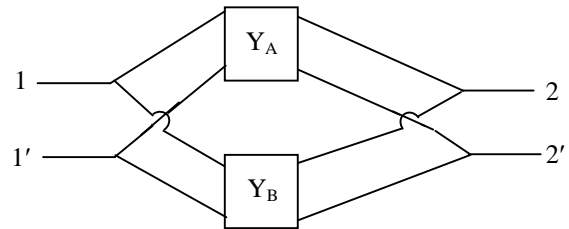
$$Y_T = \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$$



$$Y_T \text{ or } Y_{eq} = Y_A + Y_B$$

$$= \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} + \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$$

$$Y_T \text{ or } Y_{eq} = \begin{bmatrix} 2\frac{D}{B} & 2\frac{(BC - AD)}{B} \\ -\frac{2}{B} & \frac{2A}{B} \end{bmatrix}$$

Now, again connect back to ABCD parameters

$$\left. \begin{aligned} I_1 &= \frac{2D}{B} V_1 + 2\frac{(BC - AD)}{B} V_2 \\ I_2 &= -\frac{2}{B} V_1 + \frac{2A}{B} V_2 \end{aligned} \right\} (4)$$

$$\text{Make } V_2 = 0 \quad I_1 = \frac{2D}{B} V_1$$

$$I_2 = -\frac{2}{B} V_1$$



$$B_T = -\frac{V_1}{I_2} \Big|_{V_2=0} = \frac{B}{2} = 0.5B$$

$$D_T = -\frac{I_1}{I_2} \Big|_{V_2=0} = \frac{2D/B}{2/B} = D$$

Make $I_2 = 0$, equation (4) becomes

$$V_1 = AV_2 \text{ \& } I_1 = \frac{2D}{B}V_1 + 2\frac{(BC-AD)}{B}V_2$$

$$= \frac{2D}{B}AV_2 + \frac{(2BC-2AD)}{B}V_2$$

$$= \left(\frac{2AD+2BC-2AD}{B} \right) V_2$$

$$I_1 = 2CV_2$$

$$\therefore A_T = \frac{V_1}{V_2} = A$$

$$C_T = \frac{I_1}{V_2} = 2C$$

$$[T] = \begin{bmatrix} A_T & B_T \\ C_T & D_T \end{bmatrix} = \begin{bmatrix} A & 0.5B \\ 2C & D \end{bmatrix}$$



ESE | GATE - 2019

LONG TERM BATCHES

EC | EE | ME | CE | CS | IN | PI

Start Early, Gain Surely



Pioneer to
Leader



Dedicated
Service



Experienced Faculty
from Central Pool

Admissions are open at all our centers

H. O. : Hyderabad : Ph : 040-23234418,19,20

Bangalore
9341299966

Kukatpally
040-6597 4465

Delhi
9205282121

Bhopal
0755-2554512

Pune
020-25535950

Bhubaneswar
0674-2540340

Lucknow
808199966

Patna
9308699966

Chennai
044-42123289

Vijayawada
0866-2490001

Vishakapatnam
0891-6616001

Tirupathi
0877-2244388

Kolkata
8297899966




16. Ans: (c)

Sol: Given network function

$$F(s) = \frac{(s+2)}{(s+1)(s+3)}$$

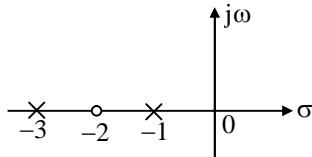The pole zero pattern for the above network function is as shown below



As we can see from above pole zero plot poles and zeros alternate on negative real axis and nearest to the origin is a pole.


∴ It can be realized as RC impedance function or RL admittance function.

17. Ans: (a)

Sol: Assume the circuit is in steady state before the switch opens.

⇒ The inductor will act as short circuit.

Then the circuit at $t = 0^-$ is

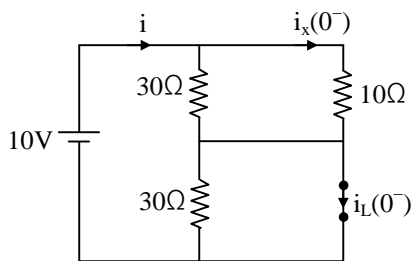

Equivalent resistance seen by the 10V voltage source is $= 30 \parallel 10$


$$= \frac{30 \times 10}{40} = 7.5 \Omega$$

$$\Rightarrow i = \frac{10}{7.5} = \frac{4}{3} \text{ A}$$


$$\begin{aligned} \therefore i_x(0^-) &= i \times \frac{30}{40} \\ &= \frac{4}{3} \times \frac{3}{4} = 1 \text{ A} \end{aligned}$$

18. Ans: (a)

$$\text{Sol: } Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

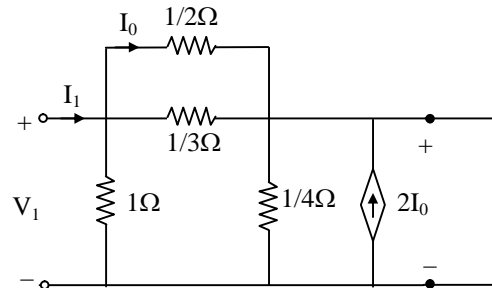

The equivalent network becomes

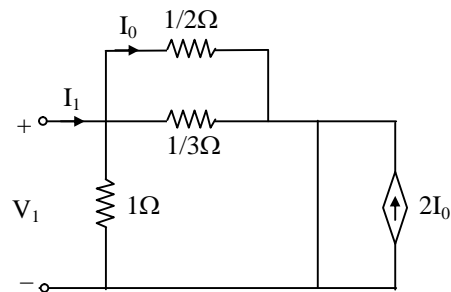

Equivalent resistance seen by the port 1 is


$$= 1 \parallel \frac{1}{2} \parallel \frac{1}{3} = \frac{1}{6} \Omega$$

$$\Rightarrow V_1 = \frac{1}{6} I_1 \Rightarrow \frac{I_1}{V_1} = 6 \text{ } \Omega$$

$$\Rightarrow Y_{11} = 6 \text{ } \Omega$$

19. Ans: (d)

Sol: Given network

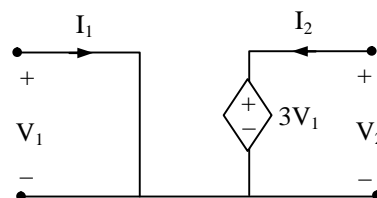

As we are unable to write I_1 in terms of V_1 and V_2 therefore Y parameters doesn't exist.




20. Ans: (a)

Sol: For parallel resonant circuit,

$$\text{Admittance, } Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$\text{Susceptance } B = \omega C - \frac{1}{\omega L}$$

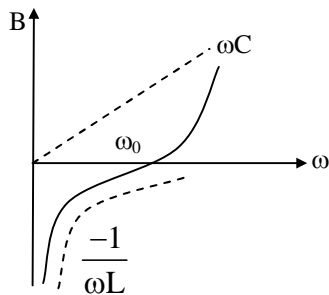
The plot of susceptance is as shown below



21. Ans: (c)

Sol: Assume the circuit is in steady state before the switch is changed from a to b
 \Rightarrow inductor will acts as short circuit.

Then the circuit is

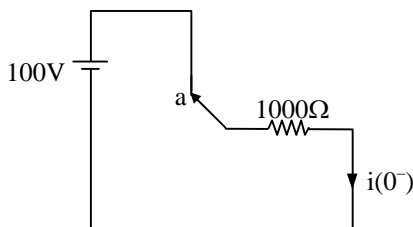


$$\Rightarrow i(0^-) = \frac{100}{1000} = 0.1 \text{ A}$$

And initial voltage across the capacitor is

$$V_C(0^-) = 0 \text{ V}$$

At $t = 0^+$ the equivalent circuit is

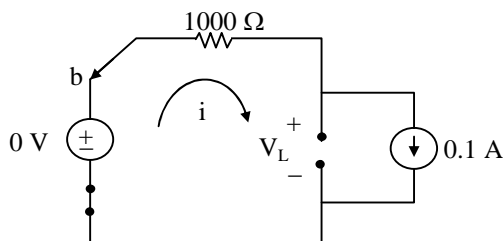

$$\Rightarrow V_L \text{ at } t = 0^+ \text{ is } = -100$$

$$\Rightarrow L \frac{di}{dt} = -100 \Rightarrow \frac{di}{dt} = -100$$

$$\therefore \frac{di}{dt} \text{ at } t = 0^+ \text{ is } = -100 \text{ A/sec.}$$

22. Ans: (b)

Sol: For


- RC driving point impedance function
- RC driving point admittance function
- RL driving point impedance function
- RL driving point admittance function

Poles and zeros should alternate only on negative real axis

23. Ans: (b)

Sol: Given $Z(S) = \frac{(s+1)(s+3)}{s(s+2)}$

The pole zero pattern is as shown below

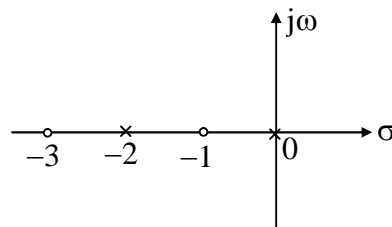


As we can see the poles and zeros alternate on negative real axis and nearest to the origin is a pole.

\therefore It can be realized as RC driving point impedance

$$Z(S) = 1 + \frac{2s+3}{s(s+2)} = 1 + \frac{3/2}{s} + \frac{1/2}{s+2}$$



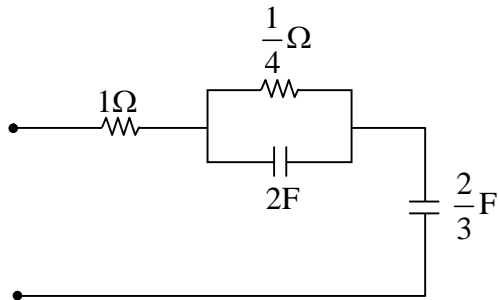
The network for the above impedance function is as shown below




∴ Two energy storage elements are present.

24. Ans: (d)

Sol: At $t=0^+$ the circuit is

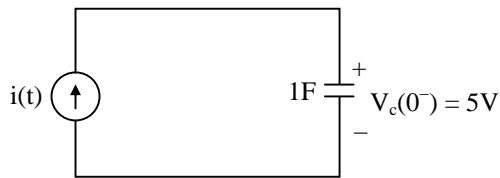

Convert into Laplace domain

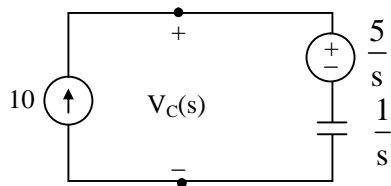

$$\Rightarrow V_C(s) = \frac{5}{s} + \frac{1}{s} \times 10$$

$$= \frac{15}{s}$$


$$\Rightarrow v_C(t) = 15 u(t)$$

$$\text{At } t=0^+ \Rightarrow u(t=0^+) = 1$$

$$\Rightarrow v_C(0^+) = 15 \text{ V}$$

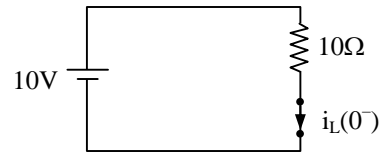
25. Ans: (b)

Sol: The equivalent network at $t=0^-$ is



$$\Rightarrow i_L(0^-) = \frac{10}{10} = 1 \text{ A}$$


At $t=0^+$ the network is

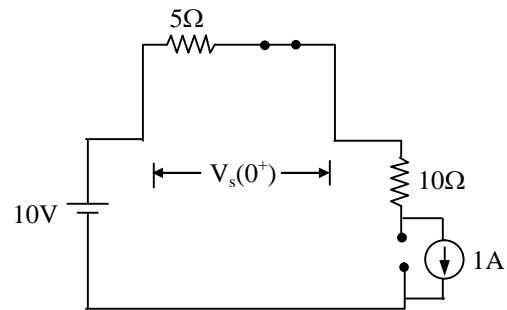

$$\Rightarrow V_S(t=0^+) = 5 \times 1 = 5 \text{ V}$$


26. Ans: (d)

Sol: At $t=0^-$ the network is

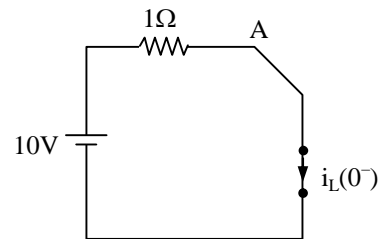


$$\Rightarrow i_L(0^-) = \frac{10}{1} = 10 \text{ A}$$

At $t=0^+$ the network is

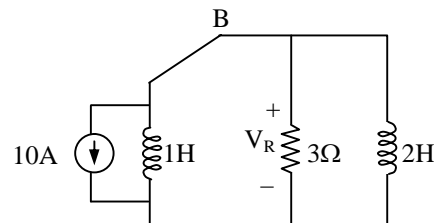



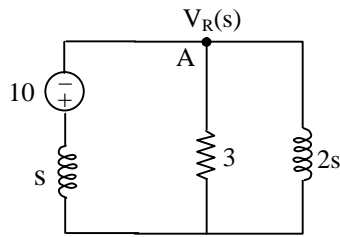Convert the above circuit into Laplace domain



Applying KCL at node 'A'

$$\Rightarrow \frac{V_R(s) + 10}{s} + \frac{V_R(s)}{3} + \frac{V_R(s)}{2s} = 0$$

$$\Rightarrow V_R(s) \left[\frac{3}{2s} + \frac{1}{3} \right] = -\frac{10}{s}$$

$$\Rightarrow V_R(s) = \frac{-30}{s + \frac{9}{2}} \Rightarrow v_R(t) = -30 e^{-4.5t}$$

As $t \rightarrow \infty \Rightarrow V_R(t) = 0V$

27. Ans: (b)

Sol: The equivalent capacitance across a, b is calculated by simplifying the bridge circuit as shown in Fig. 1 to Fig. 5.

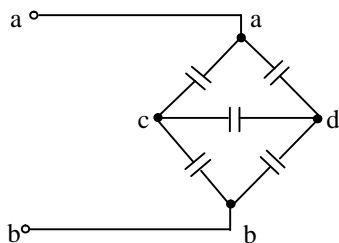


Fig. 1


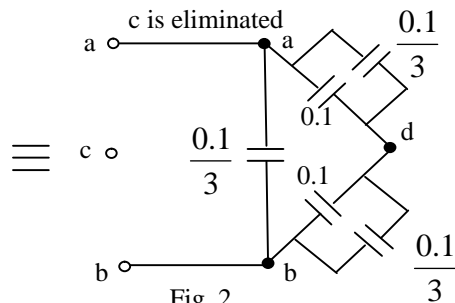


Fig. 2

Note: The bridge is balanced and the answer is easy to get.

28. Ans: (d)

Sol:

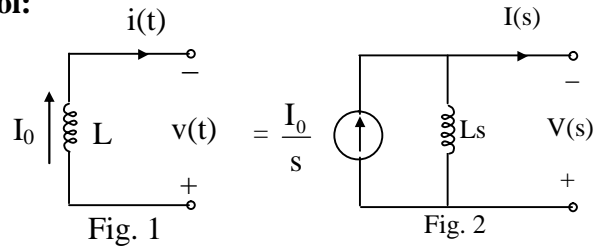

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt, \quad I(s) = \frac{I_0}{s} + \frac{1}{Ls} V(s)$$

The inductor in time domain and transform domain are shown in Fig.1 and Fig. 2.

29. Ans: (c)

Sol: $L = 3 \times 10^{-3} H,$

$$i(t) = \frac{10t}{2 \times 10^{-3}} = 5 \times 10^3 t A$$

$$\frac{di(t)}{dt} = 5 \times 10^3 A/s,$$

$$v(t) = L \frac{di(t)}{dt} = 15 V$$

$$p(t) = v(t) i(t) = 15 \times 5 \times 10^3 t W = 75000t$$

30. Ans: (a)

Sol: sub-network N_1 can be replaced by its Thevenin equivalent even if the sub-network N_2 contains a two-terminal element which is non-linear.

31. Ans: (c)

Sol: If a network has all linear elements except for a few non-linear ones, then superposition theorem may hold on careful selection of element values, source waveform and response.

Note: The reader may see this important statement and an example in comment (3), page 661, of Text Book "Basic Circuit Theory" by Desoer & Kuh.



32. Ans: (d)

Sol: The figure accompanying the question specifies voltage across C as in fig.1.

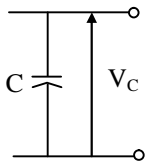
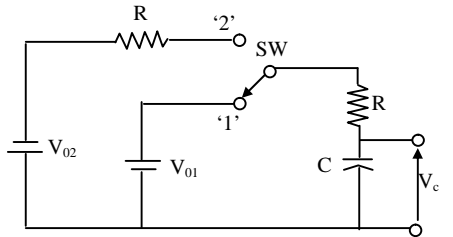


Fig: 1


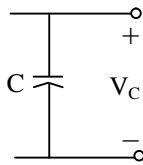


Fig: 2

Polarity of V_c is therefore specified as in fig.2.

At $t = 0^-$, V_c would have acquired a value of V_{01} volts.

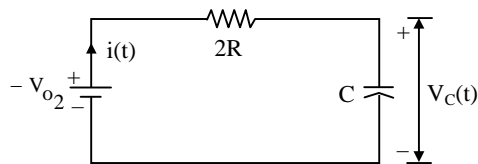For $t = 0^+$, the circuit can be redrawn as in fig.3.



$$V_c(t=0^-) = V_c(t=0^+) = V_{01}$$

Fig: 3

$$\text{KVL: } 2Ri + \frac{1}{C} \int_0^t i dt + V_{01} = -V_{02} \quad t \geq 0^+$$

$$\text{Solving, } i(t) = Ae^{-t/2RC}$$

$$\text{At } t = 0, 2R A + V_{01} = -V_{02}$$

$$\text{or } A = -\frac{V_{01} + V_{02}}{2R}$$

$$\text{thus } i(t) = -\frac{(V_{01} + V_{02})}{2R} e^{-t/2RC}$$

$$V_c(t) = \frac{1}{C} \int_0^t i dt + V_{01} = (V_{01} + V_{02}) [e^{-(t/2RC)} - 1] + V_{01}$$


Check: At $t = 0$; $V_c(t)$ must equal V_{01} , which it does.

At $t = \infty$, $V_c(t)$ must equal $-V_{02}$, which again it does.

Note: In the question if the polarity given for V_{02} is reversed, then (d) would be the answer.

33. Ans: (d)

Sol: In the circuit given below,

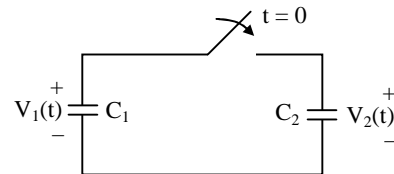


At $t = 0^-$; $V_1(t) = 12 \text{ V}$ and $V_2(t) = 0 \text{ V}$.

At $t = 0^+$ (immediately after the switch is closed) the two capacitances must acquire some common voltage. Since this means voltages across capacitances changing instantaneously, there must be an impulse current through the loop.

34. Ans: (b)

Sol:

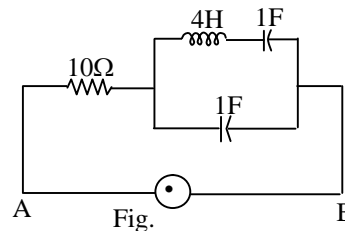

The given circuit is shown in Fig.

$$Z_{AB} = 10 + Z_1$$



$$\begin{aligned} \text{where, } Z_1 &= \left(\frac{-j}{\omega} \right) \parallel \left(j4\omega - \frac{j}{\omega} \right) \\ &= \frac{\left(\frac{-j}{\omega} \right) \left(j4\omega - \frac{j}{\omega} \right)}{\frac{-j}{\omega} + j4\omega - \frac{j}{\omega}} \\ &= \frac{4 - \frac{1}{\omega^2}}{j4\omega - \frac{j2}{\omega}} \end{aligned}$$


For circuit to be resonant i.e., $\omega^2 = \frac{1}{4}$

$$\omega = \frac{1}{2} = 0.5 \text{ rad/ sec}$$

$$\therefore \omega_{\text{resonance}} = 0.5 \text{ rad/sec}$$

35. Ans: (b)

Sol:

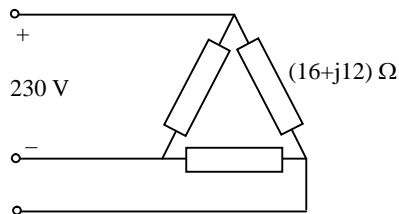

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$I_{\text{ph}} = \frac{230}{\sqrt{16^2 + 12^2}} = \frac{230}{20} = 11.5 \text{ A}$$

$$I_L = \sqrt{3} I_{\text{ph}} = 11.5(\sqrt{3}) = 19.91 \text{ A}$$

$$\cos \phi = \frac{R}{|Z|} = \frac{16}{\sqrt{16^2 + 12^2}} = \frac{16}{20} = \frac{4}{5} = 0.8$$

$$\begin{aligned} P &= \sqrt{3}(230)(19.91)(0.8) = 6348 \\ &= 6.34 \text{ kW} \end{aligned}$$

36. Ans: (a)

$$\begin{aligned} \text{Sol: Output voltage} &= t \times g \times p \\ &= 2 \times 10^{-3} \times 0.055 \times 1.25 \times 10^6 \\ &= 137.5 \text{ V} \end{aligned}$$

37. Ans: (a)

Sol: Ionic polarization takes place by displacement of cations and anions. It is independent of temperature

$$\alpha_i = \frac{e^2}{\omega^2 m}$$

Ionic Polarizability is inversely proportional to the square of natural frequency (ω)

38. Ans: (b)

$$\begin{aligned} \text{Sol: Polarization (P)} &= \epsilon_0(\epsilon_r - 1)E \\ &= 8.854 \times 10^{-12} \times (8 - 1) \times 10 \times 10^3 \\ &= 6.2 \times 10^{-7} \end{aligned}$$

39. Ans: (c)

40. Ans: (a)

41. Ans: (b)

$$\begin{aligned} \text{Sol: } \rho &= \frac{1}{ne\mu} \Rightarrow \mu = \frac{1}{ne\rho} \\ &= \frac{1}{6 \times 10^{28} \times 1.6 \times 10^{-19} \times 1.54 \times 10^{-8}} \\ &= 6.76 \times 10^{-3} \text{ m}^2/\text{V-s} \end{aligned}$$

GATE - 2018

ONLINE TEST SERIES

No. of Tests : 62

All tests will be available till
12th February 2018

ESE - 2018 PRELIMS

ONLINE TEST SERIES

No. of Tests : 44

All tests will be available till
07th January 2018

ISRO - 2017

ONLINE TEST SERIES

No. of Tests : 15

All tests will be available till
25th December 2017

★ HIGHLIGHTS ★

- Detailed solutions are available.
- **All India rank** will be given for each test.
- Comparison with all India toppers of **ACE** students.

www.aceenggacademy.com

testseries@aceenggacademy.com

42. Ans: (c)

$$\text{Sol: } H_C = H_0 \left[1 - \left(\frac{T}{T_C} \right)^2 \right]$$

$$1 \times 10^5 = 2 \times 10^5 \left[1 - \left(\frac{8}{T_C} \right)^2 \right]$$

$$\frac{1 \times 10^5}{2 \times 10^5} = 1 - \left(\frac{8}{T_C} \right)^2$$

$$\frac{1 \times 10^5}{2 \times 10^5} + \left(\frac{8}{T_C} \right)^2 = 1$$

$$\frac{64}{T_C^2} + 0.5 = 1 \Rightarrow T_C^2 = \frac{64}{0.5}$$

$$T_C = 11.31 \text{ K}$$

43. Ans: (b)

$$\text{Sol: } J_c = \frac{i_c}{A} = \frac{H_C \times 2\pi R}{\pi R^2} = \frac{2H_C}{R}$$

44. Ans: (a)

Sol: Based on F.London and H.London research, magnetic flux density is allowed by super conductor up to some layers from the surface.

London penetration depth: It is the depth from the surface of super conductor upto which flux density is decreased by 63%.

$$B = B_0 e^{-\frac{x}{\lambda_L}}$$

B = Flux density at a depth 'X'

B₀ = flux density at surface of super conductor

λ_L = London penetration depth

45. Ans: (d)

Sol: Hall angle $\tan \theta_H = \mu B = 0.041 \times 0.1 = 0.0041$

$$\theta_H = \tan^{-1}(0.0041)$$

$$\theta_H = 0.2349$$



46. Ans: (a)

47. Ans: (c)

Sol: Total magnetic moment = $N \times i \times A$

$$= 500 \times 20 \times 10^{-3} \times \pi (2 \times 10^{-2})^2$$

$$= 500 \times 20 \times 10^{-3} \times 4\pi \times 10^{-4}$$

$$= 4\pi \times 10^{-3} \text{ A-m}^2$$

48. Ans: (a)

Sol: Magnetic flux density (b) = $88 \times 10^{-4} \text{ Wb/m}^2$

Field strength (H) = 100 A/m

$$\mu_R = \frac{\mu}{\mu_0} = \frac{B}{H\mu_0} = \frac{88 \times 10^{-4}}{100 \times 4\pi \times 10^{-7}} = 70$$


49. Ans: (a)

Sol: The hysteresis loop of ferromagnetic material depends on

1. Temperature
2. Crystallographic imperfection
3. Cold working

50. Ans: (a)

Sol:

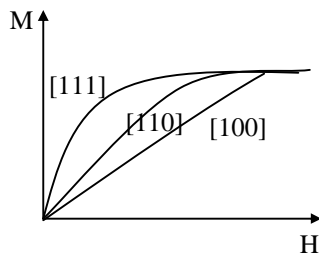

51. Ans: (b)

Sol: Magnetorheological materials has the ability to increase viscosity drastically with applied field.

52. Ans: (c)

53. Ans: (d)

54. Ans: (a)

Sol: Weiss-Domain Theory: Based on Weiss Domain theory in a domain all the dipoles are aligned in a particular direction. If the magnetic field is applied Domain growth takes place in the field direction and at higher field, inside domain dipole relation takes place.

55. Ans: (b)

Sol: Reason: The no. of atoms per unit cell in BCC Crystal = 2

The no. of atoms per unit cell in FCC crystal = 4 So, the difference is 4-2=2

56. Ans: (d)

Sol: Ga-As compound is a zinc blende structure

57. Ans: (b)

Sol: $\sqrt{2} a = 4R$

$$a = \frac{4R}{\sqrt{2}}$$

$$d_{111} = \frac{a}{\sqrt{h^2 + k^2 + l^2}}$$

$$= \frac{4(0.128 \times 10^{-9})}{\sqrt{2} \times \sqrt{1^2 + 1^2 + 1^2}} = 2 \text{ \AA}$$



58. Ans: (d)

Sol: X → 1 (-1, 2, ∞)
 Y → 2 $\left(\frac{-1}{1}, \frac{1}{2}, \frac{1}{\infty}\right) = (\bar{2}10)$
 Z → ∞

59. Ans: (d)

Sol: The bullet proof jacket is made up of aramid fiber reinforced polymer (AFRB) with reinforcement phase is Aramid and matrix phase is polymer.

60. Ans: (b)

61. Ans: (c)

62. Ans: (c)

63. Ans: (d)

Sol: The bonding in ceramics is predominantly ionic, it consists of anions and cations. The crystal structure of ceramics is influenced by the radius ratios of the ions. The coordination number depends on the radius of the bonding ions. Ceramics are classified according to their crystal structure as AX, AX₂, ABX₃ and AB₂X₄ types.

Examples under each type are given below:

- AX : NaCl, CsCl, ZnS
- AX₂: SiO₂, CaF₂, PuO₂, ThO₂
- ABX₃: BaTiO₃, SrZrO₃, SrSnO₃
- AB₂X₄: MgAl₂O₄, FeAl₂O₄

64. Ans: (c)

Sol: If the temperature of metal increases, the lattice vibration in the crystal structure increases. Hence collision frequency increases and relaxation time decreases. Due to that resistivity of metal increases.

65. Ans: (c)

Sol: Ceramics have high melting point and can with stand high temperature.

66. Ans: (b)

Sol: If the radius X = 0.155, a more stable configuration is possible with three anions bonding with cation. This form a stable structure only upto an X value of 0.225 for 0.155 < X < 0.225 the anions do not touch each other.

67. Ans: (a)

68. Ans: (a)


Sol: BaTiO₃ crystal is Ferroelectric material upto 120°C, due to non-centro symmetric (asymmetric) structure. But above 120°C it become centro-symmetric and hence it loses its ferroelectric character.

69. Ans: (b)

Sol: The antiferro magnetic material depends on Neel's law



$$\chi = \frac{C}{T - T_N}$$

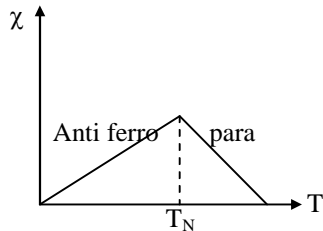

70. Ans: (d)

Sol: Impressed voltage $V = (100 - j90) \text{ V}$

Current $I = (3 - j4) \text{ A}$

Complex power, $S = V I^*$

$$= (100 - j90)(3 + j4)$$

$$= (660 + j130) \text{ VA}$$

\therefore Real power = 660 W \therefore Statement (I) is false.

71. Ans: (b)

72. Ans: (d)

Sol: Equivalent network obtained from $\Delta - Y$ transformation relation is valid for any frequency.
So statement (I) is false.

73. Ans: (b)

74. Ans: (b)

Sol: Conversion to equivalent T - NW and application of Thevenin's Theorem have no relation.

75. Ans: (b)

Sol: Poly crystal materials are stronger than single crystal material because they require more stresses to initiate slip and yielding. Poly crystalline materials there are many preferred planes and direction for different grains due to their random orientation.

GATE TOPPERS

GATE 2017

1 EC PRAMOD	1 ME SUDHEER	1 ME HASAN ASIF	1 EE SHIVAM SINGH	1 CE ABHIR BAKSH	1 CS DEVAL N. PATEL	1 IN NAVEEN	2 EC SREE KALYANI
2 CE PUNEET KHARNA	2 IN RAHUL MAHATO	2 IN SHUBHAM BANSAL	2 PI GAURAV BHARDWAJ	3 EC KARUNJ	3 EE RAVI TEJA	3 ME PRADIP BOBADE	3 CS RAVI SHANKAR
3 CE ANKUR TRIPATHI	4 EC SONU SHARMA	4 EE SARFRAJ NAWAZ	4 CE CHIRAG MITTAL	4 ME GAUSH ALAM	4 IN MONTI	4 PI Sanghamitra Adikari	5 IN VRAJESH SHAH
5 PI ANKIT TIWARI	6 EC LICHITA SAI LEPLU	6 CS MEGHASHAYAM	6 EE RAJESHVAR EBODY	6 IN RANESH KAMALLA	6 PI PINAL KUMAR RANA	7 IN RAHUL MEHRA	8 ME DIPRANSHU JHA
8 PI Nora Bhargava	9 EC Anand Upadhi	9 CS Nitin Kumar Singh	9 ME DHRUV KUMAR JHA	10 EC ANIL KAWAT	10 ME ANURAG GUPTA	10 EE SURAJ DASH	10 IN NISHA CHOPRA

ESE TOPPERS

ESE 2017

(CE)	(E&T)	(EE)	(ME)
1 CE NAMIT JAIN	2 E&T RICHANSHU CHAUDHARY	2 EE PRIYI KUMARI	3 ME SAURABH
2 CE PRAVESH SINGH	3 E&T ANJAN BHARGAVA	3 EE NANUJ KUMAR	4 ME ANIL KUMAR DW
3 CE ANBT	5 E&T ANHT GAUTAM	4 EE SNEHIL KUMAR SINGH	6 ME ANJAN GUPTA
6 CE RANABJI DINGRAJACH	6 E&T SUBIRANJAN MISHRA	5 EE NISHU KUMAR	7 ME DHRUV JHA
8 CE ADITYA SINGH	7 E&T DEVAJYOTIRAN KUMAR	6 EE DUSHYANT SINGH	9 ME ADHARAJ GUPTA
9 CE HRANGANSHU GAUTAM	8 E&T DEEPAI GOYAL	8 EE APOORVA GUPTA	
10 CE AYUSHI DUBEY	9 E&T ADARSH PRADIP SINGH	9 EE KIRAN BABU KOREKU	5 IN TOP 10 RANKS
7 IN TOP 10 RANKS	10 E&T LIMESH	7 IN TOP 10 RANKS	27 Ranks in Top 10 in ESE-2017
7 All India 1 st Rank in ESE.		8 IN TOP 10 RANKS and many more...	



ACE

Engineering Academy
Leading Institute for ESE/GATE/PSUs