



ACE

Engineering Academy



Hyderabad | Delhi | Bhopal | Pune | Bhubaneswar | Bengaluru | Lucknow | Patna | Chennai | Vijayawada | Visakhapatnam | Tirupati | Kukatpally | Kolkata

H.O: 204, II Floor, Rahman Plaza, Opp. Methodist School, Abids, Hyderabad-500001,

Ph: 040-23234418, 040-23234419, 040-23234420, 040 - 24750437

ESE- 2018 (Prelims) - Offline Test Series

Test-9


ELECTRICAL ENGINEERING

**SUBJECT: ELECTRIC CIRCUITS AND FIELDS + MATERIAL SCIENCE
SOLUTIONS**

01. Ans: (a)

Sol: The dots indicate that when current entering the dotted terminal of one coil, voltage induced is positive at the dotted terminal of other coil.

Given circuit,

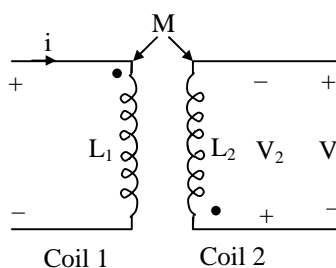

Here current entering the dotted terminal of coil 1.


\Rightarrow induced voltage is positive at the dotted terminal of coil 2.

$$\therefore V_2 = M \frac{di}{dt}$$

$$\text{But, } V = -V_2 = -M \frac{di}{dt}$$

02. Ans: (c)

Sol: Given circuit,

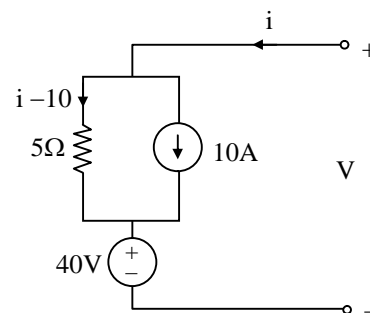

Applying KVL,


$$\Rightarrow -V + 5(I - 10) + 40 = 0$$

$$\Rightarrow V = 5i - 10$$



03. Ans: (c)

Sol: Given graph

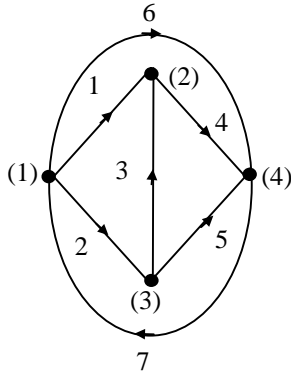

Number of possible trees = $|[A_r][A_r]^T|$

Where,

$[A_r]$ is the reduced incidence matrix

Incidence matrix, for the given graph is

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} (1) \\ (2) \\ (3) \\ (4) \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & -1 & 1 \end{bmatrix} \end{matrix}$$

By taking the (4) node as reference,

Reduced incidence matrix,

$$[A_r] = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \end{bmatrix}$$

$[A_r][A_r]^T$

$$= \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ -1 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 4 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$\therefore |[A_r][A_r]^T| = \begin{vmatrix} 4 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}$$

$$= 4(9 - 1) + 1(-3 - 1) - 1(1 + 3)$$

$$= 32 - 4 - 4 = 24$$

\therefore Number of possible trees = 24

04. Ans: (a)

Sol: Given networks,

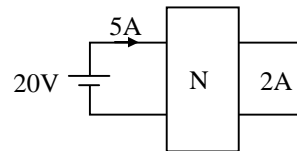


Fig.1


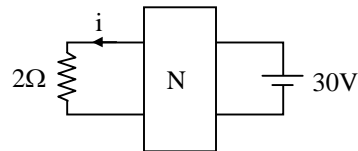


Fig.2

Applying reciprocity theorem to Fig (1)

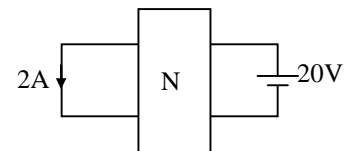

By using linearity principle,

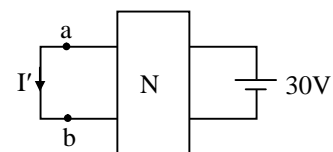


Fig.3



$$I' = \frac{30}{20} \times 2 = 3 \text{ A}$$

With respect to the terminals a and b the short circuit current $I_{SC} = I' = 3 \text{ A}$

Similarly with respect to the terminals a and b the Norton's equivalent resistance R_N is



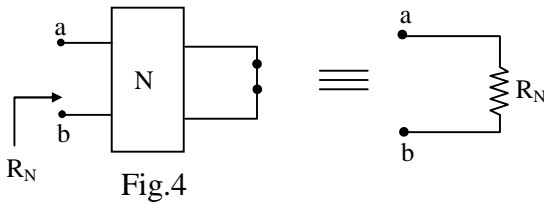


Fig (1) is the energized version of Fig. (4)

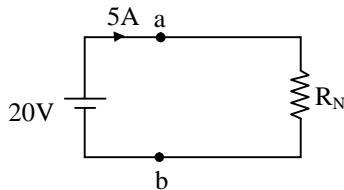


$$\Rightarrow R_N = \frac{20}{5} = 4 \Omega$$

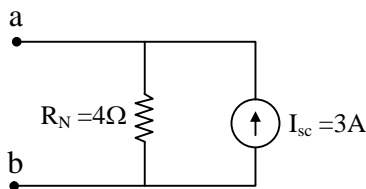The Norton's equivalent of Fig. (3) with respect to terminals a and b is



Then the Fig. (2) becomes

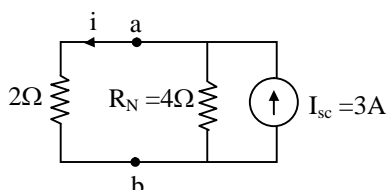


$$\Rightarrow i = I_{SC} \times \frac{4}{2+4}$$


$$\Rightarrow i = 3 \times \frac{4}{6} = 2 \text{ A}$$

05. Ans: (a)

Sol: Given network,

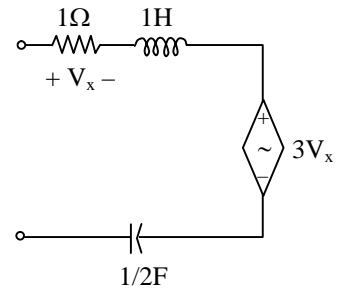

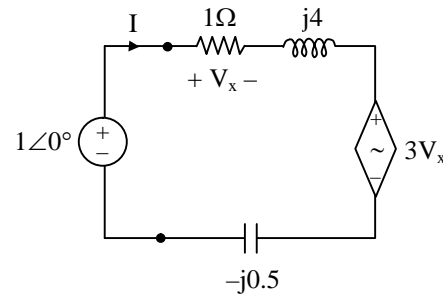Assume a voltage source of value $1 \angle 0^\circ$ having a frequency of 4 rad/sec is applied across the circuit then



$$\frac{V_x}{1} = I \Rightarrow I = V_x$$

Applying KVL in the loop,

$$\Rightarrow -1 \angle 0^\circ + V_x + j3.5I + 3V_x = 0$$

$$\Rightarrow -1 \angle 0^\circ + I + j3.5I + 3I = 0$$

$$\Rightarrow I = \frac{1 \angle 0^\circ}{4 + j3.5} = 0.1881 \angle -41.185^\circ \text{ A}$$

$$\therefore \text{Circuit power factor} = \cos(41.185)$$

$$= 0.7525 \text{ lagging}$$

Pre GATE-2018

COMPUTER BASED TEST


Date of Exam : 20th Jan 2018

Last Date To Apply : 05th Jan 2018

www.aceengacademy.com

06. Ans: (a)


Sol: Given network,

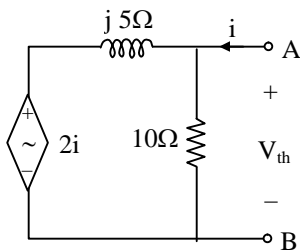

When A and B terminals are open circuited

$$\Rightarrow i = 0$$

Then the equivalent network becomes

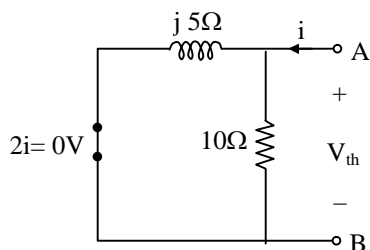


As there is no source to drive the above circuit

$$\Rightarrow V_{th} = 0V$$

07. Ans: (b)

Sol: Given network,

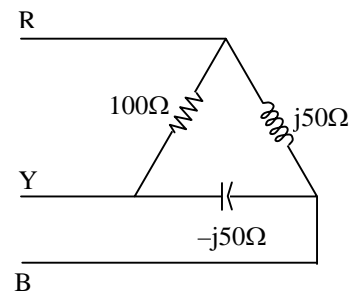


Here the power is consumed only in the 100Ω resistor and its value is

$$P_D = \frac{V_{RY}^2}{100} \dots \dots (1)$$



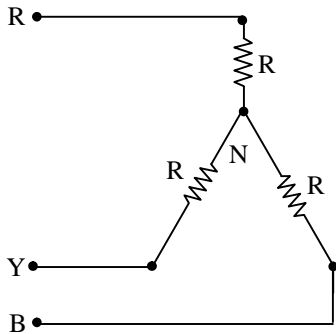Now connect a balanced star load, each of resistance value R as shown below



Power consumed $P_s = 3 \frac{V_{RN}^2}{R}$

$$P_s = \frac{(\sqrt{3}V_{RN})^2}{R} = \frac{V_{RY}^2}{R} \dots\dots (2)$$


As (1) = (2)

$$\Rightarrow \frac{V_{RY}^2}{100} = \frac{V_{RY}^2}{R}$$


$$\Rightarrow R = 100\Omega$$

08. Ans: (d)

Sol: Given network,

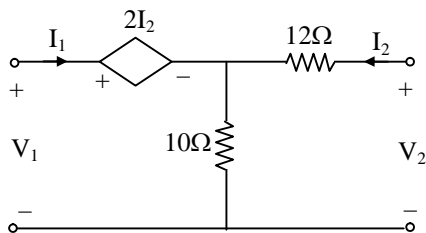

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

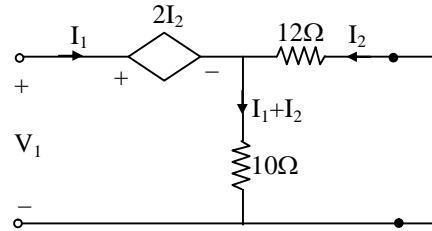

Applying KVL,


$$\Rightarrow -10 (I_1+I_2) -12I_2 = 0 \Rightarrow -10 I_1 = 22I_2$$

$$\Rightarrow \frac{I_1}{-I_2} = 2.2$$

$$\therefore D = 2.2$$

09. Ans: (a)

Sol: Given network,

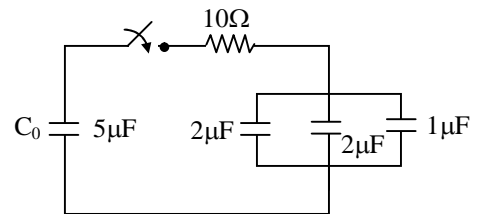


Initial charge in $C_0 = 500\mu C$

\Rightarrow Initial voltage across capacitor C_0 is


$$V_0 = \frac{q}{C_0} = \frac{500\mu}{5\mu} = 100V$$

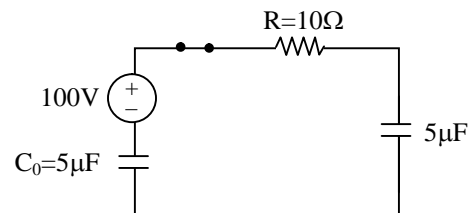The equivalent, circuit after the switch is closed is





Convert into Laplace domain

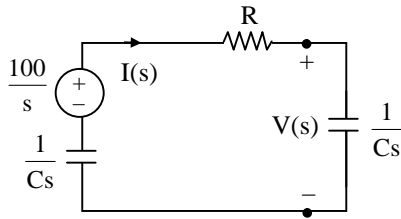

$$\Rightarrow I(s) = \frac{100/s}{R + \frac{2}{Cs}}$$

$$I(s) = \frac{100}{R \left(s + \frac{2}{RC} \right)}$$

And $V(s) = \frac{1}{Cs} I(s)$

$$= \frac{1}{Cs} \cdot \frac{100}{R \left(s + \frac{2}{RC} \right)}$$

Steady state value of $v(t)$ is $= \lim_{s \rightarrow 0} sV(s)$

$$= \lim_{s \rightarrow 0} s \cdot \frac{100}{s(RCs + 2)}$$

$$= 50V$$

\therefore Steady state voltage across $1\mu F$ capacitor

$= 50V$


\therefore Charge in the $1\mu F$ capacitor $q = CV$

$$= 1\mu \times 50$$


$$= 50 \mu C$$

10. Ans: (c)

Sol: Given network

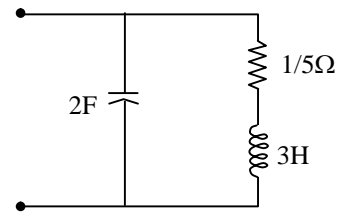


The dual of the above network is

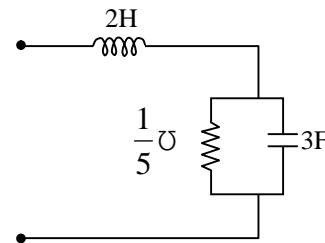

11. Ans: (b)

Sol: The wave form is as shown below

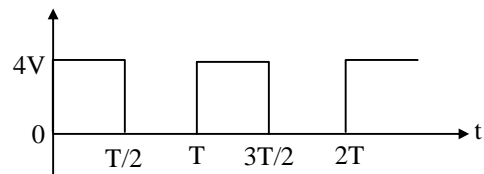

$$V_{\text{rms}}^2 = \frac{1}{T} \int_0^{T/2} (4)^2 dt$$


$$\Rightarrow V_{\text{rms}}^2 = \frac{1}{T} \times 16 \times T/2 = 8$$

$$\Rightarrow V_{\text{rms}} = 2\sqrt{2}V$$






12. Ans: (b)

Sol: Given circuit

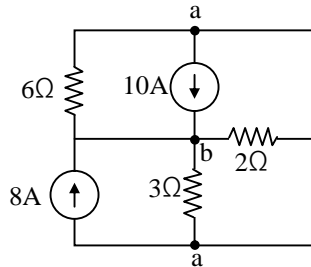

The above circuit can be redrawn as

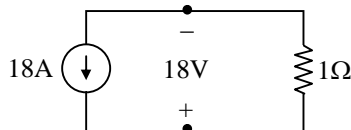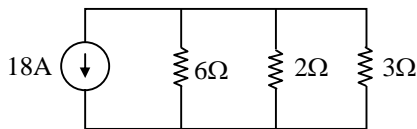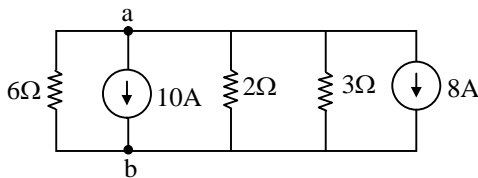

⇒ Total power delivered by the sources =
 $18 \times 18 = 324\text{W}$

13. Ans: (d)

Sol: At the cut off frequency $I = \frac{I_m}{\sqrt{2}}$

$$\Rightarrow \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{V}{\sqrt{2}R}$$

$$\Rightarrow \left(\omega L - \frac{1}{\omega C}\right)^2 = R^2 \Rightarrow \left(\omega L - \frac{1}{\omega C}\right) = \pm R$$

At the lower cut off frequency ω_1 ,


$$\omega_1 L < \frac{1}{\omega_1 C}$$

$$\therefore \omega_1 L - \frac{1}{\omega_1 C} = -R$$

⇒ Net reactance = $-R$

14. Ans: (a)

Sol:

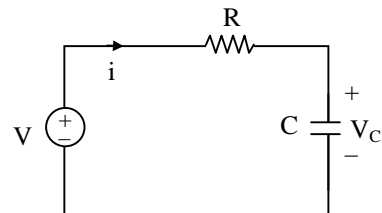

Under steady state condition $V_C = V = 100\text{V}$

$$\text{And } i(t) = \frac{V}{R} e^{-t/RC}$$

Energy dissipated by the resistor

$$E_R = \int_0^{\infty} i^2 R \, dt$$

$$E_R = \int_0^{\infty} \frac{V^2}{R^2} e^{-2t/RC} \cdot R \, dt$$

$$= \frac{V^2}{R} \left[\frac{e^{-2t/RC}}{-2/RC} \right]_0^{\infty} = \frac{-1}{2} CV^2 [0 - 1] = \frac{1}{2} CV^2$$

$$\Rightarrow E_R = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 1 \times 10^{-6} \times (100)^2 = 5\text{mJ}$$



15. Ans: (a)

Sol: We know, when two, 2-port networks are connected in parallel, their individual Y-parameters gets added.

∴ First, we need to convert given ABCD parameters to Y-parameters.

For 2-port network

Y-parameters are

$$\left. \begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned} \right\} (1)$$

ABCD parameters

$$\left. \begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned} \right\} (2)$$

Make $V_2 = 0$ to find Y_{11} & Y_{21}

Equation (2) becomes $V_1 = -BI_2$

$$I_1 = -DI_2$$

$$\therefore Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{D}{B} \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-1}{B}$$

Similarly, $V_1 = 0$, to find Y_{12} & Y_{22}

∴ From equation (2) $AV_2 = BI_2$

$$\Rightarrow V_2 = \frac{B}{A} I_2$$

$$I_1 = CV_2 - DI_2$$

$$I_1 = C \frac{B}{A} I_2 - DI_2 = \frac{CB - DA}{A} I_2$$

$$I_1 = \frac{BC - AD}{A} I_2$$

$$\text{But } I_2 = \frac{A}{B} V_2$$

$$\Rightarrow I_1 = \frac{BC - AD}{A} \frac{A}{B} V_2$$

$$\Rightarrow I_1 = \left(\frac{BC - AD}{B} \right) V_2 \dots\dots(3)$$

$$\therefore Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{BC - AD}{B}$$


And $I_1 = \frac{BC - AD}{B} I_2$ put this value in equation (3)

$$\frac{BC - AD}{A} I_2 = \frac{BC - AD}{B} V_2$$

$$I_2 = \frac{A}{B} V_2 \Rightarrow Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{A}{B}$$

Y-parameter matrix in terms of ABCD parameter is
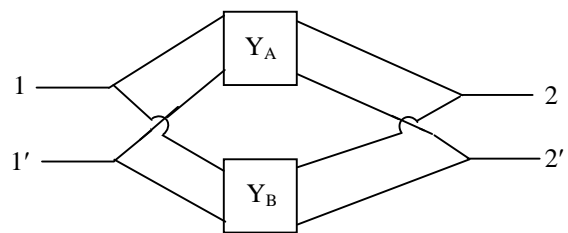
$$Y_T = \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ \frac{-1}{B} & \frac{A}{B} \end{bmatrix}$$



$$Y_T \text{ or } Y_{eq} = Y_A + Y_B$$

$$= \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ \frac{-1}{B} & \frac{A}{B} \end{bmatrix} + \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ \frac{-1}{B} & \frac{A}{B} \end{bmatrix}$$



$$Y_T \text{ or } Y_{eq} = \begin{bmatrix} 2\frac{D}{B} & 2\frac{(BC-AD)}{B} \\ -\frac{2}{B} & \frac{2A}{B} \end{bmatrix}$$

Now, again connect back to ABCD parameters

$$\left. \begin{aligned} I_1 &= \frac{2D}{B}V_1 + 2\frac{(BC-AD)}{B}V_2 \\ I_2 &= -\frac{2}{B}V_1 + \frac{2A}{B}V_2 \end{aligned} \right\} (4)$$

$$\text{Make } V_2 = 0 \quad I_1 = \frac{2D}{B}V_1$$

$$I_2 = -\frac{2}{B}V_1$$

$$B_T = -\frac{V_1}{I_2} \Big|_{V_2=0} = \frac{B}{2} = 0.5B$$

$$D_T = -\frac{I_1}{I_2} \Big|_{V_2=0} = \frac{2D/B}{2/B} = D$$

Make $I_2 = 0$, equation (4) becomes

$$\begin{aligned} V_1 = AV_2 \text{ \& } I_1 &= \frac{2D}{B}V_1 + 2\frac{(BC-AD)}{B}V_2 \\ &= \frac{2D}{B}AV_2 + \frac{(2BC-2AD)}{B}V_2 \\ &= \left(\frac{2AD+2BC-2AD}{B} \right) V_2 \end{aligned}$$

$$I_1 = 2CV_2$$

$$\therefore A_T = \frac{V_1}{V_2} = A$$

$$C_T = \frac{I_1}{V_2} = 2C$$


$$[T] = \begin{bmatrix} A_T & B_T \\ C_T & D_T \end{bmatrix} = \begin{bmatrix} A & 0.5B \\ 2C & D \end{bmatrix}$$

16. Ans: (c)

Sol: Given network function

$$F(s) = \frac{(s+2)}{(s+1)(s+3)}$$

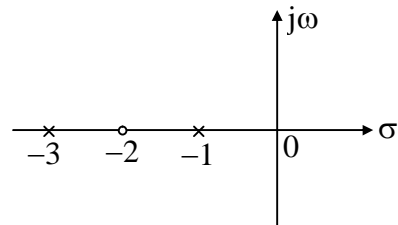The pole zero pattern for the above network function is as shown below



As we can see from above pole zero plot poles and zeros alternate on negative real axis and nearest to the origin is a pole.


\therefore It can be realized as RC impedance function or RL admittance function.

17. Ans: (a)

Sol: Assume the circuit is in steady state before the switch opens.

\Rightarrow The inductor will acts as short circuit.

Then the circuit at $t = 0^-$ is

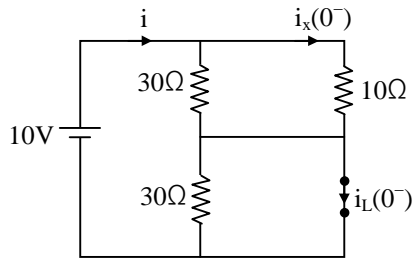

Equivalent resistance seen by the 10V voltage source is $= 30 \parallel 10$

$$= \frac{30 \times 10}{40} = 7.5 \Omega$$


$$\Rightarrow i = \frac{10}{7.5} = \frac{4}{3} \text{ A}$$

$$\therefore i_x(0^-) = i \times \frac{30}{40}$$


$$= \frac{4}{3} \times \frac{3}{4} = 1 \text{ A}$$

18. Ans: (a)

$$\text{Sol: } Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

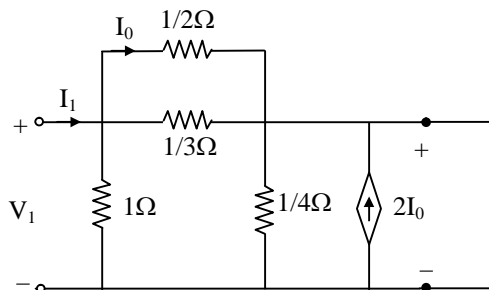

The equivalent network becomes

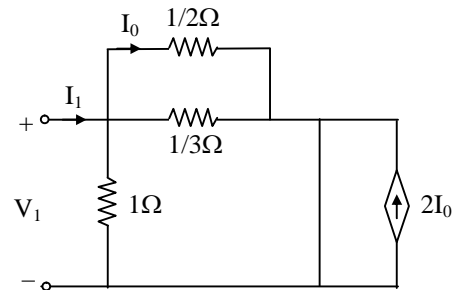


Equivalent resistance seen by the port 1 is =

$$1 \parallel \frac{1}{2} \parallel \frac{1}{3} = \frac{1}{6} \Omega$$

$$\Rightarrow V_1 = \frac{1}{6} I_1 \Rightarrow \frac{I_1}{V_1} = 6 \text{ S} \Rightarrow Y_{11} = 6 \text{ S}$$

19. Ans: (d)

Sol: Given network

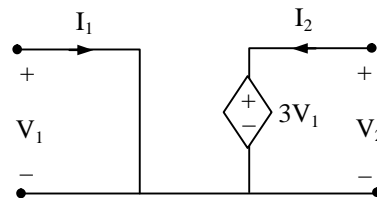

As we are unable to write I_1 in terms of V_1 and V_2 therefore Y parameters don't exist.


20. Ans: (a)

Sol: For parallel resonant circuit,

$$\text{Admittance, } Y = \frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right)$$

$$\text{Susceptance } B = \omega C - \frac{1}{\omega L}$$

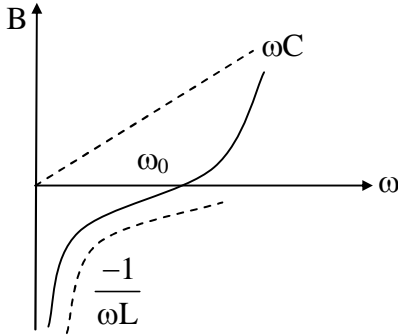
The plot of susceptance is as shown below



21. Ans: (c)

Sol: Assume the circuit is in steady state before the switch is changed from a to b
 \Rightarrow inductor will act as short circuit.

Then the circuit is

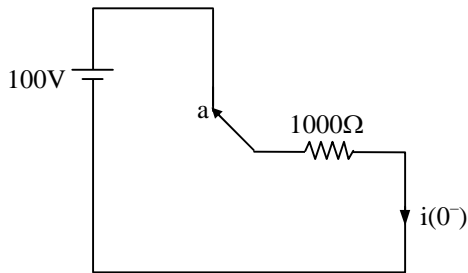


$$\Rightarrow i(0^-) = \frac{100}{1000} = 0.1 \text{ A}$$

And initial voltage across the capacitor is

$$V_C(0^-) = 0 \text{ V}$$

At $t = 0^+$ the equivalent circuit is

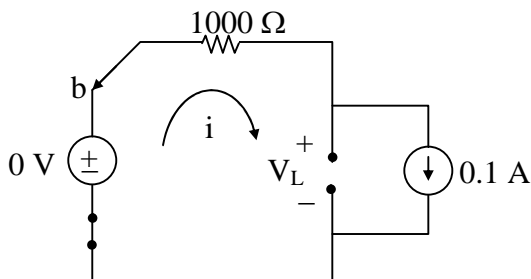

$$\Rightarrow V_L \text{ at } t = 0^+ \text{ is } = -100$$

$$\Rightarrow L \frac{di}{dt} = -100 \Rightarrow \frac{di}{dt} = -100$$

$$\therefore \frac{di}{dt} \text{ at } t = 0^+ \text{ is } = -100 \text{ A/sec.}$$

22. Ans: (b)

Sol: For


- RC driving point impedance function
- RC driving point admittance function
- RL driving point impedance function
- RL driving point admittance function

Poles and zeros should alternate only on negative real axis

23. Ans: (b)

Sol: Given $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$

The pole zero pattern is as shown below

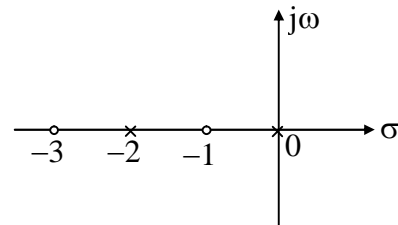


As we can see the poles and zeros alternate on negative real axis and nearest to the origin is a pole.

\therefore It can be realized as RC driving point impedance



$$Z(S) = 1 + \frac{2s + 3}{s(s + 2)} = 1 + \frac{3/2}{s} + \frac{1/2}{s + 2}$$

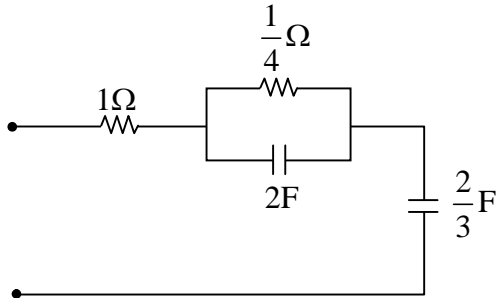
The network for the above impedance function is as shown below




∴ Two energy storage elements are present.

24. Ans: (d)

Sol: At $t = 0^+$ the circuit is

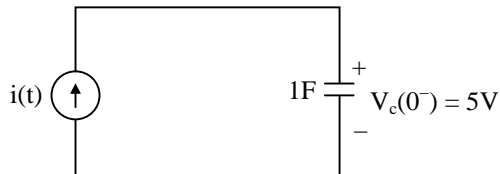

Convert into Laplace domain

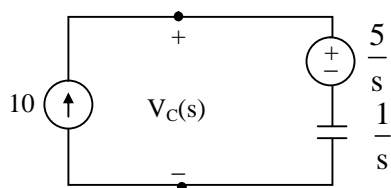

$$\Rightarrow V_C(s) = \frac{5}{s} + \frac{1}{s} \times 10 = \frac{15}{s}$$


$$\Rightarrow v_C(t) = 15 u(t)$$

$$\text{At } t = 0^+ \Rightarrow u(t=0^+) = 1$$

$$\Rightarrow v_C(0^+) = 15 \text{ V}$$

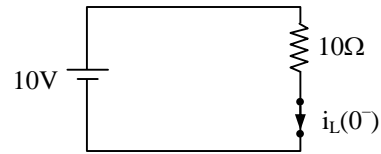
25. Ans: (b)

Sol: The equivalent network at $t = 0^-$ is



$$\Rightarrow i_L(0^-) = \frac{10}{10} = 1 \text{ A}$$


At $t = 0^+$ the network is

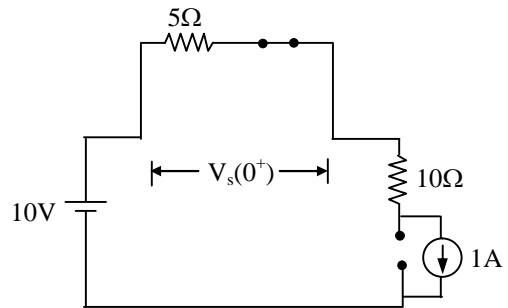

$$\Rightarrow V_S(t = 0^+) = 5 \times 1 = 5 \text{ V}$$


26. Ans: (d)

Sol: At $t = 0^-$ the network is

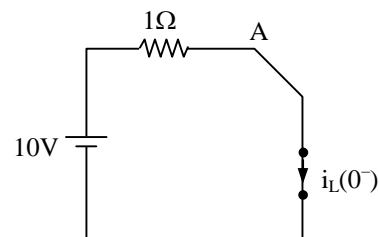


$$\Rightarrow i_L(0^-) = \frac{10}{1} = 10 \text{ A}$$

At $t = 0^+$ the network is

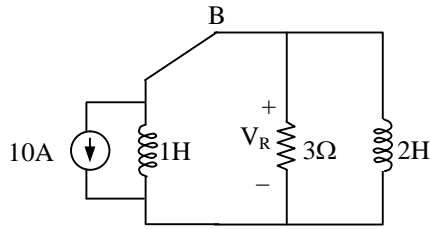

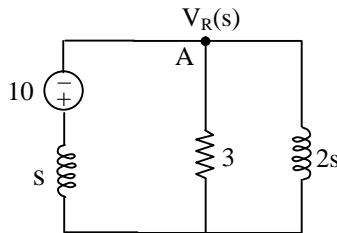Convert the above circuit into Laplace domain



Applying KCL at node 'A'

$$\Rightarrow \frac{V_R(s) + 10}{s} + \frac{V_R(s)}{3} + \frac{V_R(s)}{2s} = 0$$

$$\Rightarrow V_R(s) \left[\frac{3}{2s} + \frac{1}{3} \right] = -\frac{10}{s}$$

$$\Rightarrow V_R(s) = \frac{-30}{s + \frac{9}{2}} \Rightarrow v_R(t) = -30 e^{-4.5t}$$

As $t \rightarrow \infty \Rightarrow V_R(t) = 0V$


27. Ans: (a)

Sol: Statement-1 is correct because in case of charged bodies of arbitrary shape, it is difficult to find the actual distance between them.

Statement-2 is incorrect as Coulomb's law is valid only when the point charges are at rest.

28. Ans: (b)

Sol:

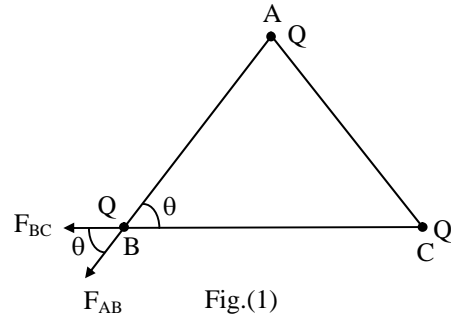

Consider string AB, the net force on string AB is given as,

$$F = F_{AB} + F_{BC} \cos \theta$$

Where,

$$F_{AB} = F_{BC} = \frac{Q^2}{4\pi\epsilon_0 a^2} \text{ and } \theta = 60^\circ$$

$$\Rightarrow F = \frac{Q^2}{4\pi\epsilon_0 a^2} (1 + \cos 60^\circ)$$

$$= \frac{Q^2}{4\pi\epsilon_0 a^2} \left(1 + \frac{1}{2} \right)$$

$$= \frac{3Q^2}{8\pi\epsilon_0 a^2} \dots\dots\dots (1)$$

For string AB to break due to electrostatic force,

$$F \geq 3$$

From equation -1,

$$\frac{3Q^2}{8\pi\epsilon_0 a^2} \geq 3 \Rightarrow Q^2 \geq 8\pi\epsilon_0 a^2$$

$$\text{or, } Q_{\min} = \sqrt{8\pi\epsilon_0} a,$$



ESE | GATE - 2019

LONG TERM BATCHES

EC | EE | ME | CE | CS | IN | PI

Start Early, Gain Surely



Pioneer to Leader



Dedicated Service



Experienced Faculty from Central Pool

Admissions are open at all our centers

H. O. : Hyderabad : Ph : 040-23234418,19,20

Bangalore
9341299966

Kukatpally
040-6597 4465

Delhi
9205282121

Bhopal
0755-2554512

Pune
020-25535950

Bhubaneswar
0674-2540340

Lucknow
808199966

Patna
9308699966

Chennai
044-42123289

Vijayawada
0866-2490001

Vishakapatnam
0891-6616001

Tirupathi
0877-2244388

Kolkata
8297899966

29. Ans: (d)

Sol: Given data, $H_1 = 2A/m$

Let, I be the current in the loop and a be the radius of the loop, then H at the centre of the loop is given as,

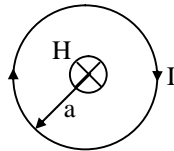


Fig.(1)

$$H = \frac{I}{2a} \text{ A/m} \Rightarrow H \propto \frac{I}{a}$$

$$\Rightarrow \frac{H_2}{H_1} = \left(\frac{I_2}{I_1} \right) \left(\frac{a_1}{a_2} \right)$$

$$\therefore I_2 = 2I_1 \text{ \& } a_2 = \frac{a_1}{2} \Rightarrow H_2 = 2 \times 2 \times H_1 = 4H_1$$

$$\Rightarrow H_2 = 4 \times 2 = 8A/m$$

30. Ans: (a)

Sol: Given data,

$$\vec{J} = kx \hat{a}_x - 5y \hat{a}_y$$

Then for a steady current i.e, charge entering and leaving a cross-section of the conductor to be equal at any time,

$$\nabla \cdot \vec{J} = 0$$

$$\{\text{Continuity equation, } \nabla \cdot \vec{J} = -\frac{\partial \rho_v}{\partial t}$$

but $\rho_v = \text{constant}\}$

$$\Rightarrow \left(\frac{\partial}{\partial x} \hat{a}_x + \frac{\partial}{\partial y} \hat{a}_y + \frac{\partial}{\partial z} \hat{a}_z \right) \cdot (kx \hat{a}_x - 5y \hat{a}_y) = 0$$

$$k - 5 = 0 \Rightarrow k = 5$$



31. Ans: (c)

Sol: 1. $\nabla \cdot (\nabla \times \vec{A}) \equiv 0$ (correct)

i.e, divergence of curl of a vector is always zero.

2. $\nabla \times (\nabla \cdot V) \equiv 0$ (correct) i.e; curl of gradient of a scalar is always zero.

3. $\int_s (\nabla \times \vec{A}) \cdot \vec{ds} = \oint_L \vec{A} \cdot d\vec{l}$ (correct)

The above expression is the Stoke's theorem which says that closed line integral of a vector is equal to the surface integral of the curl of that vector.

4. $\int_v (\nabla \times \vec{A}) \cdot d\vec{v} = \int_s \vec{A} \cdot \vec{ds}$ (incorrect)

Gauss's divergence theorems is given as,

$$\int_v (\nabla \cdot \vec{A}) \cdot d\vec{v} = \int_s \vec{A} \cdot \vec{ds}$$

Which says that closed surface integral of a vector is equal to the volume integral of the diversion of that vector.

32. Ans: (b)

Sol: Electric flux:

According to Gauss's law, the surface integral of the electric field intensity gives the amount of electric flux.

$$\oint \vec{E} \cdot \vec{ds} = \frac{q}{\epsilon_0} = \phi_{\text{electrical}}$$

$$\Rightarrow \text{unit of } \phi_e = \frac{\text{Coulombs}}{\text{Coulombs}^2 / \text{Newton} - \text{meter}^2} \\ = \text{Newton-meter}^2 / \text{Coulombs}.$$

33. Ans: (c)

Sol: Statement-1 is correct

For a linear dielectric

Polarization (P) \propto E (Electric field)

$$\Rightarrow P = \chi_e E$$

χ_e is susceptiblity (constant for a linear dielectric)

A capacitor with a linear dielectric has capacitance independent of the charge on the plates and their potential difference, rather the capacitance is equal to the ratio of the charge on the plate to that of the potential

difference between them. $C = \frac{Q}{V}$

Statement-2 is correct

As the capacitor is connected to battery, hence voltage 'V' is fixed.

Let Q_d and Q_a be the charge on the plates for dielectric and air case, then,

$$\frac{Q_d}{Q_a} = \frac{C_d V}{C_a V} = \frac{C_d}{C_a} = \frac{\epsilon_0 \epsilon_r A}{d} \times \frac{d}{\epsilon_0 A} \\ = \epsilon_r$$

$$\therefore Q_d = 2Q_a$$

$$\Rightarrow \epsilon_r = 2$$

$$\text{But, } \epsilon_r = 1 + \chi_e = 2$$

$$\Rightarrow \chi_e = 1$$



34. Ans: (b)

Sol:

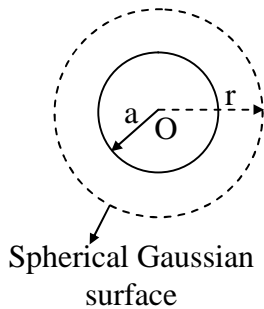


Fig. 1

Applying Gauss's law,

$$\oiint \vec{D} \cdot d\vec{s} = Q_{\text{enclosed}}$$

$$D(4\pi r^2) = \rho \frac{4}{3} \pi a^3$$

$$\Rightarrow D = \frac{\rho a^3}{3r^2}$$

At the surface of the sphere, $r = a$

$$\Rightarrow D = \frac{\rho a}{3}$$

35. Ans: (d)

Sol: Statement -1 is correct as angle between \vec{r}

and $\nabla \times \vec{r}$ is 90° , therefore,

$$\vec{r} \cdot (\nabla \times \vec{r}) = 0$$

Statement -2 is correct as

$$\nabla \cdot \vec{r} = \left(\frac{\partial}{\partial x} \hat{a}_x + \frac{\partial}{\partial x} \hat{a}_y + \frac{\partial}{\partial x} \hat{a}_z \right) \cdot (x\hat{a}_x + y\hat{a}_y + z\hat{a}_z)$$

$$\Rightarrow \nabla \cdot \vec{r} = 3$$

Statement - 3 is correct as,

$$\begin{aligned} \nabla \cdot (\vec{r} \cdot \vec{r}) &= \left(\frac{\partial}{\partial x} \hat{a}_x + \frac{\partial}{\partial x} \hat{a}_y + \frac{\partial}{\partial x} \hat{a}_z \right) \cdot (x^2 + y^2 + z^2) \\ &= 2x\hat{a}_x + 2y\hat{a}_y + 2z\hat{a}_z \end{aligned}$$

$$= 2(x\hat{a}_x + y\hat{a}_y + z\hat{a}_z)$$

$$= 2\vec{r}$$

Statement-4 is correct as, angle between

∇ and $\nabla \times \vec{r}$ is 90°

Therefore,

$$\nabla \cdot (\nabla \times \vec{r}) = 0$$

36. Ans: (d)

Sol: As the sphere is conducting and has potential 0 on its surface (grounded)

Hence, $V_A = V_B = 0$

Where, V_A and V_B are the potential at points

A and B due to q and q' , hence

For $V_A = 0$

$$\Rightarrow \frac{q}{4\pi\epsilon_0(d-a)} + \frac{q'}{4\pi\epsilon_0(a-b)} = 0 \dots\dots\dots (1)$$

For $V_B = 0$,

$$\Rightarrow \frac{q}{4\pi\epsilon_0(d+a)} + \frac{q'}{4\pi\epsilon_0(a+b)} = 0 \dots\dots\dots (2)$$

$$\text{Eqn (1)} \Rightarrow q' = -q \frac{(a-b)}{(d-a)}$$

$$\text{Eqn (2)} \Rightarrow q' = -q \frac{(a+b)}{(d+a)}$$

$$\Rightarrow \frac{a-b}{d-a} = \frac{a+b}{d+a}$$

$$ad + a^2 - bd - ab = ad - a^2 + bd - ab$$

$$\Rightarrow 2a^2 = 2bd \Rightarrow a^2 = bd$$

$$\Rightarrow b = \frac{a^2}{d} \dots\dots\dots (3)$$



$$\text{Then, } q' = \frac{-q\left(a - \frac{a^2}{d}\right)}{(d-a)} = \frac{-qa\left(\frac{d-a}{d}\right)}{(d-a)}$$

$$\Rightarrow q' = -\frac{qa}{d} \dots\dots\dots (4)$$

37. Ans: (a)

Sol: Ionic polarization takes place by displacement of cations and anions. It is independent of temperature

$$\alpha_i = \frac{e^2}{\omega^2 m}$$

Ionic Polarizability is inversely proportional to the square of natural frequency (ω)

38. Ans: (b)

Sol: Polarization (P) = $\epsilon_0(\epsilon_r - 1)E$

$$= 8.854 \times 10^{-12} \times (8 - 1) \times 10 \times 10^3$$

$$= 6.2 \times 10^{-7}$$

39. Ans: (b)

Sol: If the radius $X = 0.155$, a more stable configuration is possible with three anions bonding with cation. This form a stable structure only upto an X value of 0.225 for $0.155 < X < 0.225$ the anions do not touch each other.

40. Ans: (c)

41. Ans: (a)

42. Ans: (b)

Sol: $\rho = \frac{1}{ne\mu} \Rightarrow \mu = \frac{1}{nep}$

$$= \frac{1}{6 \times 10^{28} \times 1.6 \times 10^{-19} \times 1.54 \times 10^{-8}}$$

$$= 6.76 \times 10^{-3} \text{ m}^2/\text{V-s}$$

43. Ans: (c)

Sol: $H_C = H_0 \left[1 - \left(\frac{T}{T_C} \right)^2 \right]$

$$1 \times 10^5 = 2 \times 10^5 \left[1 - \left(\frac{8}{T_C} \right)^2 \right]$$

$$\frac{1 \times 10^5}{2 \times 10^5} = 1 - \left(\frac{8}{T_C} \right)^2$$

$$\frac{1 \times 10^5}{2 \times 10^5} + \left(\frac{8}{T_C} \right)^2 = 1$$

$$\frac{64}{T_C^2} + 0.5 = 1 \Rightarrow T_C^2 = \frac{64}{0.5}$$

$$T_C = 11.31 \text{ K}$$

44. Ans: (b)

Sol: $J_c = \frac{i_c}{A} = \frac{H_C \times 2\pi R}{\pi R^2} = \frac{2H_C}{R}$

45. Ans: (a)

Sol: Based on F.London and H.London research, magnetic flux density is allowed by super conductor up to some layers from the surface.



London penetration depth: It is the depth from the surface of super conductor upto which flux density is decreased by 63%.

$$B = B_0 e^{\frac{-x}{\lambda_L}}$$

B = Flux density at a depth 'X'

B_0 = flux density at surface of super conductor

λ_L = London penetration depth

46. Ans: (d)

Sol: Hall angle $\tan \theta_H = \mu B = 0.041 \times 0.1 = 0.0041$

$$\theta_H = \tan^{-1}(0.0041)$$

$$\theta_H = 0.2349$$

47. Ans: (a)

48. Ans: (c)

Sol: Total magnetic moment = $N \times i \times A$

$$= 500 \times 20 \times 10^{-3} \times \pi (2 \times 10^{-2})^2$$

$$= 500 \times 20 \times 10^{-3} \times 4\pi \times 10^{-4}$$

$$= 4\pi \times 10^{-3} \text{ A-m}^2$$

49. Ans: (a)

Sol: Magnetic flux density (b) = $88 \times 10^{-4} \text{ Wb/m}^2$

Field strength (H) = 100 A/m

$$\mu_R = \frac{\mu}{\mu_0} = \frac{B}{H\mu_0}$$

$$= \frac{88 \times 10^{-4}}{100 \times 4\pi \times 10^{-7}} = 70$$


50. Ans: (a)

Sol: The hysteresis loop of ferromagnetic material depends on

1. Temperature
2. Crystallographic imperfection
3. Cold working

51. Ans: (a)

Sol:

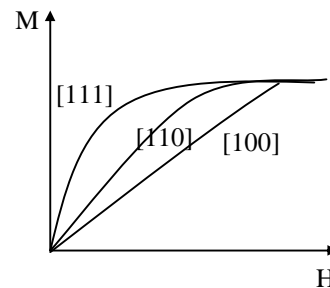

52. Ans: (b)

Sol: Magneto rheological materials has the ability to increase viscosity drastically with applied field.

53. Ans: (a)

54. Ans: (c)

55. Ans: (d)

56. Ans: (a)

Sol: Weiss-Domain Theory: Based on Weiss Domain theory in a domain all the dipoles are aligned in a particular direction. If the magnetic field is applied Domain growth takes place in the field direction and at higher field, inside domain dipole relation takes place.

GATE - 2018

ONLINE TEST SERIES

No. of Tests : 62

All tests will be available till
12th February 2018

ESE - 2018 PRELIMS

ONLINE TEST SERIES

No. of Tests : 44

All tests will be available till
07th January 2018

ISRO - 2017

ONLINE TEST SERIES

No. of Tests : 15

All tests will be available till
25th December 2017

★ HIGHLIGHTS ★

- Detailed solutions are available.
- **All India rank** will be given for each test.
- Comparison with all India toppers of **ACE** students.

 www.aceenggacademy.com

 testseries@aceenggacademy.com

57. Ans: (a)

Sol: Output voltage = $t \times g \times p$
 $= 2 \times 10^{-3} \times 0.055 \times 1.25 \times 10^6$
 $= 137.5 \text{ V}$

58. Ans: (d)

Sol: Ga-As compound is a zinc blende structure

59. Ans: (b)

Sol: $\sqrt{2} a = 4R$

$$a = \frac{4R}{\sqrt{2}}$$

$$d_{111} = \frac{a}{\sqrt{h^2 + k^2 + \ell^2}}$$

$$= \frac{4(0.128 \times 10^{-9})}{\sqrt{2} \times \sqrt{1^2 + 1^2 + 1^2}} = 2 \text{ \AA}$$

60. Ans: (d)

Sol: X \rightarrow 1 $(-1, 2, \infty)$

$$Y \rightarrow 2 \quad \left(\frac{-1}{1}, \frac{1}{2}, \frac{1}{\infty}\right) = (\bar{2}10)$$

Z \rightarrow ∞

61. Ans: (d)

Sol: The bullet proof jacket is made up of aramid fiber reinforced polymer (AFRB) with reinforcement phase is Aramid and matrix phase is polymer.



62. Ans: (d)

Sol: The bonding in ceramics is predominantly ionic, it consists of anions and cations. The crystal structure of ceramics is influenced by the radius ratios of the ions. The coordination number depends on the radius of the bonding ions. Ceramics are classified according to their crystal structure as AX, AX₂, ABX₃ and AB₂X₄ types.

Examples under each type are given below:

AX : NaCl, CsCl, ZnS

AX₂: SiO₂, CaF₂, PuO₂, ThO₂

ABX₃: BaTiO₃, SrZrO₃, SrSnO₃

AB₂X₄: MgAl₂O₄, FeAl₂O₄

63. Ans: (c)

Sol: If the temperature of metal increases, the lattice vibration in the crystal structure increases. Hence collision frequency increases and relaxation time decreases. Due to that resistivity of metal increases.

64. Ans: (c)

Sol: Ceramics have high melting point and can withstand high temperature.

65. Ans: (b)

Sol: Laplacian equation

$$\nabla^2 V = 0 \rightarrow (1)$$

But we know, $\nabla^2 V = -\frac{\rho_v}{\epsilon}$ from Poisson's

equation

Therefore Laplacian equation is true for charge free region where $\rho_v = 0$


Every physical problem must contain at least one conducting boundary but may contain more than one.

Solution of Laplace's equation with two different methods (valid methods) lead to same solution. Since E field is harmonic (conservative).

66. Ans: (d)

Sol: Statement I is incorrect as

$$\int_S \vec{B} \cdot d\vec{s} \neq 0$$

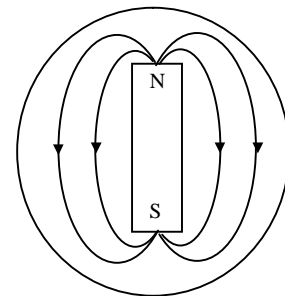

Maxwell equation: $\oint \vec{B} \cdot d\vec{s} = 0$

i.e., net flux leaving closed surface is zero.

When surface is open

$$\int \vec{B} \cdot d\vec{s} = \psi_m \rightarrow \text{weber}$$

Statement II is correct as

Tubes of magnetic flux have no source (or) sink i.e. monopoles do not exist in case of magnetic field.



67. Ans: (a)

Sol: \vec{N} When AC field is applied to a dielectric material, then dielectric constant of material is no longer real

It is having both real part as well as imaginary part

$$\epsilon_r = \epsilon_r' - j \epsilon_r''$$

$j\epsilon_r''$ part (Imaginary part) of ϵ_r is due to power loss in material.


- When AC field is applied to dielectric material, ϵ_r becomes complex quantity as a result power loss in dielectric material.

68. Ans: (b)

Sol: The antiferro magnetic material depends on

Neel's law

$$\chi = \frac{C}{T - T_N}$$

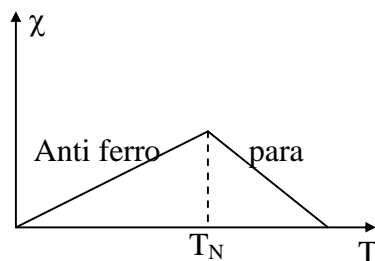

69. Ans: (d)

Sol: Impressed voltage $V = (100 - j90)$ V

$$\text{Current } I = (3 - j4) \text{ A}$$

$$\text{Complex power, } S = V I^*$$

$$= (100 - j90)(3 + j4) = (660 + j130) \text{ VA}$$

\therefore Real power = 660 W \therefore Statement (I) is false.

70. Ans: (b)

71. Ans: (d)

Sol: Equivalent network obtained from $\Delta - Y$ transformation relation is valid for any frequency.

So statement (I) is false.

72. Ans: (b)

73. Ans: (b)

Sol: Poly crystal materials are stronger than single crystal material because they require more stresses to initiate slip and yielding. Poly crystalline materials there are many preferred planes and direction for different grains due to their random orientation.

74. Ans: (a)

Sol: BaTiO₃ crystal is Ferroelectric material upto 120°C, due to non-centro symmetric (asymmetric) structure. But above 120°C it become centro-symmetric and hence it loses its ferroelectric character.

75. Ans: (d)

Sol: Statement I is incorrect

because when there is no charge inside the conductor the electric field inside a conductor is zero not infinity.

Statement II is correct as

Gauss law: Electric flux leaving any closed surface is equal to the charge enclosed.

In case of a conductor as the charge enclosed by any closed surface inside a conductor is zero hence there should not be any electric field inside the conductor.

GATE TOPPERS

GATE 2017

1 EC PRAMOD	1 ME SUDHEER	1 ME HASAN ASIF	1 EE SHEKH SINGH	1 CE ARICK RAKESH	1 CS DEVAL N PATEL	1 IN NAVEEN	2 EC SREE KALYANI
2 CE PUNEET KHANNA	2 IN RAHUL MAHATO	2 IN SHUBHAM BANSAL	2 PI GURJAY PRADEPTAL	3 EC KARUN	3 EE RAVI TEJA	3 ME PRADIP BOBACE	3 CS RAVI SHANKAR
3 CE ANKUR TIRATHI	4 EC SONU SHARMA	4 EE SARFRAJ NAWAZ	4 CE CHIRAG MITTAL	4 ME GAUSH ALAM	4 IN MONTI	4 PI Sanghavi Adhikari	5 IN VRAJESH SHAH
5 PI ANKIT TIWARI	6 EC LIPITA SAI LIPPU	6 CS MEGHASHAYAM	6 EE RAJASEKHAR REDDY	6 IN RAMESH KAMILLA	6 PI PINAL KUMAR RANA	7 IN RANJAY WISHRA	8 ME DIVYANSHU JHA
8 PI Anam Bhargava	9 EC Anand Upadhyay	9 CS Nihar Kumar Singh	9 ME SHRUTI KUMAR JHA	10 EC AMIT KAWAT	10 ME ANAND DUTTA	10 EE SUDAJ DASH	10 IN HARSH KUMAR

ESE TOPPERS

ESE 2017

CE		E&T		EE		ME	
1 CE NAMIT JAIN	2 CE PRAVIND SINGH	2 E&T RUCHANSHU CHAKRABARTY	3 E&T RISHU KUMAR	2 EE PRIYATI KUMAR	3 EE NAGU CHAKRA VERTY	3 ME SAURASH	4 ME AMIT KUMAR SAH
3 CE ANKIT	6 CE RISHAB DASGUPTA	5 E&T AMIT GAUTAM	6 E&T SUBHANSHU MISHRA	4 EE HARSHIT KUMAR SINGH	5 EE NIGEL KUMAR	6 ME ANAND GUPTA	7 ME DHIRUJ JHA
8 CE ADITHYAN SINGH	9 CE HIMANSHU GAUTAM	7 E&T DEVENDRANATH PRANAV KUMAR	8 E&T DEEPIKA GOYAL	6 EE DUSHYANT SINGH	8 EE ARPOORVA GUPTA	9 ME ANAND ACHARYA GUPTA	
10 CE AVUSH DUBEY	7 IN TOP 10 RANKS	9 E&T ABHIRAM PRASAD SINGH	10 E&T UMESH	9 EE KIRAN BASU KONERU			5 IN TOP 10 RANKS
 7 All India 1 st Rank in ESE.		8 IN TOP 10 RANKS and many more...		7 IN TOP 10 RANKS		 27 Ranks in Top 10 in ESE-2017	



ACE

Engineering Academy

Leading Institute for ESE/GATE/PSUs